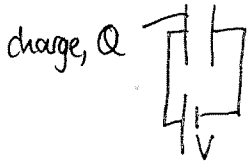


① 1.1 parallel plate capacitor $C = \epsilon_0 A/d$



(a) d increases $\Rightarrow C$ decreases [B]

(b) $Q = CV$, V is fixed, C decreases $\Rightarrow Q$ decreases [B]

(c) energy $U = \frac{1}{2} CV^2$, V is fixed, C decreases $\Rightarrow U$ decreases [B]

1.2

(a)




to remain overall neutral, plate 2 must have a charge $-Q$.

(b) all charge "pushed off" plate 2 must end up on plate 3 \Rightarrow charge on plate 3 is $+Q$



(c) in series $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ $= \frac{1}{C_{eq}}$

$$\frac{1}{C_{eq}} = \frac{1}{8nF} + \frac{1}{16nF} + \frac{1}{8nF} = \frac{2}{16nF} + \frac{1}{16nF} + \frac{2}{16nF} = \frac{5}{16nF} \Rightarrow C_{eq} = \frac{16}{5} nF = \underline{\underline{3.2nF}}$$

(d)

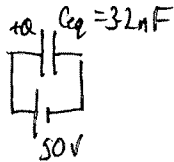

$$Q = C_{eq} V = \underline{160 nC}$$

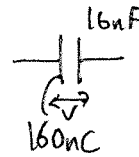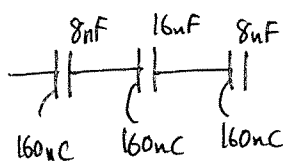

$$Q = CV \Rightarrow V = \frac{Q}{C} = \frac{160nC}{16nF} = \underline{10V}$$

1.3


(a) energy stored $U = \frac{1}{2} CV^2$

$$\Rightarrow C = \frac{2U}{V^2} = 2 \times \frac{1.0 \times 10^{-6} J}{(2.0V)^2} = \underline{0.5 \times 10^{-6} F}$$





(b) $Q = CV = (0.5 \times 10^{-6} F)(10V) = \underline{5 \times 10^{-6} C}$

the rightmost sphere is at lower potential $\Rightarrow q = \underline{-5.0 \times 10^{-6} C}$

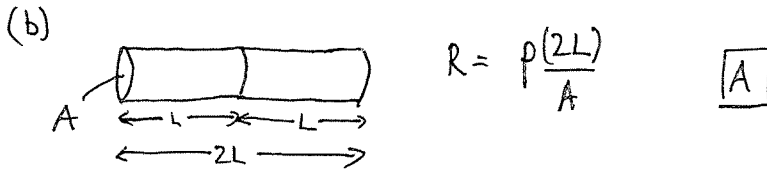
2) 2.1 (a) resistivity is independent of the dimensions of the resistor \Rightarrow B



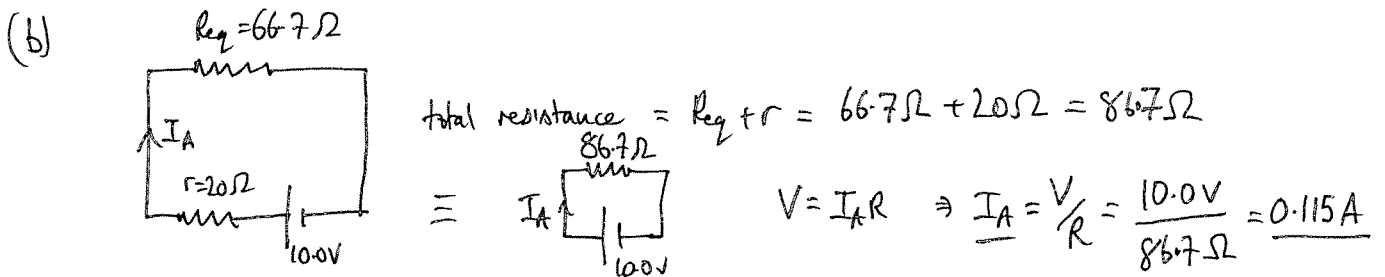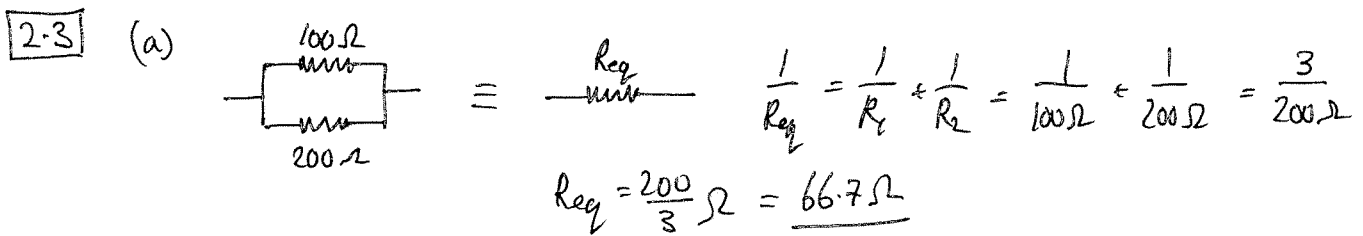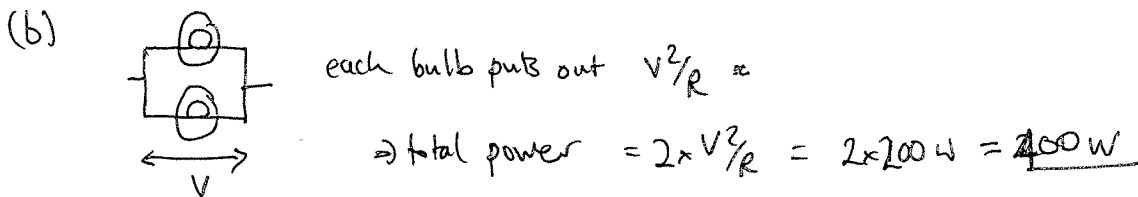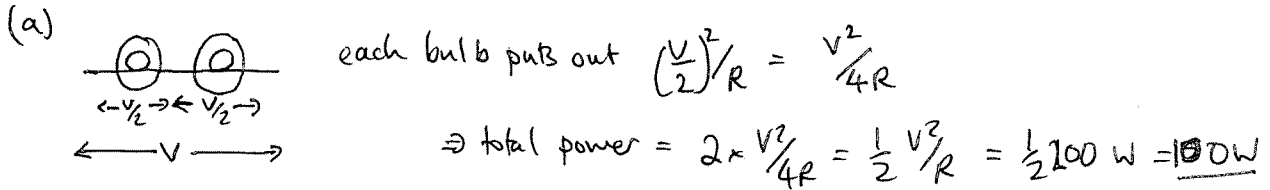2.2 voltage across bulb 1 = V
power output of bulb 1 = $V^2/R = 200 \text{ W}$




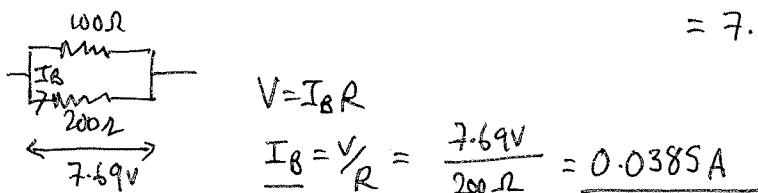Voltage drop across the R_{eq} resistance, $V = I_A R_{eq} = (0.115 \text{ A})(66.7 \Omega) = 7.69 \text{ V}$



(c) voltage drop across r : $V = I_A r = (0.115 \text{ A})(20 \Omega) = 2.3 \text{ V}$

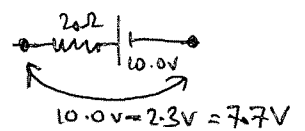(d) power lost in a resistor $\underline{P = I^2 r = (0.115 \text{ A})^2 (20 \Omega) = 0.265 \text{ W}}$




③ 3.1 (a) field lines leave positive charges & arrive at negative charges } $\Rightarrow q_1$ is positive, q_2 is negative

(b) density of field lines indicates field strength, lines are most dense at A.

(c)
$$|\vec{E}_1| = \frac{k|q_1|}{r^2} = \frac{(8.99 \times 10^9 \text{ Nm}^2/\text{C}^2)(1.0 \times 10^{-9} \text{ C})}{(1.0 \times 10^{-2} \text{ m})^2}$$


$$= 8.99 \times 10^4 \text{ N/C}$$

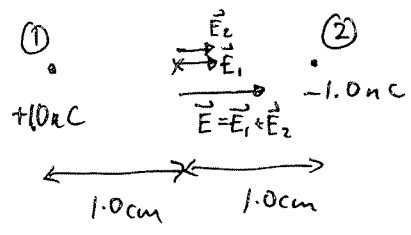

$$|\vec{E}_2| = \frac{k|q_2|}{r^2} = 8.99 \times 10^4 \text{ N/C}$$


$$E_{\text{tot}} = E_1 + E_2 = 1.80 \times 10^5 \text{ N/C}$$

3.2 (a)

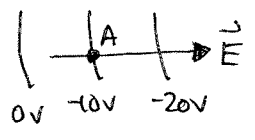

$\vec{F} = q\vec{E} \Rightarrow$ electric force points to the right [B]
 q_{proton} is positive

(b)

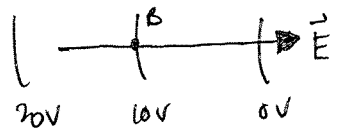


$\vec{F} = q\vec{E}$, q_{electron} is negative
 \Rightarrow electric force points to the left [A]

(c) [A] acceleration at A is larger - electric field at A is larger (hence so is the force) since the equipotentials are more closely spaced ($E = -\Delta V/\Delta s$)

(d) in moving from point B to A the potential energy of the 10C charge decreases from $(10\text{C})(10\text{V}) = 100\text{J}$ to $(10\text{C})(-10\text{V}) = -100\text{J}$,
 $U = qV$
 a decrease of energy of 200J


(e) C is on the same equipotential as B \Rightarrow change in potential energy is zero & no work is done by the electric field.

Extra Credit 15

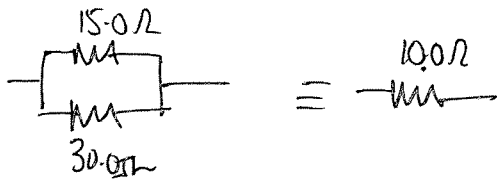

$$\frac{1}{R} = \frac{1}{30.0\Omega} + \frac{1}{15.0\Omega} = \frac{1}{30.0\Omega} + \frac{2}{30.0\Omega} = \frac{3}{30.0\Omega} = \frac{1}{10.0\Omega}$$

$$R = 10.0\Omega$$

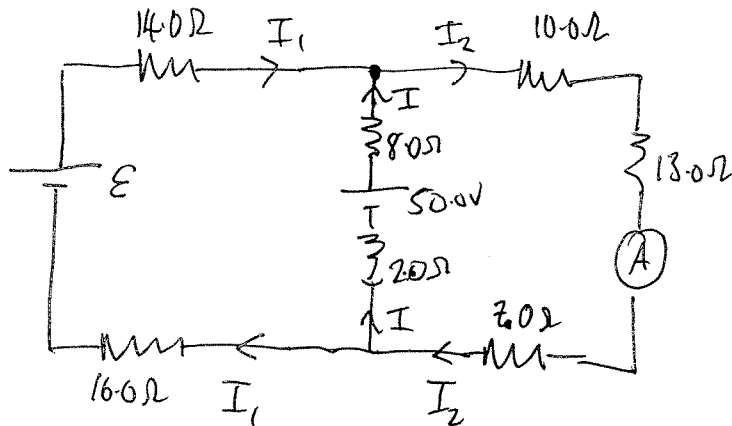

$$P = I^2 R \Rightarrow I = \sqrt{\frac{P}{R}}$$

$$I = \sqrt{\frac{11.52\text{W}}{8.0\Omega}} = 1.2\text{A}$$

• right most loop, clockwise

$$0 = -I_2(10.0\Omega) - I_2(13.0\Omega) - I_2(7.0\Omega) - I(2.0\Omega) + 50.0\text{V} - I(8.0\Omega)$$

$$0 = -I_2(30.0\Omega) - I(10.0\Omega) + 50.0\text{V}$$

$$= -I_2(30.0\Omega) - (1.2\text{A})(10.0\Omega) + 50.0\text{V}$$

$$= -I_2(30.0\Omega) - 12.0\text{V} + 50.0\text{V}$$

$$= -I_2(30.0\Omega) + 38.0\text{V}$$

$$I_2 = \frac{-38.0\text{V}}{-30.0\Omega} = 1.27\text{A}$$

current in the ammeter is 1.27 A
in the direction shown in the diagram

• left most loop, clockwise

$$0 = \mathcal{E} - I_1(14.0\Omega) + I(8.0\Omega) - 50.0\text{V} + I(2.0\Omega) - I_1(16.0\Omega)$$

$$0 = \mathcal{E} - I_1(30.0\Omega) + I(10.0\Omega) - 50.0\text{V}$$

at the upper junction $I_1 + I = I_2 \Rightarrow I_1 = I_2 - I = (1.2667 - 1.2)\text{A} = \underline{0.0667\text{A}}$

$$0 = \mathcal{E} - (0.0667\text{A})(30.0\Omega) + (1.2\text{A})(10.0\Omega) - 50.0\text{V}$$

$$= \mathcal{E} - 2.0\text{V} + 12.0\text{V} - 50.0\text{V} = \mathcal{E} - 40.0\text{V}$$

$$\Rightarrow \underline{\underline{\mathcal{E} = 40.0\text{V}}}$$