

Slide 1


Transmission Lines

Most communication systems contain components that utilize transmission line concepts. Whenever any circuit dimensions are reasonable fractions of a wavelength, transmission line effects must be considered. The concepts will be introduced in this module and the emphasis will be directed toward lines that are assumed to be lossless or nearly lossless. Various terms associated with transmission lines and their operating conditions will be explored.

Slide 2

Limitation of Lumped Circuit Theory

Basic circuit theory indicates that the current in the circuit below should be 2 A after the switch is closed and it will be when steady-state conditions are reached. However, a transient interval exists in which one or more waves will propagate between source and load before the final conditions are established.

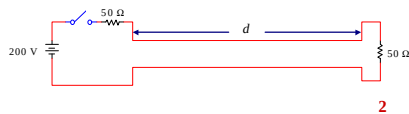

Slide 3

Propagation Time and Review of Wavelength and Frequency

The one-way delay time t_1 is

$$t_1 = \frac{\text{length of line}}{\text{velocity of propagation}} = \frac{d}{n}$$

The wavelength l is

$$l = \frac{\text{velocity of propagation}}{\text{frequency}} = \frac{n}{f}$$

In free-space $n = c = 3 \times 10^8$ m/s

$$l = \frac{c}{f} = \frac{3 \times 10^8}{f}$$

3

Slide 4

When are these effects important?

1. Pulse waveforms are used and propagation times are of the same order of magnitude as pulse widths.
2. Modulated waveforms are used and connection lengths are of the same order of magnitude as the wavelengths.

For 2, we will use the estimate of 0.1λ as the point where transmission line effects must be considered.

4

Slide 5

Example 1. A frequency of 1 MHz is near the middle of the AM band. Estimate the length at which transmission line effects must be considered.

$$l = \frac{3 \times 10^8}{f} = \frac{3 \times 10^8}{1 \times 10^6} = 300 \text{ m}$$

The length l for $0.1 l$ is

$$l = 0.1 l = 0.1 \times 300 = 30 \text{ m}$$

5

Slide 6

Example 2. A frequency of 100 MHz is near the middle of the FM band. Estimate the length at which transmission line effects must be considered.

$$l = \frac{3 \times 10^8}{f} = \frac{3 \times 10^8}{1 \times 10^8} = 3 \text{ m}$$

The length l for $0.1 l$ is

$$l = 0.1 l = 0.1 \times 3 = 0.3 \text{ m} = 30 \text{ cm}$$

6

Slide 7

Example 3. A frequency of 1 GHz is near where the *microwave region* begins. Estimate the length at which transmission line effects must be considered.

$$l = \frac{3 \times 10^8}{f} = \frac{3 \times 10^8}{1 \times 10^9} = 0.3 \text{ m} = 30 \text{ cm}$$

The length l for $0.1l$ is

$$l = 0.1l = 0.1 \times 30 = 3 \text{ cm}$$


7

Slide 8

Incremental Model of Lossless Transmission Line

Let L = inductance per unit length (H/m)

C = capacitance per unit length (F/m)

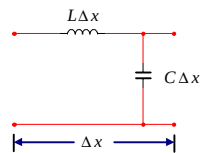

8

Slide 9

Characteristic Impedance Z_0

$$Z_0 = \frac{\text{voltage of a single wave}}{\text{current of a single wave}}$$

When line is lossless, the value is real.

For that case, we will set $Z_0 = R_0$

For a lossless line,

$$R_0 = \sqrt{\frac{L}{C}}$$

9

Slide 10

Example 4. A lossless line has $L = 320 \text{ nH/m}$ and $C = 90 \text{ pF/m}$. Determine R_0 .

$$R_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{320 \times 10^{-9}}{90 \times 10^{-12}}} \\ = 59.63 \, \Omega$$

10

Slide 11

Permittivity

Permittivity is a property of a dielectric material.

ϵ = permittivity of material in farads/meter (F/m)

ϵ_0 = permittivity of free space = $(1/36\pi) \times 10^{-9} \text{ F/m}$

ϵ_r = dielectric constant or relative permittivity

$$\epsilon = \epsilon_r \epsilon_0$$

$$\text{or } \epsilon_r = \frac{\epsilon}{\epsilon_0}$$

11

Slide 12

Permeability

Permeability is a magnetic property of a material.

μ = permeability of material in henries/m (H/m)

μ_0 = permeability of free space = $4\pi \times 10^{-7} \text{ H/m}$

μ_r = relative permeability

$$\mu = \mu_r \mu_0$$

Except for ferromagnetic materials, $\mu_r = 1$.

Unless otherwise stated,

we will assume $\mu = \mu_0$

12

Slide 13

Velocity of Propagation

For a transmission line,

$$n = \frac{1}{\sqrt{LC}}$$

For a plane wave,

$$n = \frac{1}{\sqrt{\mu\epsilon}} = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{\epsilon_r}}$$

13

Slide 14

Example 5. For line of Example 4 with $L = 320 \text{ nH/m}$ and $C = 90 \text{ pF/m}$, determine velocity of propagation.

$$\begin{aligned} n &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{320 \times 10^{-9} \times 90 \times 10^{-12}}} \\ &= 1.863 \times 10^8 \text{ m/s} \end{aligned}$$

14


Slide 15

Example 6. For line of Examples 4 and 5 with velocity of $1.863 \times 10^8 \text{ m/s}$, determine the dielectric constant.

$$\begin{aligned} n &= \frac{3 \times 10^8}{\sqrt{\epsilon_r}} \\ 1.863 \times 10^8 &= \frac{3 \times 10^8}{\sqrt{\epsilon_r}} \\ \epsilon_r &= 2.59 \end{aligned}$$

15

Slide 16

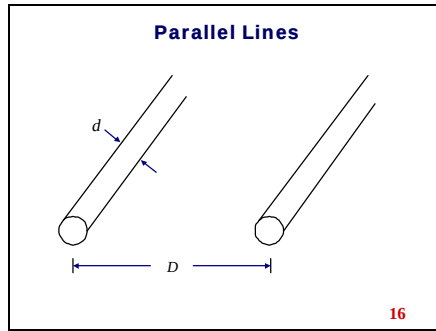

Slide 17

Formulas for Parallel Lines


$$L = \frac{m_0}{p} \ln \frac{2D}{d} = 4 \times 10^{-7} \ln \frac{2D}{d} \quad \text{H/m}$$

$$C = \frac{pe}{\ln \frac{2D}{d}} = \frac{(1/36) \times 10^{-9} e_r}{\ln \frac{2D}{d}} = \frac{27.78 \times 10^{-12} e_r}{\ln \frac{2D}{d}} \quad \text{F/m}$$

$$R_0 = \frac{120}{\sqrt{e_r}} \ln \frac{2D}{d} \quad \Omega$$

17

Slide 18

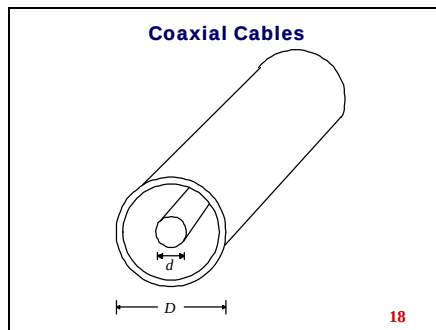

Slide 19

Formulas for Coaxial Cables

$$L = \frac{\mu_0}{2\pi} \ln \frac{D}{d} = 2 \times 10^{-7} \ln \frac{D}{d} \quad \text{H/m}$$

$$C = \frac{2\pi\epsilon}{\ln \frac{D}{d}} = \frac{(1/18) \times 10^{-9} \epsilon_r}{\ln \frac{D}{d}} = \frac{55.56 \times 10^{-12} \epsilon_r}{\ln \frac{D}{d}} \quad \text{F/m}$$

$$R_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \frac{D}{d} \quad \Omega$$

19

Slide 20

Example 6. A coaxial cable has $d = 0.29$ cm, $D = 1.05$ cm and a dielectric constant of 2.25. Find (a) L , (b) C , (c) R_0 and (d) v .

The quantity $\ln \frac{D}{d}$ is required in 3 formulas.

$$\ln \frac{D}{d} = \ln \frac{1.05}{0.29} = 1.287$$

(a) $L = 2 \times 10^{-7} \ln \frac{D}{d} = (2 \times 10^{-7})(1.287)$
 $= 257.4 \text{ nH/m}$

20

Slide 21

Example 6. (Continuation)

(b) $C = \frac{55.56 \times 10^{-12} \epsilon_r}{\ln \frac{D}{d}} = \frac{55.56 \times 10^{-12} \times 2.25}{1.287}$
 $= 97.13 \text{ pF/m}$

(c) $R_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \frac{D}{d} = \frac{60}{\sqrt{2.25}} (1.287) = 51.48 \Omega$

(d) $n = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.25}} = \frac{3 \times 10^8}{1.5} = 2 \times 10^8 \text{ m/s}$

21

Slide 22

Matched Load Impedance



At any point on line, $\overline{Z}_{in} = R_L = R_0$


$$I_{rms} = \frac{V_{rms}}{|\overline{Z}_s + R_0|} = \frac{V_{rms}}{|\overline{Z}_s + R_L|}$$

$$P_{in} = P_L = I_{rms}^2 R_0 = I_{rms}^2 R_L$$

22

Slide 23

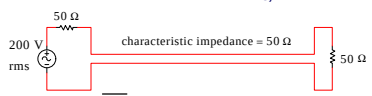Example 7. Determine $\overline{Z}_{in}$, I_{rms} , P_{in} and P_L



$$\overline{Z}_{in} = R_{in} = 50 \Omega$$

$$I_{rms} = \frac{400 \text{ V}}{50 \Omega + 50 \Omega} = 4 \text{ A}$$

$$P_{in} = I_{rms}^2 R = (4)^2 \times 50 = 800 \text{ W}$$

$$P_L = P_{in} = 800 \text{ W}$$

23

Slide 24

Example 8. Assume system of Example 7 except that line has loss of 0.01 dB/m. Find load power for line length of 50 m.

Strictly speaking, line now has complex $\overline{Z}_0$, but approach is reasonable for low losses.

$$L_{dB} = 50 \text{ m} \times 0.01 \text{ dB/m} = 0.5 \text{ dB}$$

$$L = 10^{0.5/10} = 1.122$$


$$P_L = \frac{P_{in}}{L} = \frac{800}{1.122} = 713.0 \text{ W}$$

Line dissipates $800 - 713 = 87 \text{ W}$

24

Slide 25

Mismatched Load Impedance

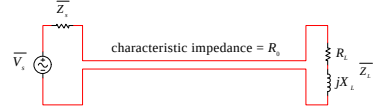

Reflection Coefficient at Load

$$\overline{\Gamma}_L = \frac{Z_L - R_0}{Z_L + R_0} \quad 0 \leq \Gamma_L \leq 1$$

For matched load, $\overline{\Gamma}_L = 0$

25

Slide 26

Voltage Standing Wave Ratio

$$\text{VSWR} = S = \frac{V_{\max}}{V_{\min}} \quad 1 \leq S \leq \infty$$

$$S = \frac{1 + \Gamma_L}{1 - \Gamma_L} \quad \Gamma_L = \frac{S - 1}{S + 1}$$

The angle of $\overline{\Gamma}_L$ cannot be determined from S .

For resistive load, $S = \frac{R_L}{R_0}$ or $\frac{R_0}{R_L}$
depending on which value is ≥ 1 .

26

Slide 27

Power Relationships at Mismatch

Let P_{inc} = power incident to load
 P_{ref} = power reflected by load
 P_L = power absorbed by load

$$P_{inc} = P_{ref} + P_L \quad P_{ref} = \Gamma_L^2 P_{inc}$$

$$P_L = (1 - \Gamma_L^2) P_{inc}$$

decibel mismatch loss = $-10 \log(1 - \Gamma_L^2)$
decibel return loss = $-10 \log \Gamma_L^2$

27

Slide 28

Input Impedance

$$\overline{Z_{in}} = R_0 \frac{(1 + \overline{\Gamma_L} e^{-j4\pi d / l})}{(1 - \overline{\Gamma_L} e^{-j4\pi d / l})}$$

The input impedance of a lossless line with a mismatch can be determined by the equation above. This means that the power reaching the load is a function of the line length. The pattern repeats at intervals of $\lambda/2$.

28

Slide 29

Example 9. A 50- Ω lossless line is terminated with an impedance of 50 + j100 Ω . Determine the reflection coefficient and the standing-wave ratio.

$$\begin{aligned} \overline{\Gamma_L} &= \frac{Z_L - R_0}{Z_L + R_0} = \frac{50 + j100 - 50}{50 + j100 + 50} \\ &= \frac{j100}{100 + j100} = \frac{100 \angle 90^\circ}{141.4 \angle 45^\circ} = 0.7071 \angle 45^\circ \end{aligned}$$

$$S = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + 0.7071}{1 - 0.7071} = 5.828$$

29

Slide 30

Example 10. A 300- Ω lossless line is terminated with a resistance of 300 Ω . Determine the reflection coefficient and the standing-wave ratio.

$$\overline{\Gamma_L} = \frac{R_L - R_0}{R_L + R_0} = \frac{100 - 300}{100 + 300} = -0.5$$

$$S = \frac{R_0}{R_L} = \frac{300}{100} = 3$$

30

Slide 31

Example 11. For the system of the preceding example, determine the decibel mismatch loss.

decibel mismatch loss

$$= -10 \log(1 - \Gamma_L^2)$$

$$= -10 \log[1 - (0.5)^2]$$

$$= -10 \log 0.75$$

$$= -10(-0.125) = 1.25 \text{ dB}$$

31

Slide 32

Summary

- Transmission line effects must be considered when a connection is an appreciable fraction of a wavelength.
- Important properties of a transmission line are the *characteristic impedance* and the *velocity of propagation*.
- Important properties of a line with load are the *reflection coefficient* at the load and the *voltage standing wave ratio*.
- The ideal condition at the load is for the load impedance to be real and equal to the characteristic impedance of the line.

32