


FE REVIEW

LOGIC

1

The 'AND' gate

2

 


The '**AND**' gates output will achieve its active state, "**ACTIVE HIGH**", when **BOTH of its inputs** achieve their active state, "**ACTIVE HIGH**".

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

$$\begin{aligned} f(A, B) &= AB \\ &= \sum m(3) \end{aligned}$$

The 'OR' gate

3

 

$$f(A, B) = A + B$$


The 'OR' gates output will achieve its active state, "ACTIVE HIGH", when ONE OR MORE of its inputs achieve their active state, "ACTIVE HIGH".

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

$$\begin{aligned} f(A, B) &= A + B \\ &= \sum m(1, 2, 3) \end{aligned}$$

The 'NOT' gate (Inverter)

4

 


The '**NOT**' gates output will achieve its active state, "**ACTIVE LOW**", when **ITS SINGLE input** achieves its active state, "**ACTIVE HIGH**".

A	$f(A)$
0	1
1	0

$$\begin{aligned} f(A) &= \bar{A} \\ &= \sum m(0) \end{aligned}$$

The 'NAND' gate

5

 


The '**NAND**' gates output will achieve its active state, "**ACTIVE LOW**", when **BOTH of its inputs** achieve their active state, "**ACTIVE HIGH**".

<i>A</i>	<i>B</i>	<i>AB</i>	\overline{AB}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

$$\begin{aligned} f(A, B) &= \overline{AB} \\ &= \sum m(0, 1, 2) \end{aligned}$$

The 'NOR' gate

6

 


The '**NOR**' gates output will achieve its active state, "**ACTIVE LOW**", when **ONE OR MORE** of its inputs achieve their active state, "**ACTIVE HIGH**".

<i>A</i>	<i>B</i>	<i>A + B</i>	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

$$\begin{aligned} f(A, B) &= \overline{A + B} \\ &= \sum m(0) \end{aligned}$$

The 'XOR' gate

7

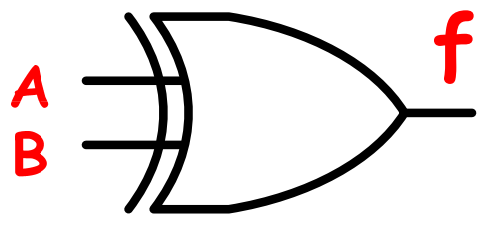

$f(A, B) = A \oplus B$
 $= \overline{A}B + A\overline{B}$

The 'XOR' gates output will achieve its active state, "ACTIVE HIGH", when AN ODD # of its inputs achieve their active state, "ACTIVE HIGH".

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$$f(A, B) = A \oplus B$$
$$= \sum m(1, 2)$$

A Few Boolean Rules

8

$$a + 0 = a$$

$$a + a = a$$

=

$$a = a$$

$$a + \bar{a}b = a + b$$

$$ab + a\bar{b}c = ab + ac$$

$$a + \bar{a} = 1$$

$$a + 1 = 1$$


$$a + ab = a$$

$$ab + a\bar{b} = a$$

$$\overline{a + b} = \bar{a} \cdot \bar{b}$$

Combinational Logic Example

9

 

$$(\bar{A} + B)(\overline{AC})$$

$$(\bar{A} + B)(\bar{A} + \bar{C})$$

$$\bar{A}(\bar{A} + \bar{C}) + B(\bar{A} + \bar{C})$$

$$(\overline{AA} + \overline{AC}) + (\overline{AB} + \overline{BC})$$

$$\bar{A} + \bar{A}\bar{C} + \bar{A}B + B\bar{C}$$

$$\underbrace{\bar{A}}_a + \underbrace{\bar{A}\bar{C}}_{a \quad b} + \bar{A}B + B\bar{C}$$


$$a + ab = a$$

$$\bar{A} + \bar{A}B + B\bar{C}$$

$$\bar{A} + B\bar{C}$$

Another Boolean Example


10

 

$$\begin{aligned}
 & (A + C) + \underbrace{\underbrace{\overline{A}}_a + \underbrace{AB}_{\overline{a}b}}_{\overline{A}+B} \\
 & \overline{(A + C) + (\overline{A} + B)} \\
 & \overline{(A + C)} \overline{(\overline{A} + B)} \\
 & \left(\overline{A} \overline{C} \right) \left(\overline{\overline{A} B} \right) \\
 & \left(\overline{A} \overline{C} \right) \left(A \overline{B} \right) \\
 & \left(\underbrace{A \overline{A}}_0 \overline{B} \overline{C} \right) \\
 & 0
 \end{aligned}$$

State Table Example

11

 


A	B	C	$f(A, B, C)$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Flip-Flops

12

FF's and some Definitions

 


Synchronous Input: Controls the device based on the timing from a clock signal. When the clocking signal occurs, the synchronous input is allowed to affect the output. If the signal does not occur the synchronous input can not affect anything.

Asynchronous Input

14

 Affects the output without waiting for a clocking signal. It IGNORES the clock.




ACTIVE HIGH OR LOW

15

ACTIVE HIGH or LOW?

 The activity level of an input or output is determined by the existence of an inverting bubble on the terminal or not. Both the **PRE** and the **CLR** inputs below are **ACTIVE LOW** inputs. This means that a '0' is required on the input in order for the input to affect the output.



PRE and CLR

16

'PRE' Input

The 'PRE' input will cause the Q output to SET (go HIGH) when a '0' is applied to the PRE input. This occurs ASYNCHRONOUSLY (without the clock).

'CLR' Input


The 'CLR' input will cause the Q output to RESET (go LOW) when a '0' is applied to the 'CLR' input. This occurs ASYNCHRONOUSLY (without the clock).

The CLOCK

17


There are three types of clock inputs:

 - **Level Triggered** (not used often)
- **Leading Edge Triggered**
- **Trailing Edge Triggered** (pictured below)




Level Triggering

18

 

 
The problem with this type of triggering is that the input could change millions of times during each 'Level' period, thus affecting the output millions of times.



The clock will allow input signals to affect the output during these time periods.

Leading Edge Triggering



19

 

The “Leading” edge of each pulse will allow “one and only one” input event for each edge to affect the output.

Trailing Edge Triggering



20

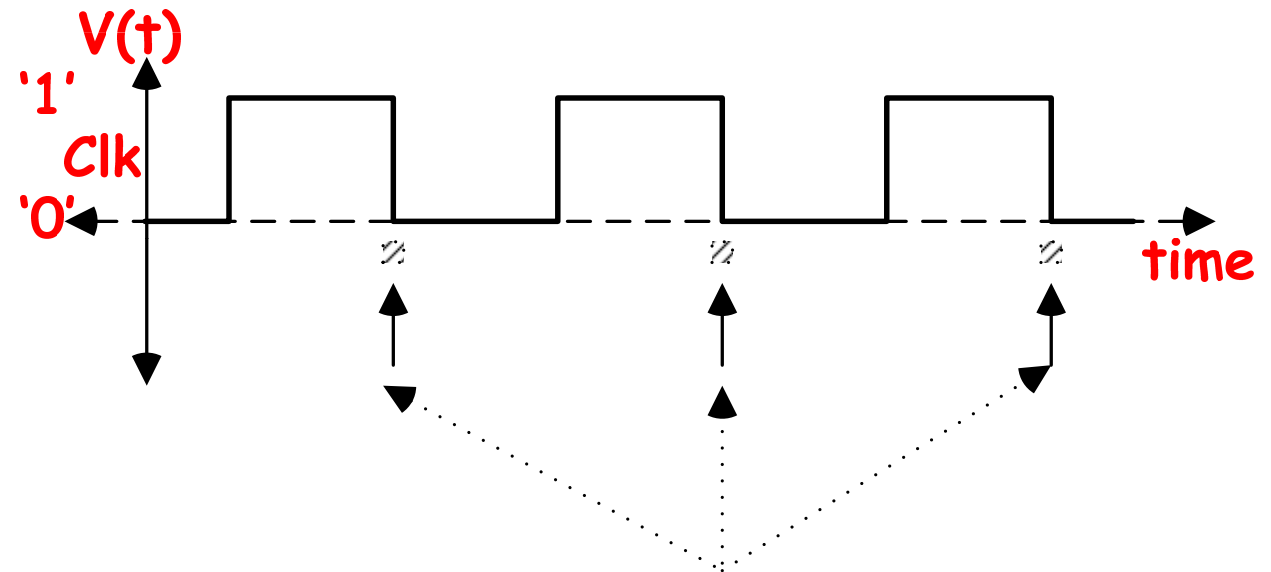 

The “Trailing” edge of each pulse will allow “one and only one” input event for each edge to affect the output.

How the edge trigger is accomplished

21

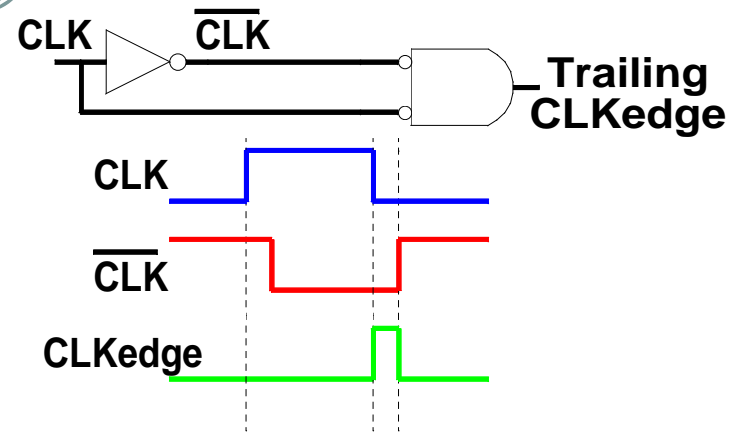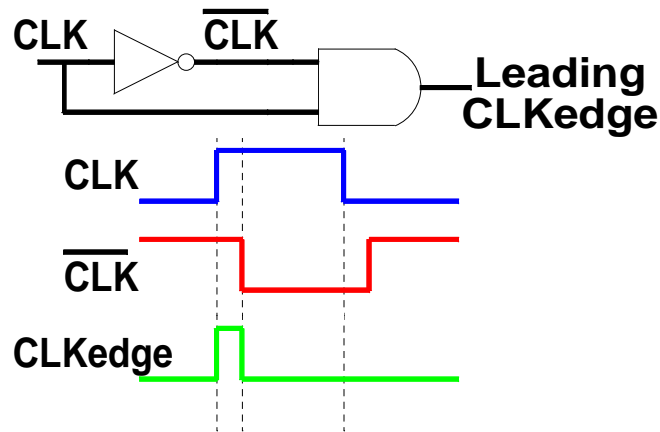


These circuits work by using the fact that there is no such thing as an "ideal" gate. Instead, there exists a delay from the input and the output. The Gate on the far right is a "negative logic" representation of a NOR gate.

The 'D' Flip-flop

22

The 'D' Flip-flop output will take on the value of the 'D' input. So, if there is a logic '1' on the 'D' input when the trigger event occurs, the '1' will be transferred to the output until the next trigger event. At that point, if 'D' changes to a logic '0', so will the Q output.

D	Q_p	Q_N
0	0	0
0	1	0
1	0	1
1	1	1

 

Present State and Next State

23

- $Q_P = Q$ present = Present state:
The state of the output before the clock signal.
- $Q_N = Q$ next = Next state:
The state the output will attain based on the flip-flop synchronous inputs after the clock signal occurs. It is what will happen in the FUTURE!

D FF wrap up

24

D	Q_p	Q_N	
0	0	0	} Reset
0	1	0	
1	0	1	} Set
1	1	1	

We note that whenever the **D input** is a '0', the output will be '**Reset**', while whenever the **D input** is a '1', the output will be '**Set**'.


The D FF is performs two basic named functions:

Data: The **D-ff** is one of the most basic memory cells. Data placed on the input "**D**" is transferred to the output "**Q**" and "stored" there until it is replaced during the next clock active period.

Delay: Data placed on the input "**D**" is delayed in its transition to the output "**Q**" until the clocks active period occurs.

The 'T' Flip-flop

25

 


T	Q_p	Q_N	
0	0	0	} Hold
0	1	1	
1	0	1	} Toggle
1	1	0	

For a 'T' FF, whenever the T input is '0', the output will be in a 'Hold' condition in which whatever Q_p is will be held there.

Whenever the T input is '1', the output will be in a "Toggle" condition where if Q_p is '0' the output will toggle to a '1' and **vice versa**.

The 'JK' Flip-flop

26

 

Row	J	K	Q_p	Q_N	
0	0	0	0	0	} Hold
1	0	0	1	1	
2	0	1	0	0	} Reset
3	0	1	1	0	
4	1	0	0	1	} Set
5	1	0	1	1	
6	1	1	0	1	} Toggle
7	1	1	1	0	

The JK used as a T-FF


27

Before simplifying the JK truth table we can note that the table looks like it is made up of both the T and the D flip-flops.

The JK used as a T-FF

28

 - We can convert the **JK** into a **T-FF** by simply shorting the two inputs together and using the resulting input as a T input.




Row	J	K	Q_p	Q_N	
0	0	0	0	0	} Hold
1	0	0	1	1	
2					
3					
4					
5					
6	1	1	0	1	} Toggle
7	1	1	1	0	

The JK used as a D-FF

29

 All that is necessary to convert a JK into a D-FF is to place an inverter between the J and the K inputs so that they will always be opposite values.



Row	J	K	Q_p	Q_N
0				
1				
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6				
7				

} Reset

} Set

Simplifying the JK truth table

30

We can simplify the JK table and make it more useful at the same time by introducing the concept of the "Don't Care".

- An input is in a "Don't Care" state when it really doesn't matter what value is placed on the input. There will be no change on the output due to any value on the input.

The State Transition Table

31

- We start out by switching the order of the columns so that the state transitions are first. The table now becomes a "Transition Table".

Q_P	\Rightarrow	Q_N	J	K
0	\Rightarrow	0		
0	\Rightarrow	1		
1	\Rightarrow	0		
1	\Rightarrow	1		

The '0' to '0' transition

32

Next we look for the two rows that have transitions from state '0' to state '0'. It doesn't matter what K is because the transition remains the same. So we place a '0' in the J column and an X for "don't care" in the K column.

Row	J	K	Q_p	Q_n
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Q_p	\Rightarrow	Q_n	J	K
0	\Rightarrow	0	0	X
0	\Rightarrow	1		
1	\Rightarrow	0		
1	\Rightarrow	1		

The '0' to '1' transition

33

Next we look for the two rows that have transitions from state '0' to state '1'. Note that it doesn't matter what value **K** assumes because the transition remains the same. So we place a '1' in the **J** column and an **X** for "don't care" in the **K** column.

Row	J	K	Q_p	Q_N
0				
1	0	0	1	1
2				
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$Q_p \Rightarrow Q_N$	J	K
0 \Rightarrow 0	0	X
0 \Rightarrow 1	1	X
1 \Rightarrow 0		
1 \Rightarrow 1		

The '1' to '0' transition

34

Next we look for the two rows that have transitions from state '1' to state '0'. Note that it doesn't matter what value **J** assumes because the transition remains the same. So we place a '1' in the **K** column and an **X** for "don't care" in the **J** column.

Row	J	K	Q_p	Q_N
0				
1	0	0	1	1
2				
3	0	1	1	0
4				
5	1	0	1	1
6				
7	1	1	1	0

Q_p	\Rightarrow	Q_N	J	K
0	\Rightarrow	0	0	X
0	\Rightarrow	1	1	X
1	\Rightarrow	0	X	1
1	\Rightarrow	1		

The '1' to '1' transition

35

Next we look for the two rows that have transitions from state '1' to state '1'. Note that it doesn't matter what value J assumes because the transition remains the same. So we place a '0' in the K column and an X for "don't care" in the J column.

Row	J	K	Q_p	Q_N
0				
1	0	0	1	1
2				
3				
4				
5	1	0	1	1
6				
7				

Q_p	\Rightarrow	Q_N	J	K
0	\Rightarrow	0	0	X
0	\Rightarrow	1	1	X
1	\Rightarrow	0	X	1
1	\Rightarrow	1	X	0

Timing Diagrams

36

- The figure below is a "Timing" diagram for a JK-FF. Note that the 'Pre' and 'Clr' inputs as well as the leading edge trigger are demonstrated as well.

