

FE Review

1

ELECTRONICS # 1 FUNDAMENTALS

Electric Charge

2

In an electric circuit there is a conservation of charge. The net electric charge is constant. There are positive and negative charges. Like charges repel while unlike charges attract. The SI unit for electric charge (q) is the **Coulomb (C)**

Electric Energy

3

Energy is the ability to perform work and has the same units as work: **Work = force x dist.**
The SI unit for **energy (w)** is the **Joule (J)**.

Basic Variables

4

Quantity	Symbol	Unit
Mass	m, M	kg
Length	l, L	meter, m
Time	t	sec, s
Energy	w, W	joule, J
charge	q, Q	coulomb, C

Lower case usually indicates a time variant unit.

Electric Current

5

Charge is moved through a circuit as current, which is simply a measure of the **charge transferred/sec**. The SI unit is the **Ampere** with the symbol **(A)**.


$$i = \frac{dq}{dt} = I = \frac{Q}{t} \quad \left(\frac{\text{Coulombs}}{s} \right)$$

Voltage

6

The work performed/unit charge while moving a charge from one point to another in a circuit is voltage. Voltage is analogous to pressure. The SI unit for voltage is the **volt (v)**
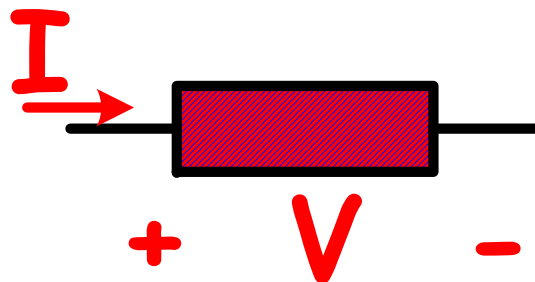
$$V = \frac{dw}{dq} \left(\frac{\text{joules}}{\text{coulomb}} \right) = \text{volts}$$



Power

7

Power (P), watt, w

$$P = \frac{dw}{dt} \left(\frac{\text{joules}}{\text{sec}} \right) \text{ or (watt)}$$

$$P = VI$$

Power is defined as the rate of energy transfer


Resistance

8

Resistance (R) unit is the **Ohm (Ω)**

A resistance is an element which dissipates energy and can not store energy
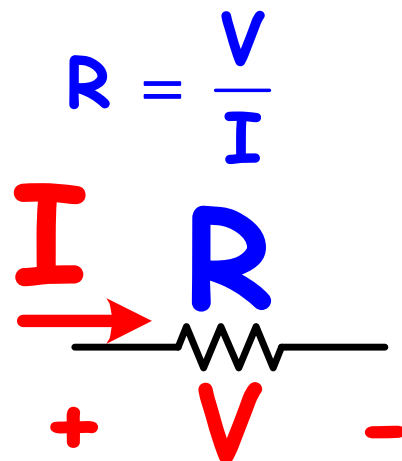
$$i = \frac{V}{R} \Leftarrow \text{Ohm's Law} \Rightarrow V = IR$$




Capacitance

9

A capacitor is an element which stores energy in an **electric field**. This energy is returned to the circuit later. The SI unit for **capacitance (C)** is the farad, **F**.

$$C = \frac{i}{dv/dt}$$

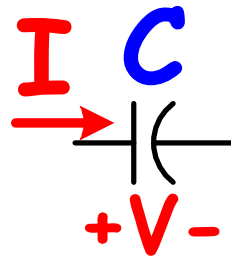

Alternate
Symbol




$$i = C \, dv/dt \quad \text{and} \quad v = \frac{1}{C} \int_0^+ i(t) dt + v(0)$$

Inductance

10

An **inductor (Coil)** is an element which stores energy in a **magnetic field**. The energy is then returned to the circuit later. The SI unit for **Inductance (L)** is the **Henry, H**.
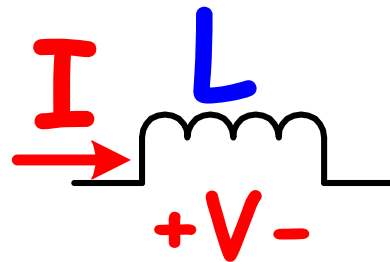
$$L = \frac{v}{\cancel{di}/dt} \quad \text{or} \quad v = L \frac{di}{dt} \quad \text{and} \quad i = \frac{1}{L} \int_0^+ v(t) dt + i(0)$$




Electrical variables

11

Quantity	Symbol	Unit
Current	$i(I)$	Ampere, A
Voltage	$v(V)$	Volt, V
Power	$p(P)$	Watt, W
Resistance	R	Ohm, Ω
Capacitance	C	Farad, F
Inductance	L	Henry, H

Some definitions

12

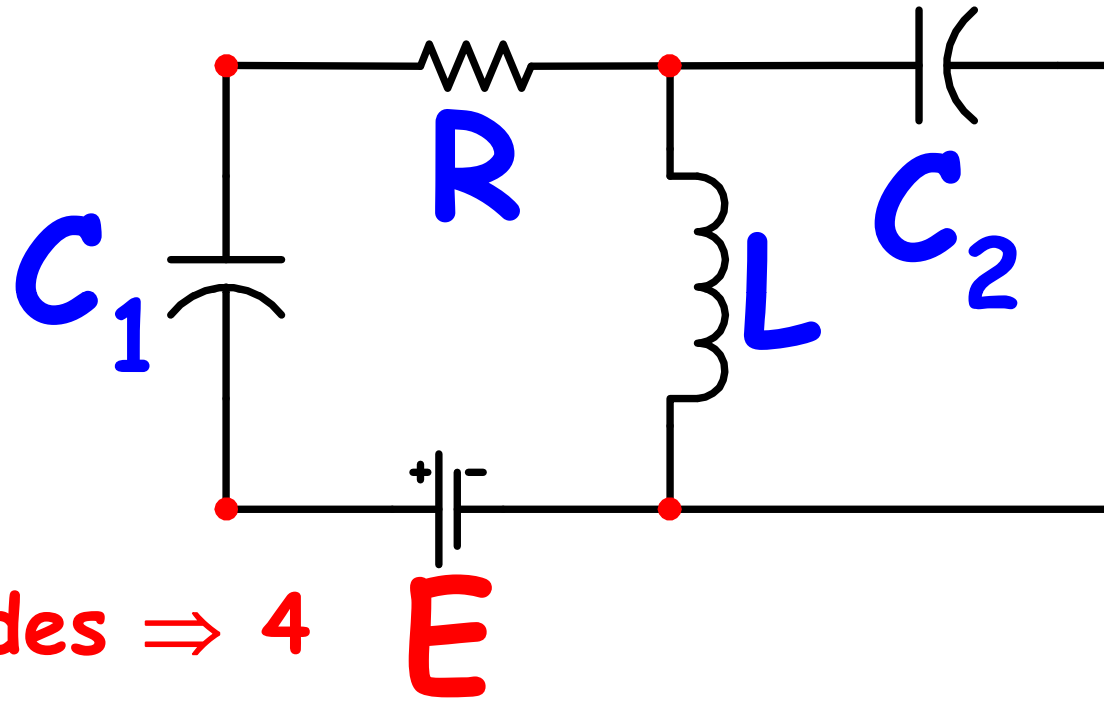

nodes $\Rightarrow 4$ E


loops $\Rightarrow 3$

meshs $\Rightarrow 2$ (also known as panes)

Kirchhoff's Voltage Law (KVL)

13
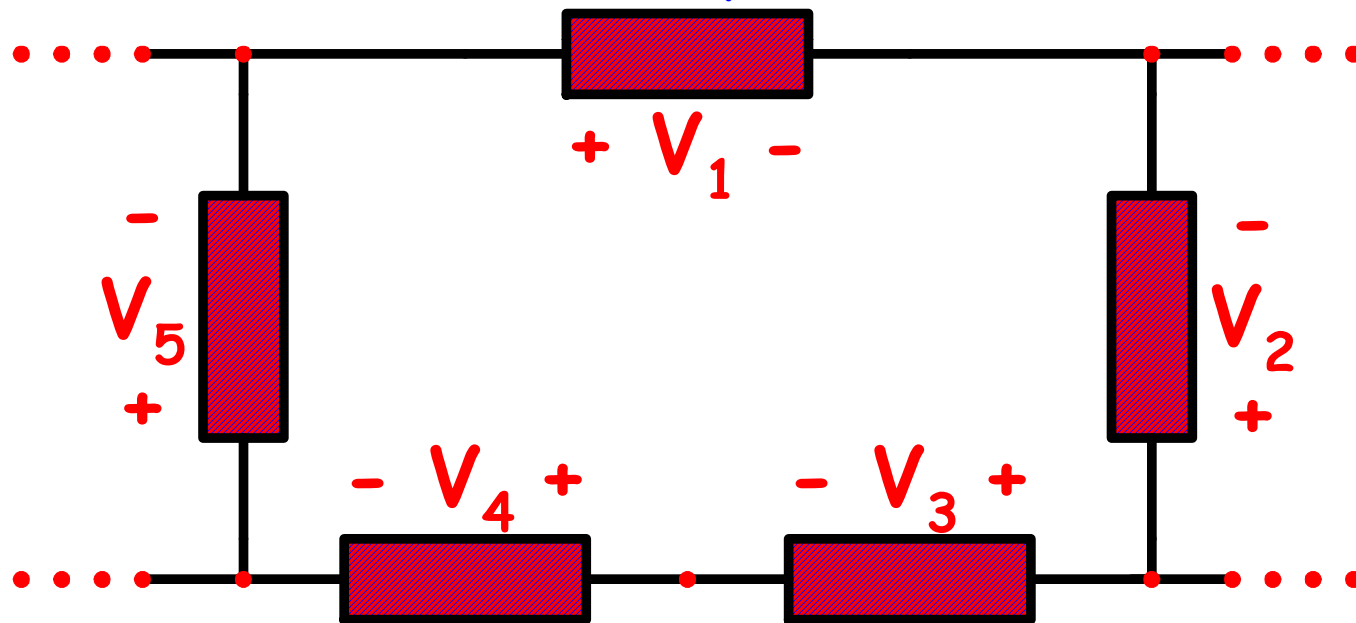
$$\text{KVL} \triangleq \sum_{\text{closed loop}} V = 0$$




$$V_1 - V_2 + V_3 + V_4 + V_5 = 0$$

Kirchhoff's Current Law(KCL)

14

$$KCL \triangleq \sum_{\text{node}} i = 0$$

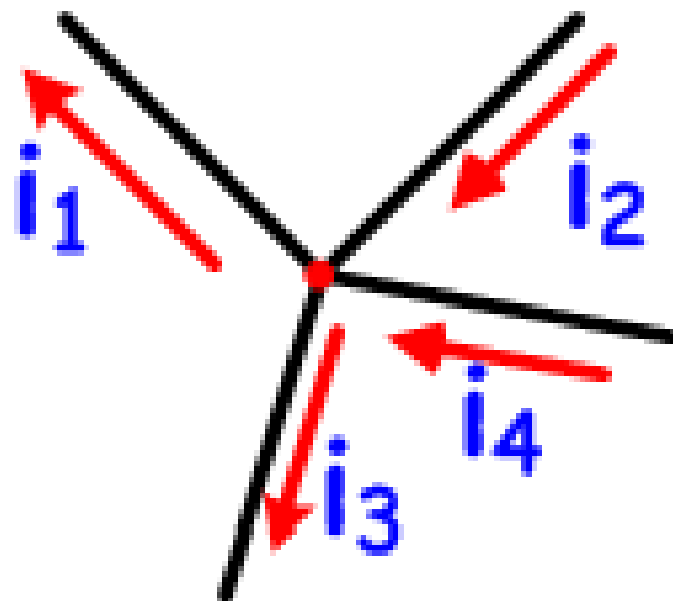currents entering a node
are defined as -
currents leaving a node
are defined as +




$$i_1 - i_2 + i_3 - i_4 = 0$$

Total Resistance of Series Elements

15

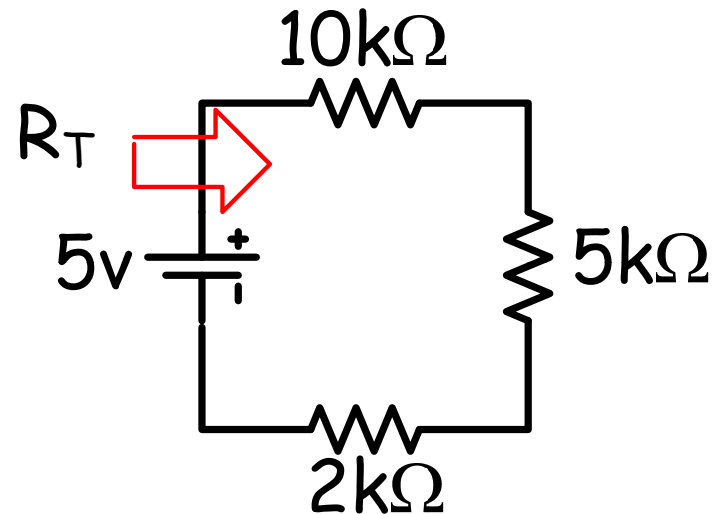When resistors are in series, the total resistance is simply the sum of the resistors.



$$R_T = 10k\Omega + 5k\Omega + 2k\Omega = 17k\Omega$$

KVL/KCL Example 1


16

Determine the unknown voltages, currents, and R in the circuit to the right.

Step 1:

Perform a **KVL** to find the voltage across the 2 parallel resistors, V_1 :

The 2 resistors share the same voltage.

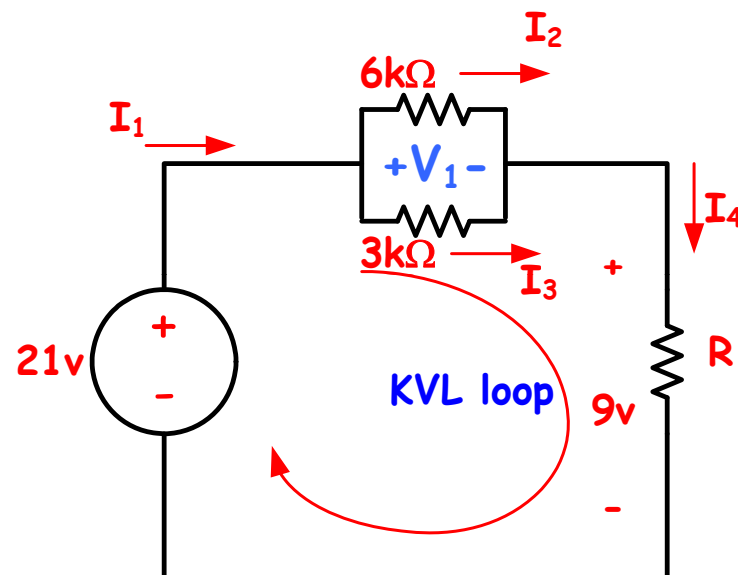

$$0 = -21\text{v} + V_1 + 9\text{v}$$


$$V_1 = 21\text{v} - 9\text{v} = \boxed{12\text{v}}$$

Example continued on the next slide.

KVL/KCL Example 1 (cont)

17

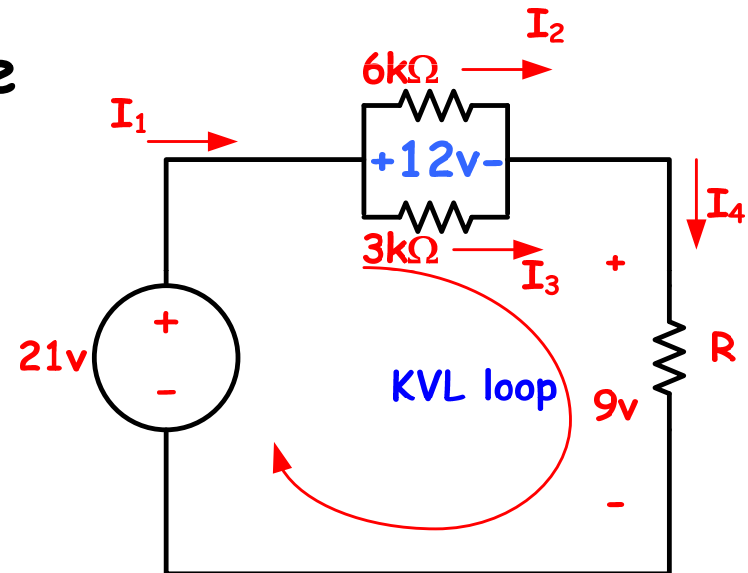Now that V_1 is known, the currents thru the 2 parallel resistors can be found via **Ohm's Law**.



$$I_2 = \frac{12\text{v}}{6\text{k}\Omega} = \boxed{2\text{mA}}$$

$$I_3 = \frac{12\text{v}}{3\text{k}\Omega} = \boxed{4\text{mA}}$$

Example continued on the next slide.

KVL/KCL Example 1 (cont)

18


Next, use **KCL** to determine the value of I_1 . Perform a **KCL** at the node to the left of the parallel combination:

$$0 = I_1 - 2\text{mA} - 4\text{mA}$$

$$I_1 = \boxed{6\text{mA}}$$

Finally, with the value of I_1 , use **Ohm's law** to determine the value of R :
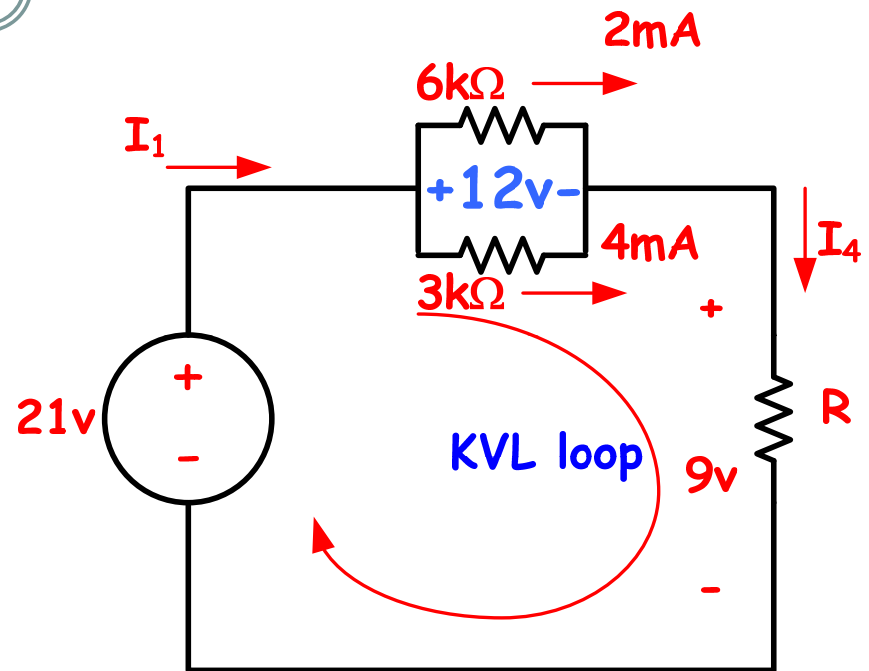
$$R = \frac{V_R}{I_1} = \frac{9\text{V}}{6\text{mA}} = \boxed{1.5\text{k}\Omega}$$




Voltage Divider example

19

$$\begin{aligned} V_1 &= \frac{30(5\text{k}\Omega)}{5\text{k}\Omega + 10\text{k}\Omega + 15\text{k}\Omega} \\ &= \frac{150}{30} = \boxed{5\text{v}} \end{aligned}$$

$$\begin{aligned} V_2 &= \frac{30(10\text{k}\Omega)}{30\text{k}\Omega} \\ &= \frac{300}{30} = \boxed{10\text{v}} \end{aligned}$$
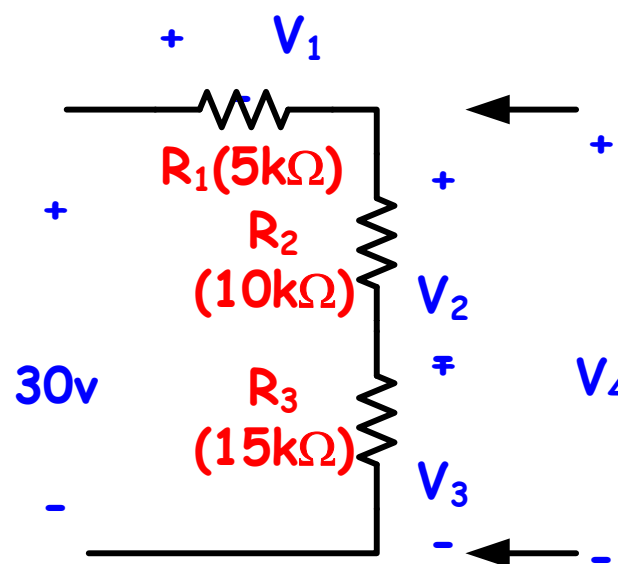
$$\begin{aligned} V_3 &= \frac{30(15\text{k}\Omega)}{30\text{k}\Omega} \\ &= \frac{450}{30} = \boxed{15\text{v}} \end{aligned}$$



$$\begin{aligned} V_4 &= \frac{30(10\text{k}\Omega + 15\text{k}\Omega)}{30\text{k}\Omega} \\ &= \frac{30(25)}{30} = \frac{750}{30} = \boxed{25\text{v}} \end{aligned}$$


Current Divider example

20

$$\begin{aligned} I_1 &= \frac{10A (6k\Omega \parallel 3k\Omega)}{2k\Omega + (6k\Omega \parallel 3k\Omega)} \\ &= \frac{10A (2k\Omega)}{2k\Omega + (2k\Omega)} \\ &= \frac{20A}{4} = \boxed{5A} \end{aligned}$$

$$R_T = \frac{1}{\frac{1}{6k} + \frac{1}{3k} + \frac{1}{2k}} = 1k\Omega$$
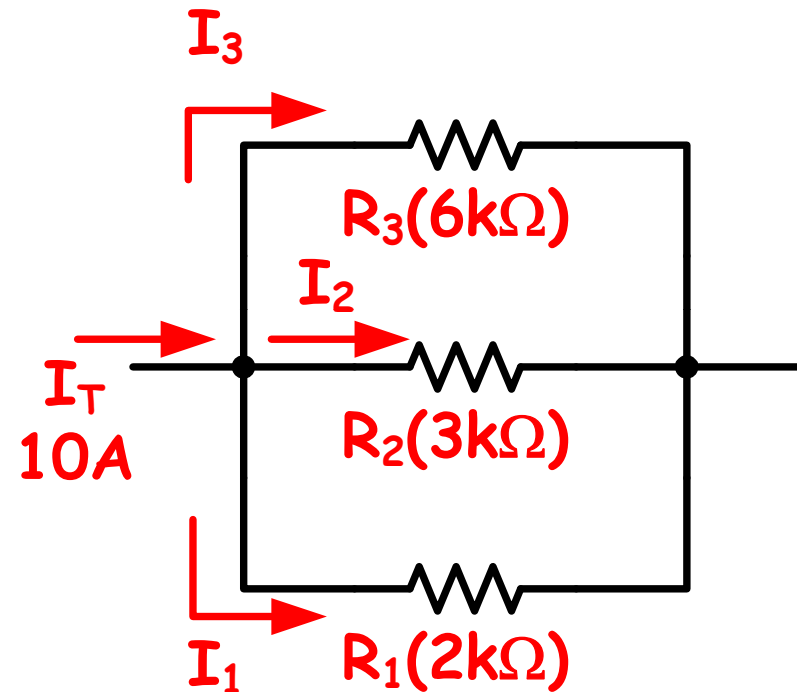
$$R_{1\parallel 2} = \frac{R_1(R_2)}{R_1 + R_2} = \frac{2k(3k)}{2k + 3k} = 1.2k\Omega$$



Example

21

Find all voltages and currents.
Verify with KVL.



1st, reduce the circuit.

$$R_{eq1} = R_3 + R_4$$

$$= 16\Omega + 5\Omega = \boxed{21\Omega}$$

$$R_{eq2} = R_2 \parallel R_{eq1}$$
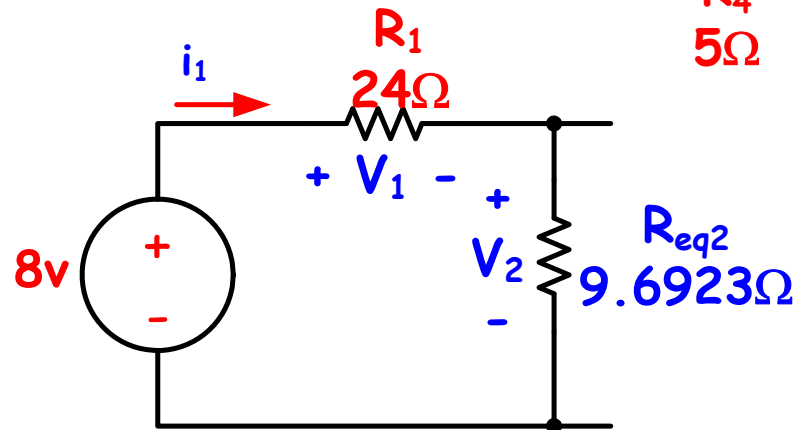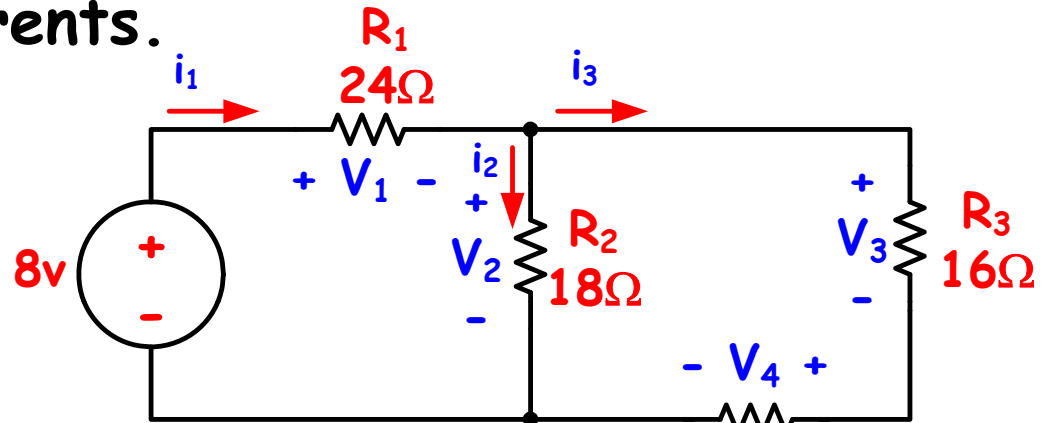
$$= \frac{18\Omega (21\Omega)}{18\Omega + 21\Omega} = \boxed{9.6923\Omega}$$



Example continued on the next slide.


Example (continued)

22

$$\begin{aligned} I_1 &= \frac{8\text{v}}{24\Omega + 9.6923\Omega} \\ &= 237.443\text{mA} \end{aligned}$$

$$\begin{aligned} V_1 &= I_1 R_1 \\ &= (237.443\text{mA}) 24\Omega \\ &= 5.6986\text{v} \end{aligned}$$

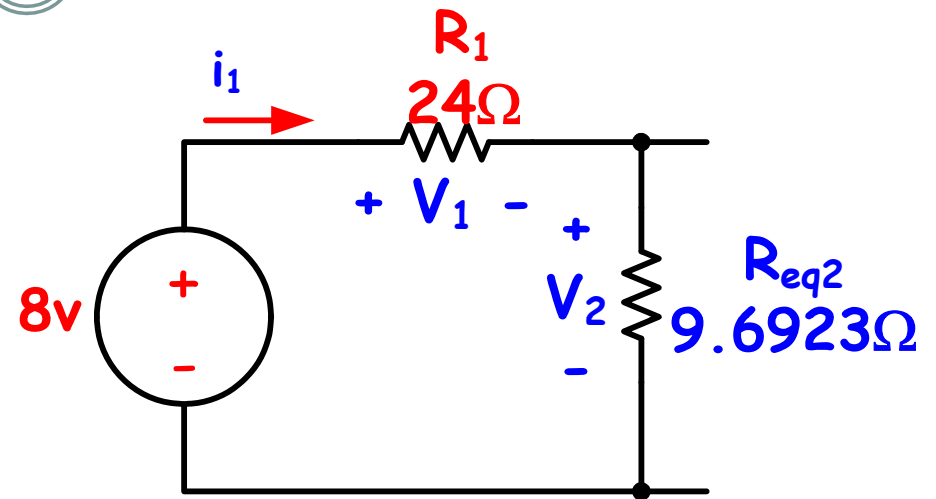
$$\begin{aligned} V_2 &= I_1 R_{eq2} \\ &= (237.443\text{mA}) 9.6923\Omega \\ &= 2.3014\text{v} \end{aligned}$$



Example continued on the next slide.

Example (continued)


23

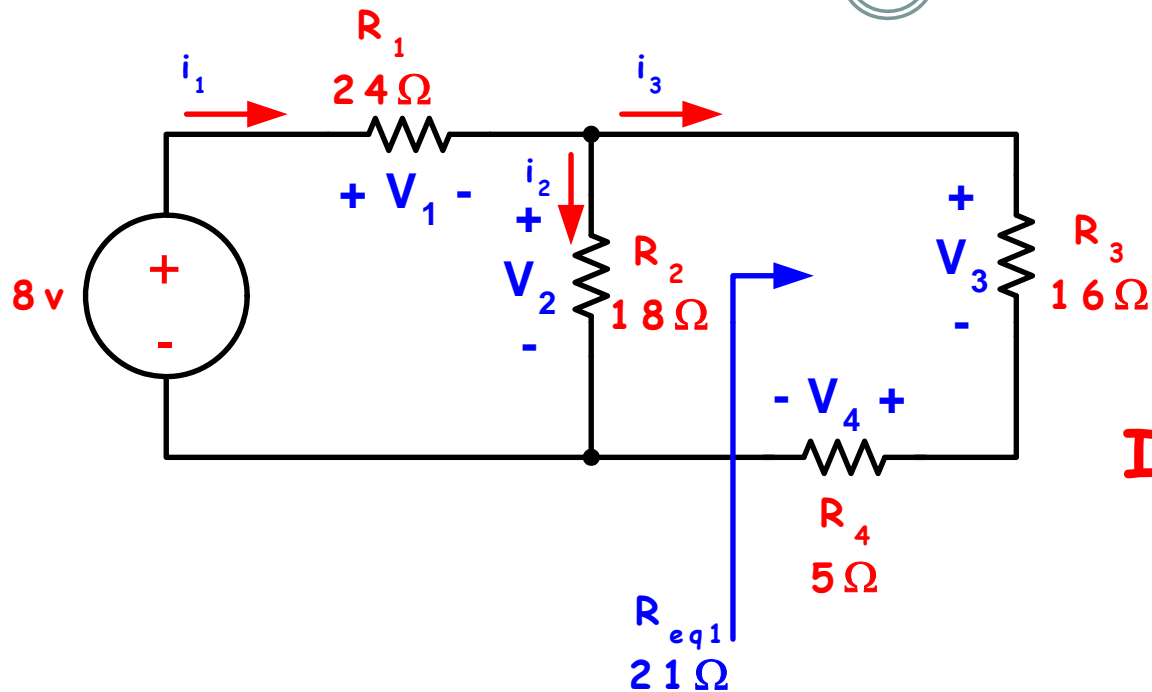

$$\begin{aligned} I_2 &= V_2 / R_2 \\ &= 2.3014\text{v} / 18\Omega \\ &= 127.8556\text{mA} \end{aligned}$$

Example continued on the next slide.

Example (continued)

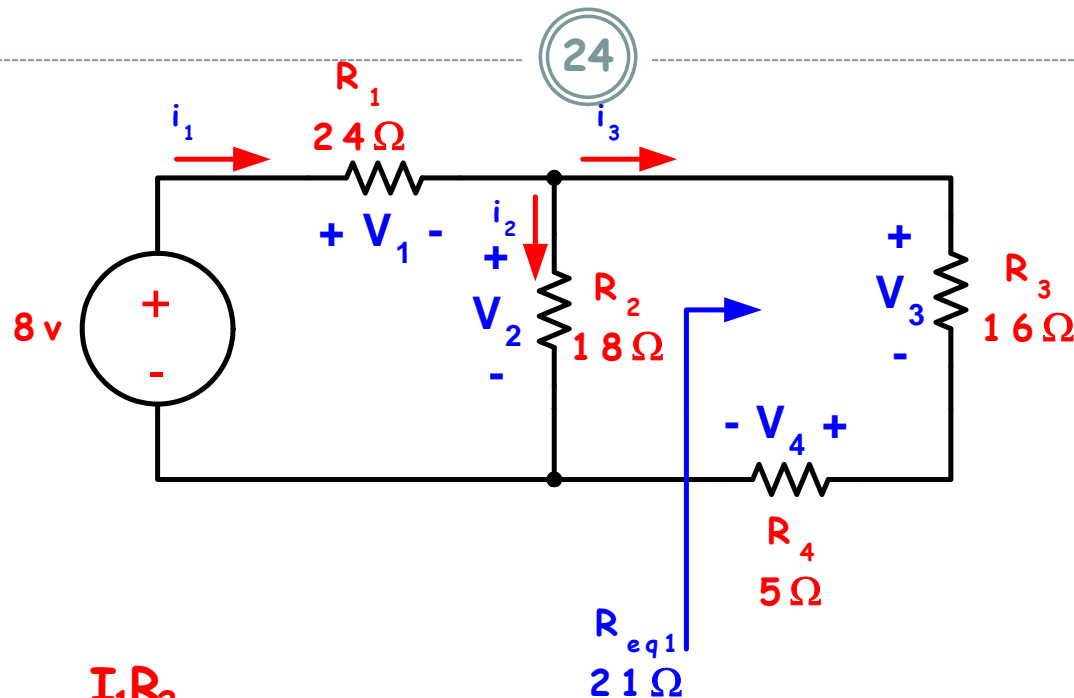

$$\begin{aligned}
 I_3 &= \frac{I_1 R_2}{R_2 + R_{eq1}} \\
 &= \frac{237.443\text{mA} (18\Omega)}{18\Omega + 21\Omega} \\
 &= \boxed{109.5891\text{mA}}
 \end{aligned}$$

or


$$\begin{aligned}
 0 &= -I_1 + I_2 + I_3 \\
 I_3 &= I_1 - I_2 \\
 &= 237.443\text{mA} - 127.8556\text{mA} \\
 &= \boxed{109.5874\text{mA}}
 \end{aligned}$$

Difference is due to round off.


Sources

25



Ideal
AC voltage
source

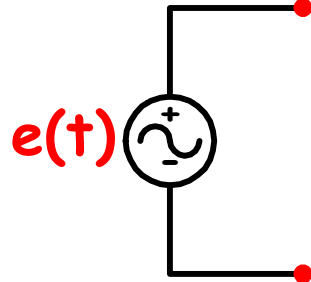


Ideal
DC voltage
source

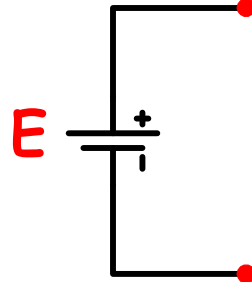


Non-ideal
DC voltage
source

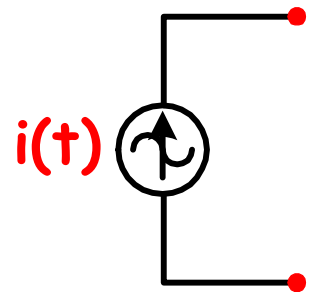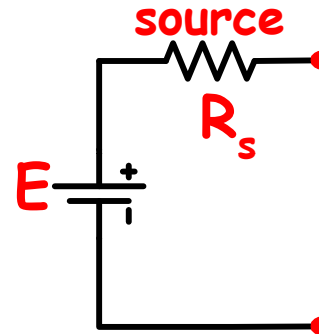

Ideal
AC current
source

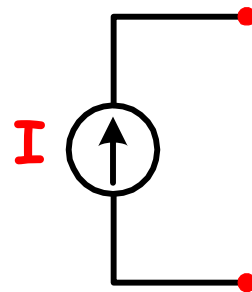

Ideal
DC current
source

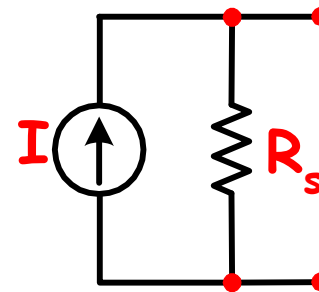

Non-ideal
DC current
source


Waveform shape

26

1.	$i(t) = I = -4$	dc current
2.	$v(t) = 2e^{-3t}$	AC voltage aperiodic associated with transients
3.	$v(t) = 25 \cos(\omega t + \theta)$	AC voltage periodic associated with steady state analysis

The Sine Wave

27

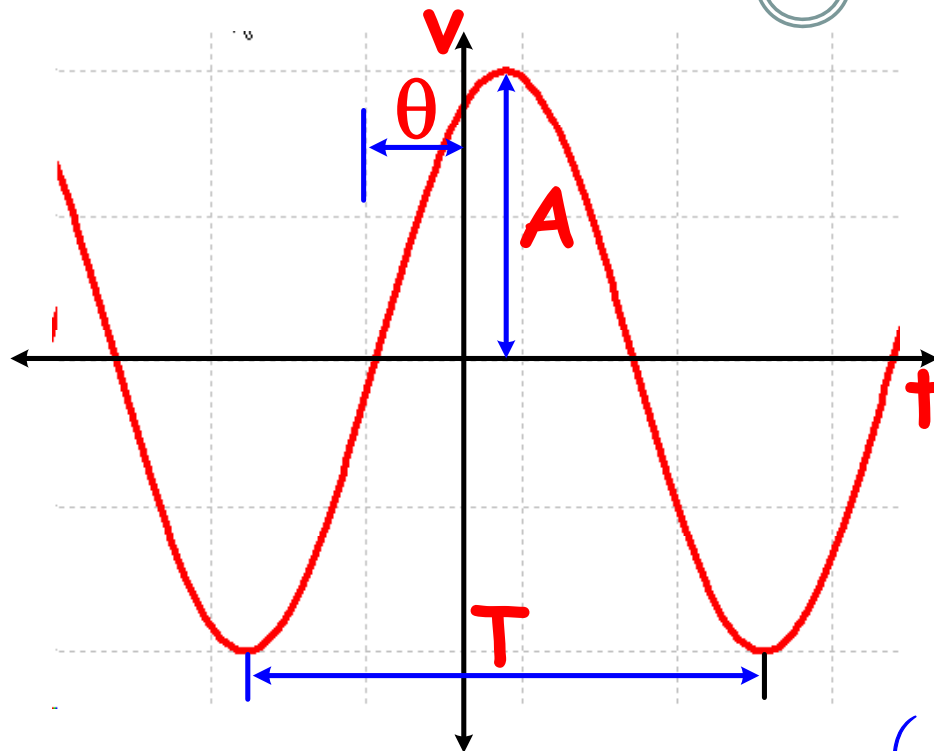

$$f = \frac{\omega}{2\pi} = \frac{1}{T} = \frac{\text{cycles}}{\text{sec}} = \text{hz}$$

$$f(t) = A \sin\left(\frac{2\pi}{T}t \pm \theta\right)$$

phase + if shifts left

phase - if shifts right

$$\sin(\omega t + \theta) = \cos\left(\omega t + \theta - \frac{\pi}{2}\right)$$

$$\cos(\omega t + \theta) = \sin\left(\omega t + \theta + \frac{\pi}{2}\right)$$

Average Value

28

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$

Effective value

29

$$P_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T P^2(t) dt}$$

Essentially, effective heating value
How much power will it use.

Instantaneous Power

30

$$P = VI$$