

FE Review


1

ELECTRONICS # 2 DC CIRCUIT ANALYSIS

8/25/2010

Source or Sink?

2

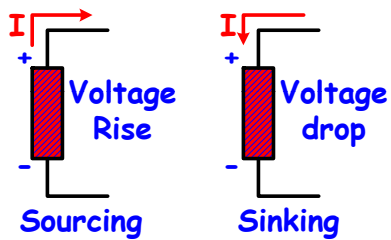

8/25/2010

Power

3

$$\text{Power} = P = VI$$

From Ohm's Law we have

$$V=IR \quad I=\frac{V}{R}$$

From these equations we get

$$\begin{aligned} P &= VI & P &= VI \\ &= (IR)I & P &= V\left(\frac{V}{R}\right) \\ P &= I^2R & P &= \frac{V^2}{R} \end{aligned}$$

8/25/2010

Capacitors and Inductors in DC circuits

4

Since V and I don't vary with time in a DC circuit, Capacitors and Inductors don't act the way they would in an AC circuit.

In DC circuits:


Capacitors act like OPEN-CIRCUITS

Inductors act like SHORT-CIRCUITS

8/25/2010

DC Circuit Analysis Mesh Example

5

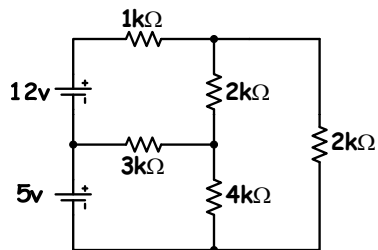


Example continued
on the next slide.

8/25/2010

Example (continued)

6

Add in three CLOCKWISE
loop currents

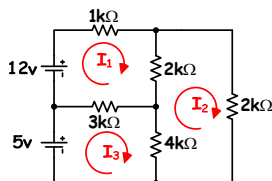


Step 1:
It is important that
the loop currents be
drawn in the **clock-
wise direction**

Example continued
on the next slide.

8/25/2010

Example (continued)

7

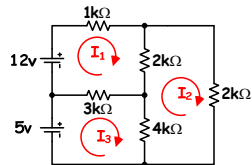

Call on good old KVL

Step 2:

We will use KVL to write a loop eqn. for each mesh current.

@ I_1

$$0 = -12\text{v} + 1\text{k}\Omega I_1 + 2\text{k}\Omega (I_1 - I_2) + 3\text{k}\Omega (I_1 - I_3)$$

$$12\text{v} = 1\text{k}\Omega I_1 + 2\text{k}\Omega I_1 - 2\text{k}\Omega I_2 + 3\text{k}\Omega I_1 - 3\text{k}\Omega I_3$$


$$12\text{v} = 6\text{k}\Omega I_1 - 2\text{k}\Omega I_2 - 3\text{k}\Omega I_3$$

Example continued on the next slide.

8/25/2010

Example (cont.) Call on good old KVL

8

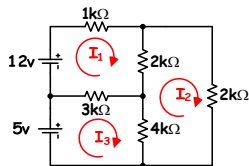

Note that the sign for the current we are working with is + while the signs of both of the others is negative. This is a good 'idiot' check.

@ I_1


$$12\text{v} = 6\text{k}\Omega I_1 - 2\text{k}\Omega I_2 - 3\text{k}\Omega I_3$$

Example continued on the next slide.

8/25/2010

Example (cont.) Call on good old KVL

9

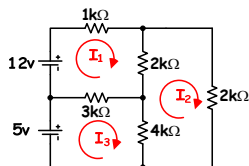

Also note that the sum of the resistors in the I_1 loop is 6k just as in the equation. This is another 'idiot' check.

@ I_1


$$12\text{v} = 6\text{k}\Omega I_1 - 2\text{k}\Omega I_2 - 3\text{k}\Omega I_3$$

Example continued on the next slide.

8/25/2010

Example (cont.) Call on good old KVL

10

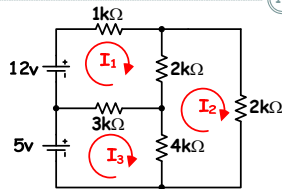

Perform the same idiot checks on the I2 loop equation below.

@ I_2

$$0 = 2k\Omega I_2 + 4k\Omega (I_2 - I_3) + 2k\Omega (I_2 - I_1)$$

$$0 = 2k\Omega I_2 + 4k\Omega I_2 - 4k\Omega I_3 + 2k\Omega I_2 - 2k\Omega I_1$$


$$0 = -2k\Omega I_1 + 8k\Omega I_2 - 4k\Omega I_3$$

Example continued on the next slide.

8/25/2010

Example (cont) Call on good old KVL

11

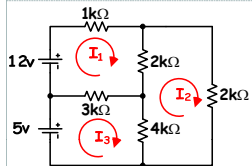

Perform the same idiot checks on the I3 loop equation below.

@ I_3

$$0 = -5v + 3k\Omega (I_3 - I_1) + 4k\Omega (I_3 - I_2)$$

$$5v = 3k\Omega I_3 - 3k\Omega I_1 + 4k\Omega I_3 - 4k\Omega I_2$$

$$5v = -3k\Omega I_1 - 4k\Omega I_2 + 7k\Omega I_3$$

Example continued on the next slide.

8/25/2010

Example (continued)

12

Three eqn's, three unknowns

1 : $12v = 6k\Omega I_1 - 2k\Omega I_2 - 3k\Omega I_3$

2 : $0 = -2k\Omega I_1 + 8k\Omega I_2 - 4k\Omega I_3$

3 : $5 = -3k\Omega I_1 - 4k\Omega I_2 + 7k\Omega I_3$

Example continued on the next slide.

8/25/2010

Example (cont) Build that matrix equation

(13)

$$\#1: 12v = 6k\Omega I_1 - 2k\Omega I_2 - 3k\Omega I_3$$

$$\#2: 0 = -2k\Omega I_1 + 8k\Omega I_2 - 4k\Omega I_3$$

$$\#3: 5 = -3k\Omega I_1 - 4k\Omega I_2 + 7k\Omega I_3$$

$$\begin{bmatrix} 12v \\ 0 \\ 5v \end{bmatrix} = \begin{bmatrix} 6k & -2k & -3k \\ -2k & 8k & -4k \\ -3k & -4k & 7k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Example continued
on the next slide.

8/25/2010

Example (cont) Cramer's Rule

(14)

$$\begin{bmatrix} 12v \\ 0 \\ 5v \end{bmatrix} = \begin{bmatrix} 6k & -2k & -3k \\ -2k & 8k & -4k \\ -3k & -4k & 7k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$D = \begin{vmatrix} 6k & -2k & -3k \\ -2k & 8k & -4k \\ -3k & -4k & 7k \end{vmatrix} \quad D_1 = \begin{vmatrix} 12 & -2k & -3k \\ 0 & 8k & -4k \\ 5 & -4k & 7k \end{vmatrix}$$

$$D_2 = \begin{vmatrix} 6k & 12 & -3k \\ -2k & 0 & -4k \\ -3k & 5 & 7k \end{vmatrix} \quad D_3 = \begin{vmatrix} 6k & -2k & 12 \\ -2k & 8k & 0 \\ -3k & -4k & 5 \end{vmatrix}$$

By Cramer's Rule,

$$I_1 = \frac{D_1}{D} \quad I_2 = \frac{D_2}{D} \quad I_3 = \frac{D_3}{D}$$

Example continued
on the next slide.

8/25/2010

Example (cont) Solve for the main determinate (D)

(15)

Demonstrating the special method which applies
ONLY to 3x3 matrices.

$$D = \begin{vmatrix} 6k & -2k & -3k \\ -2k & 8k & -4k \\ -3k & -4k & 7k \end{vmatrix}$$

$$D = [(6k)(8k)(7k) + (-2k)(-4k)(-3k) + (-3k)(-2k)(-4k)] - [(-3k)(8k)(-3k) + (6k)(-4k)(-4k) + (-2k)(-2k)(7k)]$$

$$D = [288G - 24G - 24G] - [72G + 96G + 28G]$$

$$D = [288G] - [196G] = 92G$$

Example continued
on the next slide.

8/25/2010

Example (cont) Solve for the I_1

16

$$D = 92G \quad D_1 = \begin{vmatrix} 12v & -2k & -3k \\ 0v & 8k & -4k \\ 5v & -4k & 7k \end{vmatrix} \quad \text{and} \quad I_1 = \frac{D_1}{D}$$

cofactor sign equation: $a^{ij} = (-1)^{i+j}$

$$D_1 = (-1)^{1+1} \begin{vmatrix} 8k & -4k \\ -4k & 7k \end{vmatrix} + (-1)^{1+2} \begin{vmatrix} 0 & -4k \\ 5 & 7k \end{vmatrix} + (-1)^{1+3} \begin{vmatrix} 0 & 8k \\ 5 & -4k \end{vmatrix}$$

$$D_1 = (1) \begin{vmatrix} 8k & -4k \\ -4k & 7k \end{vmatrix} + (-1) \begin{vmatrix} 0 & -4k \\ 5 & 7k \end{vmatrix} + (1) \begin{vmatrix} 0 & 8k \\ 5 & -4k \end{vmatrix}$$

$$D_1 = 12[8k(7k) - (-4k)(-4k)] + 2k[0(7k) - (-4k)(5)] - 3k[0(-4k) - (8k)(5)]$$

$$D_1 = 12[56k^2 - 16k^2] + 2k[0 - (-20k)] - 3k[0 - 40k]$$

$$= 12[40k^2] + 2k[20k] - 3k[-40k]$$

$$D_1 = 480k + 40k + 120k = 640k$$

$$I_1 = \frac{D_1}{D} = \frac{640k}{92G} = 6.957mA$$

Example continued on the next slide.

8/25/2010

Example (cont) Solve for the I_2

17

$$D = 92G \quad D_2 = \begin{vmatrix} 6k & 12v & -3k \\ -2k & 0v & -4k \\ -3k & 5v & 7k \end{vmatrix} \quad I_2 = \frac{D_2}{D}$$

cofactor sign equation $a^{ij} = (-1)^{i+j}$

$$D_2 = (-1)^{1+1} \begin{vmatrix} 0 & -4k \\ 5 & 7k \end{vmatrix} + (-1)^{1+2} \begin{vmatrix} -2k & -4k \\ -3k & 7k \end{vmatrix} + (-1)^{1+3} \begin{vmatrix} -2k & 0 \\ -3k & 5 \end{vmatrix}$$

$$= (-1)^2 (6k)[0(7k) - (-4k)(5)] + (-1)^3 (12)[-2k(7k) - (-4k)(-3k)]$$

$$+ (-1)^4 (-3k)[-2k(5) - (0)(-3k)]$$

$$= (1)(6k)[0 - (-20k)] + (-1)(12)[-14k - (12k)] + (1)(-3k)[-10k - 0]$$

$$= 6k[20k] + (-12)[-26k] + (-3k)[-10k]$$

$$= 120k + 312k + 30k = 462k$$

$$I_2 = \frac{D_2}{D} = \frac{462k}{92G} = 5.022mA$$

Example continued on the next slide.

8/25/2010

Example (cont) Solve for the I_3

18

$$D = 92G \quad D_3 = \begin{vmatrix} 6k & -2k & 12v \\ -2k & 8k & 0v \\ -3k & -4k & 5v \end{vmatrix} \quad \text{and} \quad I_3 = \frac{D_3}{D}$$

cofactor sign equation $a^{ij} = (-1)^{i+j}$

$$D_3 = (-1)^{1+1} \begin{vmatrix} 8k & 0 \\ -4k & 5 \end{vmatrix} + (-1)^{1+2} \begin{vmatrix} -2k & 0 \\ -3k & 5 \end{vmatrix} + (-1)^{1+3} \begin{vmatrix} -2k & 8k \\ -3k & -4k \end{vmatrix}$$

$$= (-1)^2 (6k)[(8k)(5) - 0(-4k)] + (-1)^3 (-2k)[-2k(5) - (0)(-3k)]$$

$$+ (-1)^4 (12)[-2k(-4k) - (8k)(-3k)]$$

$$= (1)(6k)[40k - 0] + (-1)(-2k)[-10k - 0] + (1)(12)[8k + 24k]$$

$$= 6k[40k] + 2k[-10k] + 12[32k]$$

$$= 240k - 20k + 384k = 604k$$


$$I_3 = \frac{D_3}{D} = \frac{604k}{92G} = 6.565mA$$

Example continued on the next slide.

8/25/2010

Example (cont) Intermediate results

19

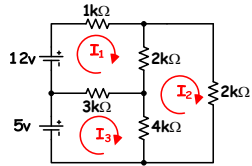

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$

Using these values you can calculate the rest of the unknowns. For this set of notes, we will only calculate two: I_{3k} and I_{4k} .


Example continued on the next slide.

8/25/2010

Example (continued)

20

Add in the currents in random directions

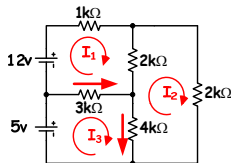

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$


Current directions have been added to the circuit. Since at this point we don't know the actual directions, we will just guess.

Example continued on the next slide.

8/25/2010

Example (cont) Calculate I_{3k}

21

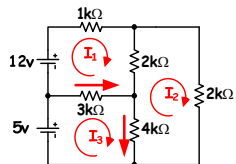

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$

I_{3k} consists of I_1 and I_3 . Since the drawn direction is in the direction of I_3 , the calc will be:


$$I_{3k} = I_3 - I_1$$

Example continued on the next slide.

8/25/2010

Example (cont) Calculate I_{3k}

22

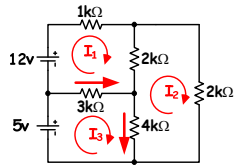

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$

$$I_{3k} = I_3 - I_1$$

$$I_{3k} = 6.565\text{mA} - 6.957\text{mA}$$


$$= \boxed{-392.0\mu\text{A}}$$

Example continued
on the next slide.

8/25/2010

Example (cont) Calculate I_{4k}

23

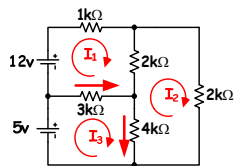

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$

$$I_{4k} = I_3 - I_2$$

$$I_{4k} = 6.565\text{mA} - 5.022\text{mA}$$

$$= \boxed{1.543\text{mA}}$$

Example continued
on the next slide.

8/25/2010
