



FE Review

1

ELECTRONICS # 2 DC CIRCUIT ANALYSIS

Source or Sink?

2

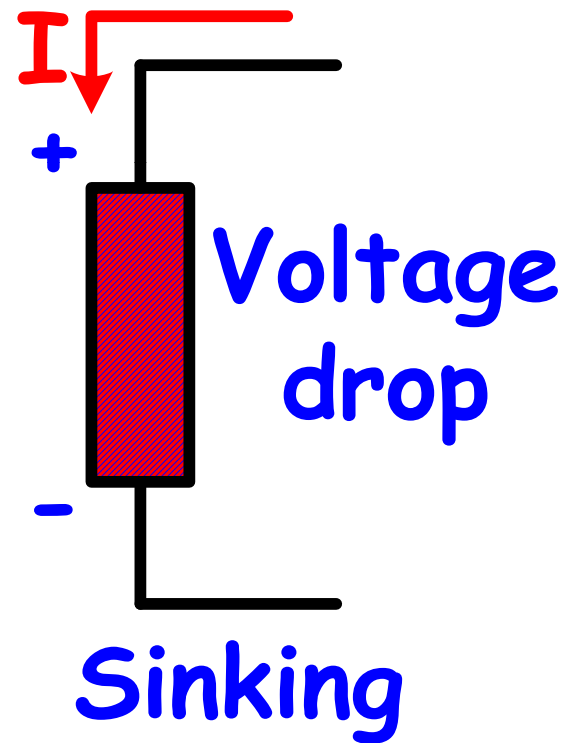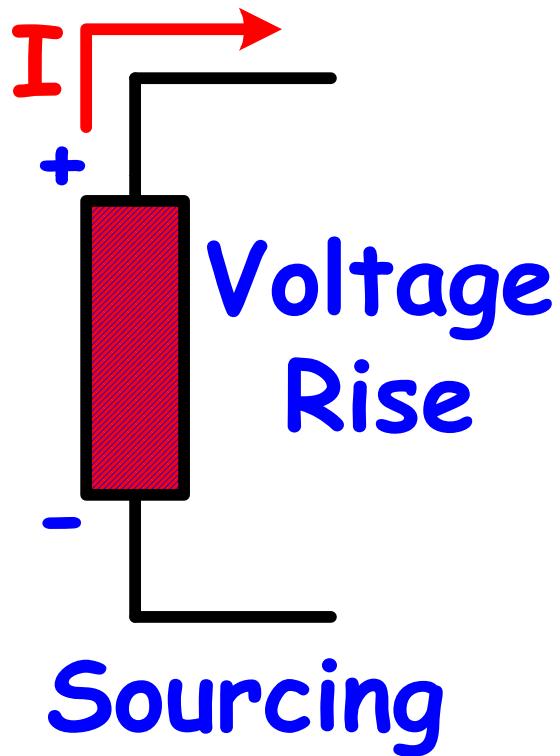

Power

3

$$\text{Power} = P = VI$$

From Ohm's Law we have

$$V=IR \quad I=\frac{V}{R}$$

From these equations we get

$$\begin{aligned} P &= VI & P &= VI \\ &= (IR)I & P &= V\left(\frac{V}{R}\right) \\ P &= I^2R & P &= \frac{V^2}{R} \end{aligned}$$

Capacitors and Inductors in DC circuits

4

Since V and I don't vary with time in a DC circuit, Capacitors and Inductors don't act the way they would in an AC circuit.


In DC circuits:

Capacitors act like OPEN-CIRCUITS

Inductors act like SHORT-CIRCUITS

DC Circuit Analysis Mesh Example

5

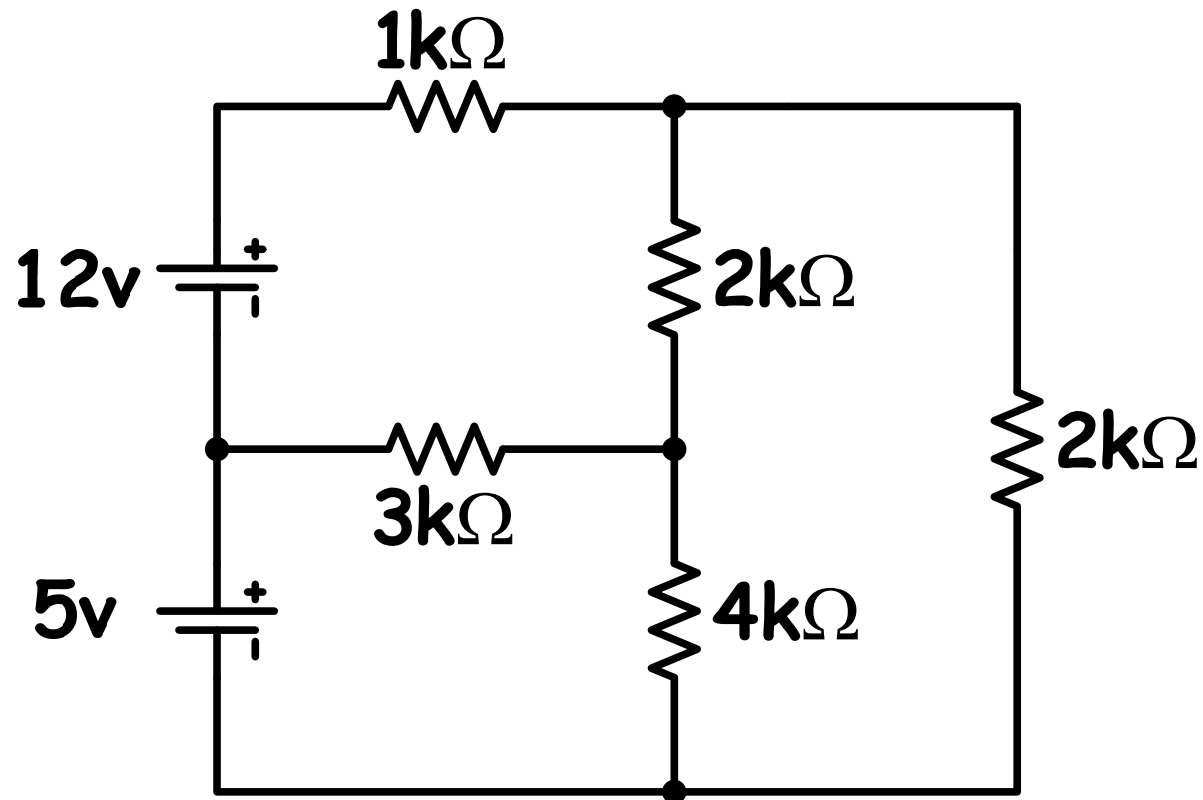


Example continued
on the next slide.

Example (continued)

6

Add in three **CLOCKWISE** loop currents

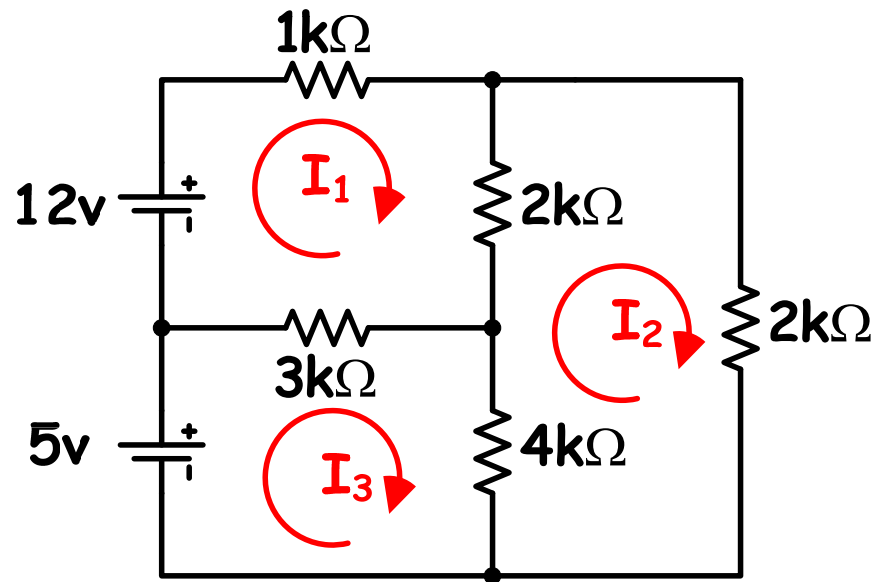


Step 1:
It is important that
the loop currents be
drawn in the **clock-
wise direction**

Example continued
on the next slide.

Example (continued)

7

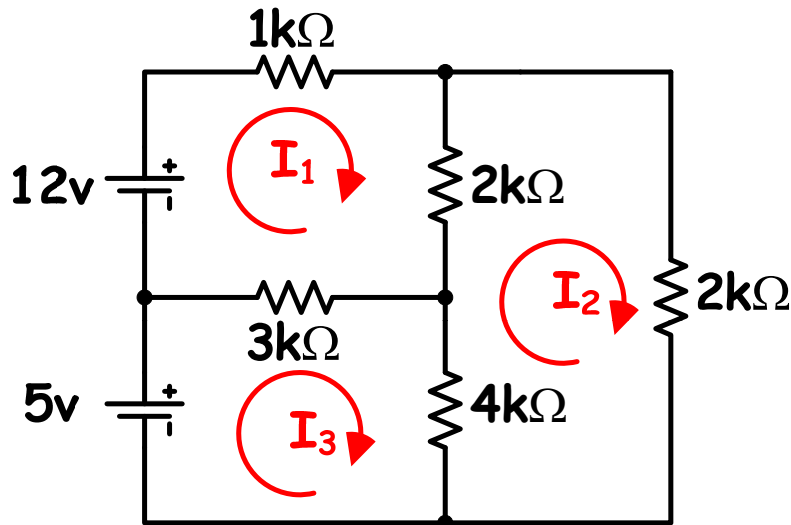

Call on good old KVL

Step 2:
We will use KVL to
write a loop eqn. for
each mesh current.

@ I₁

$$0 = -12\text{v} + 1\text{k}\Omega I_1 + 2\text{k}\Omega (I_1 - I_2) + 3\text{k}\Omega (I_1 - I_3)$$


$$12\text{v} = 1\text{k}\Omega I_1 + 2\text{k}\Omega I_1 - 2\text{k}\Omega I_2 + 3\text{k}\Omega I_1 - 3\text{k}\Omega I_3$$

$$\boxed{12\text{v} = 6\text{k}\Omega I_1 - 2\text{k}\Omega I_2 - 3\text{k}\Omega I_3}$$

Example continued
on the next slide.

Example (cont.) Call on good old KVL

8

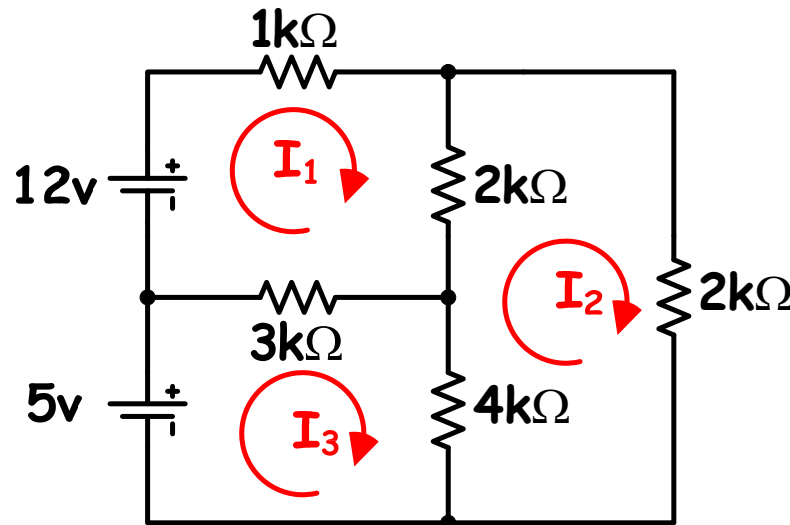


Note that the sign for the current we are working with is + while the signs of both of the others is negative. This is a good 'idiot' check.

$$@ I_1 \quad 12\text{v} = 6\text{k}\Omega I_1 - 2\text{k}\Omega I_2 - 3\text{k}\Omega I_3$$

Example continued on the next slide.

Example (cont.) Call on good old KVL

9

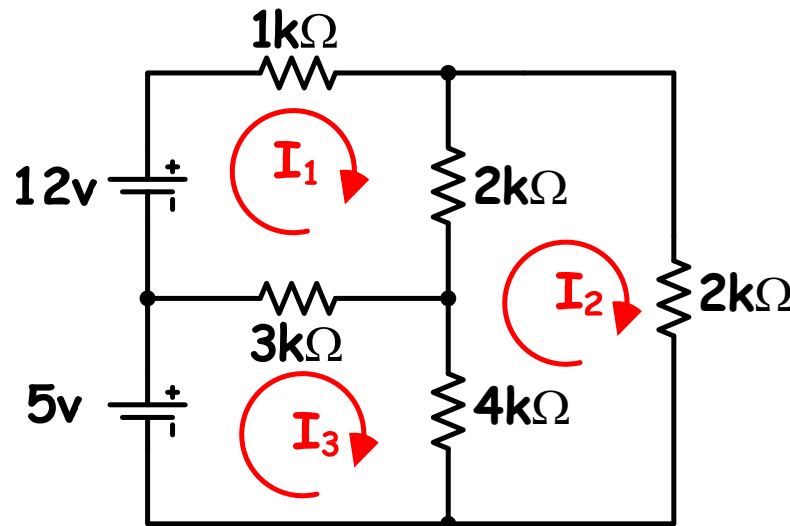

Also note that the sum of the resistors in the I₁ loop is 6k just as in the equation. This is another 'idiot' check.


@ I₁

$$12\text{v} = 6\text{k}\Omega\text{I}_1 - 2\text{k}\Omega\text{I}_2 - 3\text{k}\Omega\text{I}_3$$

Example continued on the next slide.

Example (cont.) Call on good old KVL

10

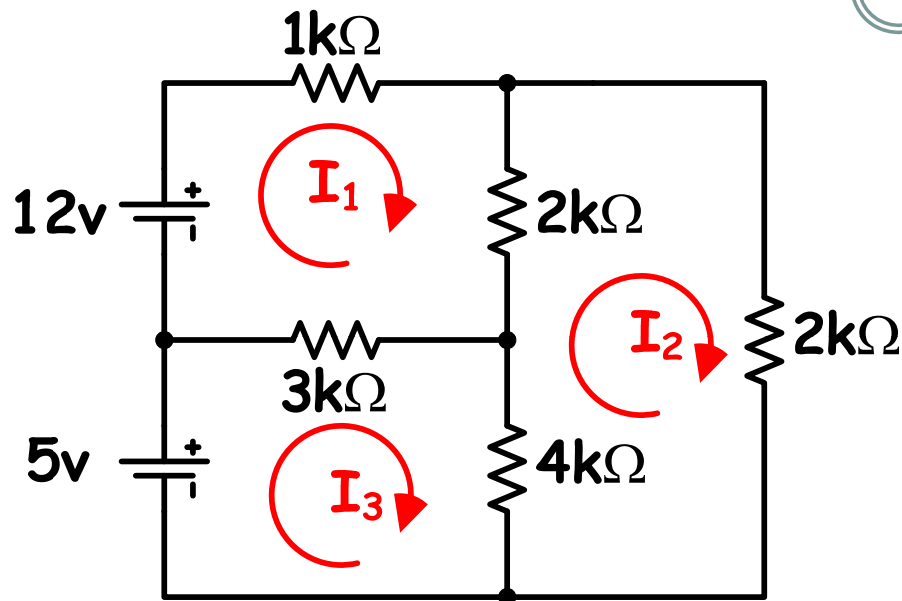

Perform the same idiot checks on the I2 loop equation below.

@ I_2

$$0 = 2kI_2 + 4k\Omega(I_2 - I_3) + 2k\Omega(I_2 - I_1)$$


$$0 = 2kI_2 + 4k\Omega I_2 - 4k\Omega I_3 + 2k\Omega I_2 - 2k\Omega I_1$$

$$0 = -2k\Omega I_1 + 8k\Omega I_2 - 4k\Omega I_3$$

Example continued on the next slide.

Example (cont) Call on good old KVL

11

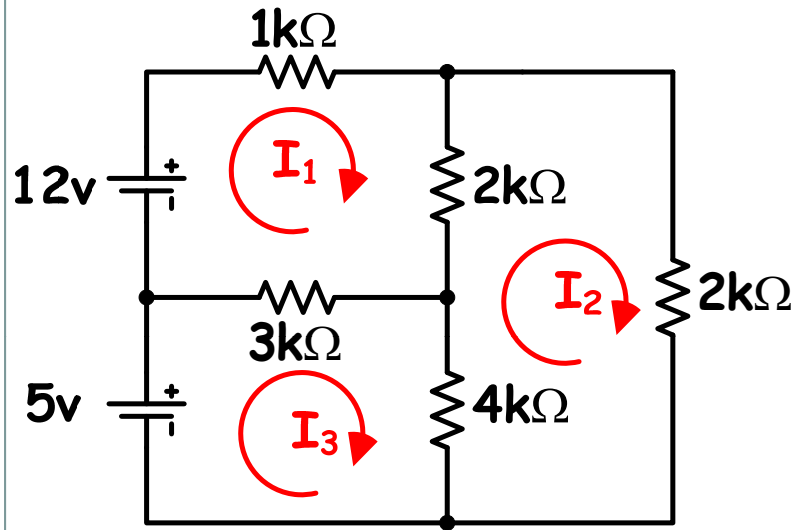

Perform the same idiot checks on the I3 loop equation below.

@ I_3

$$0 = -5\text{v} + 3\text{k}\Omega(I_3 - I_1) + 4\text{k}\Omega(I_3 - I_2)$$

$$5\text{v} = 3\text{k}\Omega I_3 - 3\text{k}\Omega I_1 + 4\text{k}\Omega I_3 - 4\text{k}\Omega I_2$$

$$\boxed{5\text{v} = -3\text{k}\Omega I_1 - 4\text{k}\Omega I_2 + 7\text{k}\Omega I_3}$$

Example continued on the next slide.

Example (continued)

12

Three eqn's, three unknowns

$$\# 1 : 12\text{v} = 6\text{k}\Omega I_1 - 2\text{k}\Omega I_2 - 3\text{k}\Omega I_3$$

$$\# 2 : 0 = -2\text{k}\Omega I_1 + 8\text{k}\Omega I_2 - 4\text{k}\Omega I_3$$

$$\# 3 : 5 = -3\text{k}\Omega I_1 - 4\text{k}\Omega I_2 + 7\text{k}\Omega I_3$$

Example continued
on the next slide.

Example (cont) Build that matrix equation

13

$$\# 1 : 12v = 6k\Omega I_1 - 2k\Omega I_2 - 3k\Omega I_3$$

$$\# 2 : 0 = -2k\Omega I_1 + 8k\Omega I_2 - 4k\Omega I_3$$

$$\# 3 : 5 = -3k\Omega I_1 - 4k\Omega I_2 + 7k\Omega I_3$$

$$\begin{bmatrix} 12v \\ 0 \\ 5v \end{bmatrix} = \begin{bmatrix} 6k & -2k & -3k \\ -2k & 8k & -4k \\ -3k & -4k & 7k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Example continued
on the next slide.

Example (cont) Cramer's Rule

14

$$\begin{bmatrix} 12v \\ 0 \\ 5v \end{bmatrix} = \begin{bmatrix} 6k & -2k & -3k \\ -2k & 8k & -4k \\ -3k & -4k & 7k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$D = \begin{vmatrix} 6k & -2k & -3k \\ -2k & 8k & -4k \\ -3k & -4k & 7k \end{vmatrix} \quad D_1 = \begin{vmatrix} 12 & -2k & -3k \\ 0 & 8k & -4k \\ 5 & -4k & 7k \end{vmatrix}$$

$$D_2 = \begin{vmatrix} 6k & 12 & -3k \\ -2k & 0 & -4k \\ -3k & 5 & 7k \end{vmatrix} \quad D_3 = \begin{vmatrix} 6k & -2k & 12 \\ -2k & 8k & 0 \\ -3k & -4k & 5 \end{vmatrix}$$

By Cramer's Rule,

$$I_1 = \frac{D_1}{D} \quad I_2 = \frac{D_2}{D} \quad I_3 = \frac{D_3}{D}$$

Example continued
on the next slide.

Example (cont) Solve for the main determinate (D)

15

Demonstrating the special method which applies ONLY to 3x3 matrices.

$$D = D = \begin{vmatrix} 6k & -2k & -3k & | & 6k & -2k \\ -2k & 8k & -4k & | & -2k & 8k \\ -3k & -4k & 7k & | & -3k & -4k \end{vmatrix}$$

$$D = \left[(6k)(8k)(7k) + (-2k)(-4k)(-3k) + (-3k)(-2k)(-4k) \right] \\ - \left[(-3k)(8k)(-3k) + (6k)(-4k)(-4k) + (-2k)(-2k)(7k) \right]$$

$$D = [288G - 24G - 24G] - [72G + 96G + 28G]$$

$$D = [288G] - [196G] = 92G$$

Example continued
on the next slide.

Example (cont) Solve for the I_1

16

$$D = 92G \quad D_1 = \begin{vmatrix} 12v & -2k & -3k \\ 0v & 8k & -4k \\ 5v & -4k & 7k \end{vmatrix} \quad \text{and} \quad I_1 = \frac{D_1}{D}$$

cofactor sign equation: $a^{ij} = (-1)^{i+j}$

$$D_1 = (-1)^{1+1}(12) \begin{vmatrix} 8k & -4k \\ -4k & 7k \end{vmatrix} + (-1)^{2+1}(-2k) \begin{vmatrix} 0 & -4k \\ 5 & 7k \end{vmatrix} + (-1)^{3+1}(-3k) \begin{vmatrix} 0 & 8k \\ 5 & -4k \end{vmatrix}$$

$$D_1 = (1)(12) \begin{vmatrix} 8k & -4k \\ -4k & 7k \end{vmatrix} + (-1)(-2k) \begin{vmatrix} 0 & -4k \\ 5 & 7k \end{vmatrix} + (1)(-3k) \begin{vmatrix} 0 & 8k \\ 5 & -4k \end{vmatrix}$$

$$D_1 = 12[8k(7k) - (-4k)(-4k)] + 2k[0(7k) - (-4k)(5)] - 3k[0(-4k) - (8k)(5)]$$

$$D_1 = 12[56M - 16M] + 2k[0 - (-20k)] - 3k[0 - 40k]$$

$$= 12[40M] + 2k[20k] - 3k[-40k]$$

$$D_1 = 480M + 40M + 120M = 640M$$

$$I_1 = \frac{D_1}{D} = \frac{640M}{92G} = 6.957mA$$

Example continued
on the next slide.

Example (cont) Solve for the I_2

17

$$D = 92G \quad D_2 = \begin{vmatrix} 6k & 12v & -3k \\ -2k & 0v & -4k \\ -3k & 5v & 7k \end{vmatrix} \quad I_2 = \frac{D_2}{D}$$

cofactor sign equation $a^{ij} = (-1)^{i+j}$

$$\begin{aligned} D_2 &= (-1)^{1+1} (6k) \begin{vmatrix} 0 & -4k \\ 5 & 7k \end{vmatrix} + (-1)^{1+2} (12) \begin{vmatrix} -2k & -4k \\ -3k & 7k \end{vmatrix} + (-1)^{1+3} (-3k) \begin{vmatrix} -2k & 0 \\ -3k & 5 \end{vmatrix} \\ &= (-1)^2 (6k) [0(7k) - (-4k)5] + (-1)^3 (12) [-2k(7k) - (-4k)(-3k)] \\ &\quad + (-1)^4 (-3k) [-2k(5) - (0)(-3k)] \\ &= (1)(6k) [0 - (-20k)] + (-1)(12) [-14M - (12M)] + (1)(-3k) [-10k - 0] \\ &= 6k [20k] + (-12) [-26M] + (-3k) [-10k] \\ &= 120M + 312M + 30M = 462M \end{aligned}$$

$$I_2 = \frac{D_2}{D} = \frac{462M}{92G} = 5.022mA$$

Example continued
on the next slide.

Example (cont) Solve for the I_3

18

$$D = 92G \quad D_3 = \begin{vmatrix} 6k & -2k & 12v \\ -2k & 8k & 0v \\ -3k & -4k & 5v \end{vmatrix} \quad \text{and} \quad I_3 = \frac{D_3}{D}$$

cofactor sign equation $a^{ij} = (-1)^{i+j}$


$$\begin{aligned} D_3 &= (-1)^{1+1} (6k) \begin{vmatrix} 8k & 0 \\ -4k & 5 \end{vmatrix} + (-1)^{1+2} (-2k) \begin{vmatrix} -2k & 0 \\ -3k & 5 \end{vmatrix} + (-1)^{1+3} (12) \begin{vmatrix} -2k & 8k \\ -3k & -4k \end{vmatrix} \\ &= (-1)^2 (6k) [(8k)5 - 0(-4k)] + (-1)^3 (-2k) [-2k(5) - (0)(-3k)] \\ &\quad + (-1)^4 (12) [-2k(-4k) - (8k)(-3k)] \\ &= (1)(6k)[40k - 0] + (-1)(-2k)[-10k - 0] + (1)(12)[8M + 24M] \\ &= 6k[40k] + 2k[-10k] + 12[32M] \\ &= 240M - 20M + 384M = \boxed{604M} \end{aligned}$$

$$I_3 = \frac{D_3}{D} = \frac{604M}{92G} = \boxed{6.565mA}$$

Example continued
on the next slide.

Example (cont) Intermediate results

19

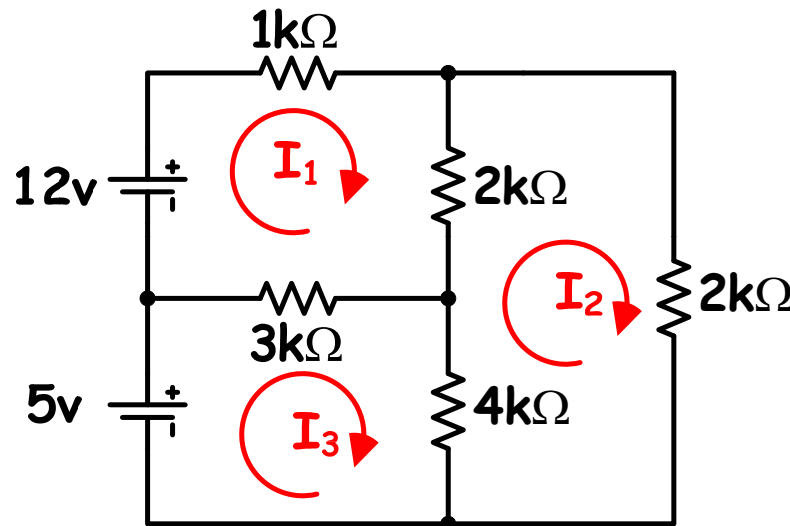

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$


Using these values you can calculate the rest of the unknowns. For this set of notes, we will Only calculate two: I_{3k} and I_{4k} .

Example continued on the next slide.

Example (continued)

20

Add in the currents in random directions

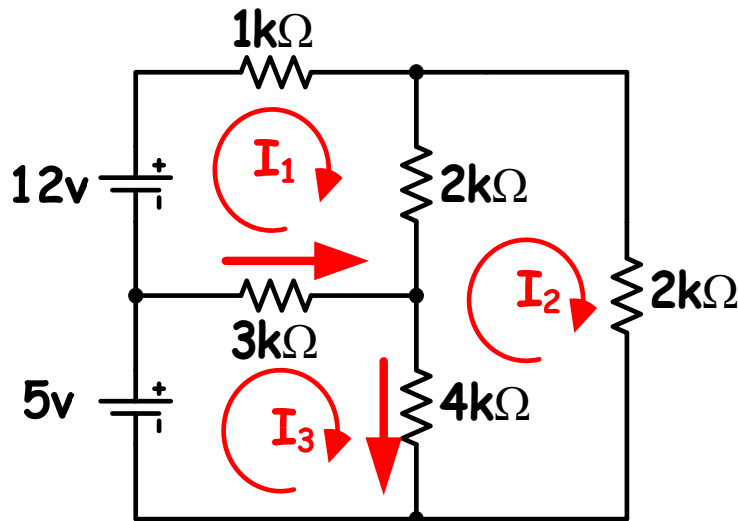

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$


$$I_3 = 6.565\text{mA}$$

Current directions have been added to the circuit. Since at this point we don't know the actual directions, we will just guess.

Example continued
on the next slide.

Example (cont) Calculate I_{3k}

21

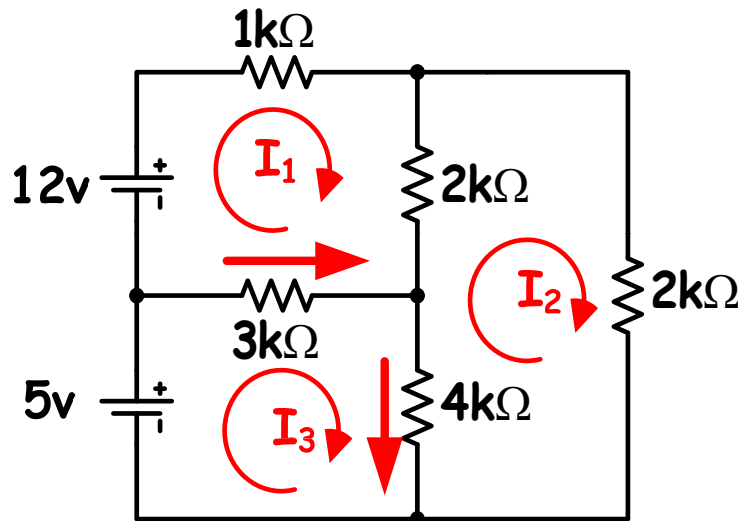

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$


I_{3k} consists of I_1 and I_3 . Since the drawn direction is in the direction of I_3 , the calc will be:

$$I_{3k} = I_3 - I_1$$

Example continued on the next slide.

Example (cont) Calculate I_{3k}

22

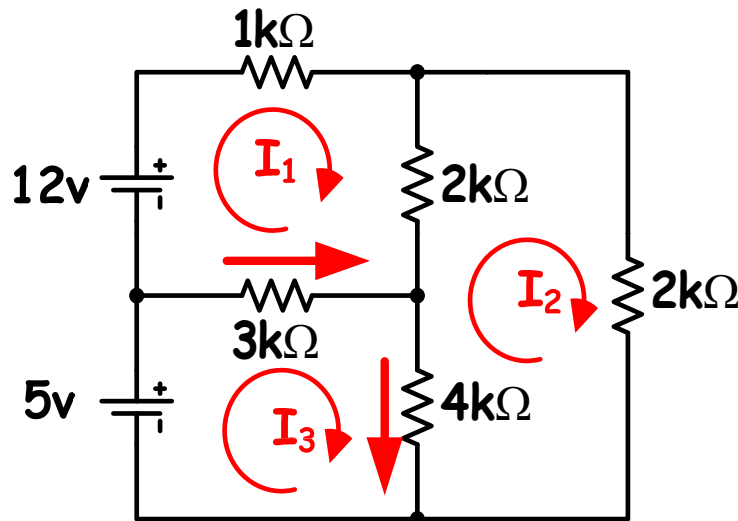

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$

$$I_{3k} = I_3 - I_1$$


$$I_{3k} = 6.565\text{mA} - 6.957\text{mA}$$

$$= \boxed{-392.0\mu\text{A}}$$

Example continued
on the next slide.

Example (cont) Calculate I_{4k}

23

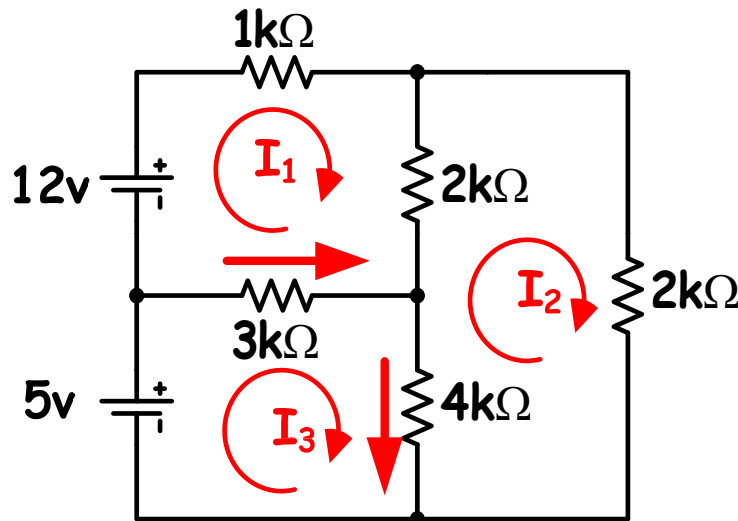

Results

$$I_1 = 6.957\text{mA}$$

$$I_2 = 5.022\text{mA}$$

$$I_3 = 6.565\text{mA}$$

$$I_{4k} = I_3 - I_2$$

$$I_{4k} = 6.565\text{mA} - 5.022\text{mA}$$

$$= \boxed{1.543\text{mA}}$$

Example continued
on the next slide.