# **FE Review** 1 THEVENIN AND NORTON ANALYSIS

### Thevenin's Theorem

Any linear, two-terminal network with dependent and independent sources can be represented by an equivalent circuit consisting of a single voltage source and a single series resistor representing the circuit from the VIEWPOINT of the circuits load.









Step 3: Find the Equivalent Resistance from the viewpoint of the load

Note that the 16 ohm resistor is shorted out!

$$R_{\text{th}} = 4 || 12 = \frac{4\Omega(12\Omega)}{4\Omega + 12\Omega} = \frac{48\Omega}{16} = 3\Omega$$
Continued on the next page





### Maximum Power Transfer

Another way the question may be asked: What value of  $R_{TH}$  is necessary below for max power transfer to the load?

![](_page_7_Figure_2.jpeg)

#### Maximum Power Transfer

Another way the question may be asked: What value of  $R_{TH}$  is necessary below for max power transfer to the load?

![](_page_8_Figure_2.jpeg)

The answer is 'O ohms'. The difference here is that the load is no longer the variable.

## Norton's Theorem

 Any linear, two-terminal network with dependent and independent sources can be represented by an equivalent circuit consisting of a single current source and a single parallel resistor representing the circuit from the VIEWPOINT of the circuits load.

![](_page_10_Figure_0.jpeg)

![](_page_11_Figure_0.jpeg)

![](_page_12_Figure_0.jpeg)

![](_page_13_Picture_0.jpeg)

![](_page_14_Figure_0.jpeg)

![](_page_15_Figure_0.jpeg)

![](_page_16_Figure_0.jpeg)

![](_page_17_Figure_0.jpeg)

Note that the right hand 8 ohm resistor is shorted out

Continued on the next page

![](_page_18_Figure_0.jpeg)

![](_page_19_Figure_0.jpeg)