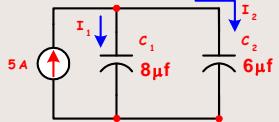


Capacitor Current Divider (Like a resistor voltage divider)




$$I_1 = \frac{IC_1}{C_1 + C_2} = \frac{5A(8\mu F)}{8\mu F + 6\mu F} = [2.857A]$$

$$I_2 = \frac{IC_2}{C_1 + C_2} = \frac{5A(6\mu F)}{8\mu F + 6\mu F} = [2.143A]$$

The two currents together **MUST** add up to 5 amps (Naturally) (taking roundoff error into account)

4

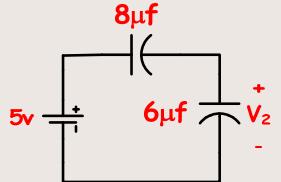Capacitor voltage divider (Like a resistor current divider)



$$V_2 = \frac{5vC_1}{C_1 + C_2} = \frac{5v(8\mu F)}{8\mu F + 6\mu F} = \frac{40v}{14} = [2.857v]$$

5

Inductors

Treat inductors just like resistors.
This includes the inductive voltage and current divider equations.

6

First Order Fundamentals

$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$$

Final Value
(steady state value)

Initial Value

time constant

7

Initial and Final Values

To start with, let's consider a switch. In analyzing the switch, we will consider two extremes:

- ♦ The instant a switch is closed (the **Initial Value**), and
- ♦ the **steady state value** (a long time has passed since the switch closed) (The **Final Value**).

8

When you have a circuit in which you are working out the initial values,

- An **uncharged capacitor** acts as a **short circuit**.
(It opposes a change in voltage)
- A **un-fluxed inductor** acts as an **open circuit**.
(It opposes a change in current).

9

Extending this idea to the device with an Initial charge, we get:

$$V_C(0+) = V_o \Leftarrow \text{a voltage source!}$$

$$i_L(0+) = I_o \Leftarrow \text{a current source!}$$

10

Final Conditions

$$i_c(t \Rightarrow \infty) = 0 \quad \text{Capacitor current} \Rightarrow 0 \quad [\text{open}]$$

$$v_L(t \Rightarrow \infty) = 0 \quad \text{Inductor voltage} \Rightarrow 0 \quad [\text{short}]$$


another way to write these values would be:

$$i_c(\infty) = 0 \quad \text{and} \quad v_L(\infty) = 0$$



11

RC circuit - Charge Phase

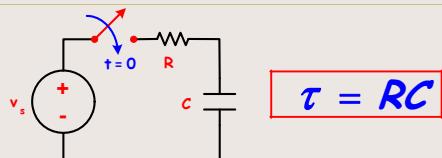

12

$$\gamma = V_c(t)$$


$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-t/\tau}$$

$$\left. \begin{array}{l} y(0^+) = V_c(0^+) = 0v \\ y(\infty) = V_c(\infty) = V_s \end{array} \right\} \begin{array}{l} \text{determined} \\ \text{earlier} \end{array}$$

$$V_c(t) = V_s + [0v - V_s] e^{-t/\tau}$$

$$V_c(t) = V_s \left(1 - e^{-t/\tau} \right)$$

13

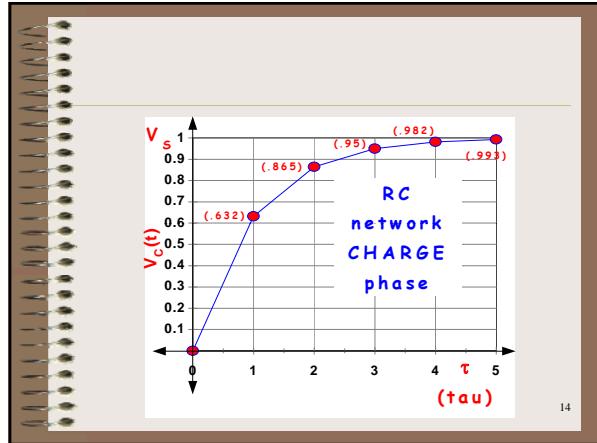

RC Circuit - Discharge Phase

Discharge phase - Voltage


$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-t/\tau}$$

$$V_c(0^+) = V_s \quad V_c(\infty) = 0v$$


Note that it is assumed here that the capacitor had time to completely charge to V_s .

$$V_c(t) = 0v + [V_s - 0v] e^{-t/\tau} \Rightarrow V_c(t) = V_s e^{-t/\tau}$$


15

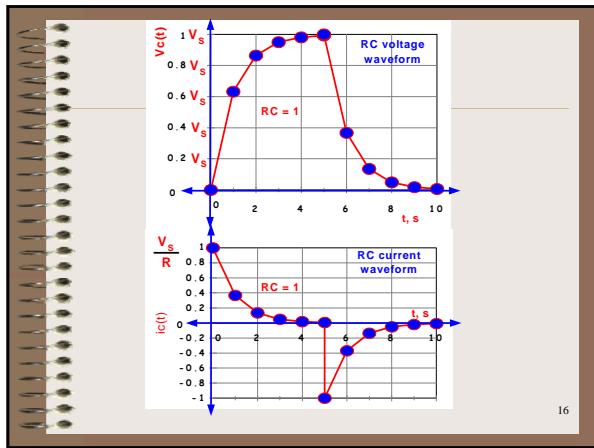


16

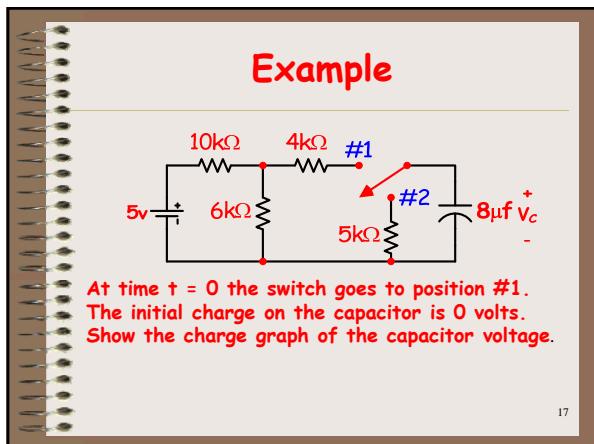

17

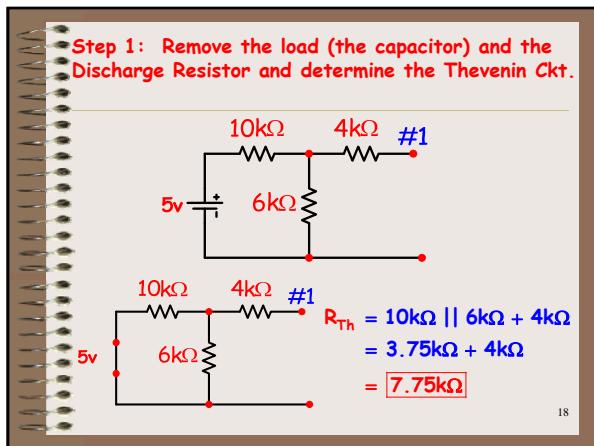


18

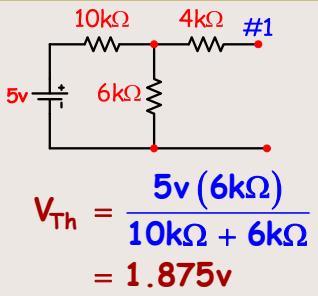

$$V_{Th} = \frac{5v(6k\Omega)}{10k\Omega + 6k\Omega} = 1.875v$$

19

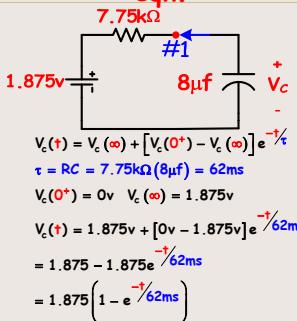
Place the Cap onto the Thevenin circuit and then calculate the charge eqn.



$$\begin{aligned} V_c(t) &= V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-\frac{t}{\tau}} \\ \tau &= RC = 7.75k\Omega (8\mu F) = 62ms \\ V_c(0^+) &= 0v \quad V_c(\infty) = 1.875v \\ V_c(t) &= 1.875v + [0v - 1.875v] e^{-\frac{t}{62ms}} \\ &= 1.875 - 1.875e^{-\frac{t}{62ms}} \\ &= 1.875 \left(1 - e^{-\frac{t}{62ms}}\right) \end{aligned}$$

20

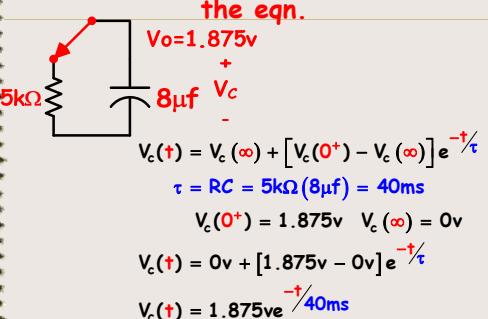Now place the cap with the discharge resistor and recalculate the eqn.



$$\begin{aligned} V_c(t) &= V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-\frac{t}{\tau}} \\ \tau &= RC = 5k\Omega (8\mu F) = 40ms \\ V_c(0^+) &= 1.875v \quad V_c(\infty) = 0v \\ V_c(t) &= 0v + [1.875v - 0v] e^{-\frac{t}{40ms}} \\ V_c(t) &= 1.875ve^{-\frac{t}{40ms}} \end{aligned}$$

21