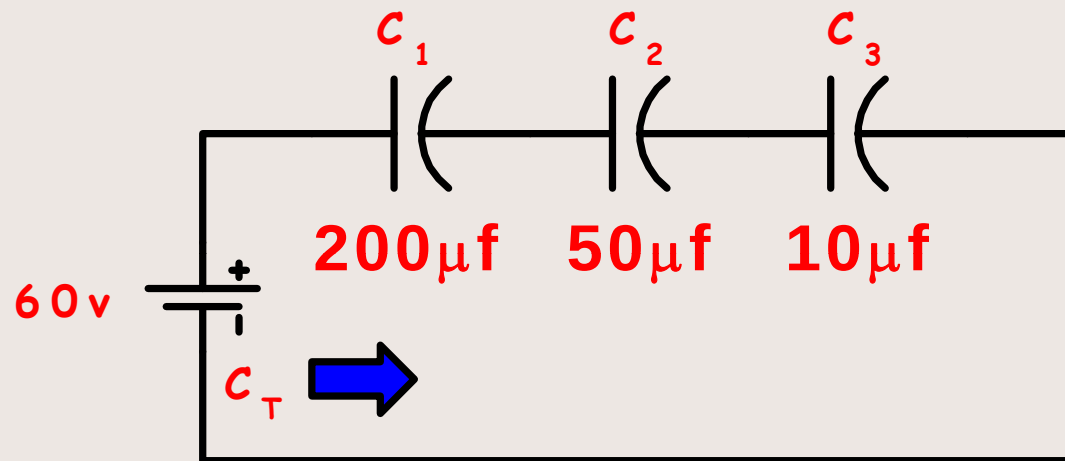


FE Review

RC and RL Analysis

Series Capacitors

Treat like parallel resistors




$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_T} = \frac{1}{200\mu f} + \frac{1}{50\mu f} + \frac{1}{10\mu f} = 125k$$

$$C_T = 8\mu f$$

Parallel Capacitors


Treat like series resistors

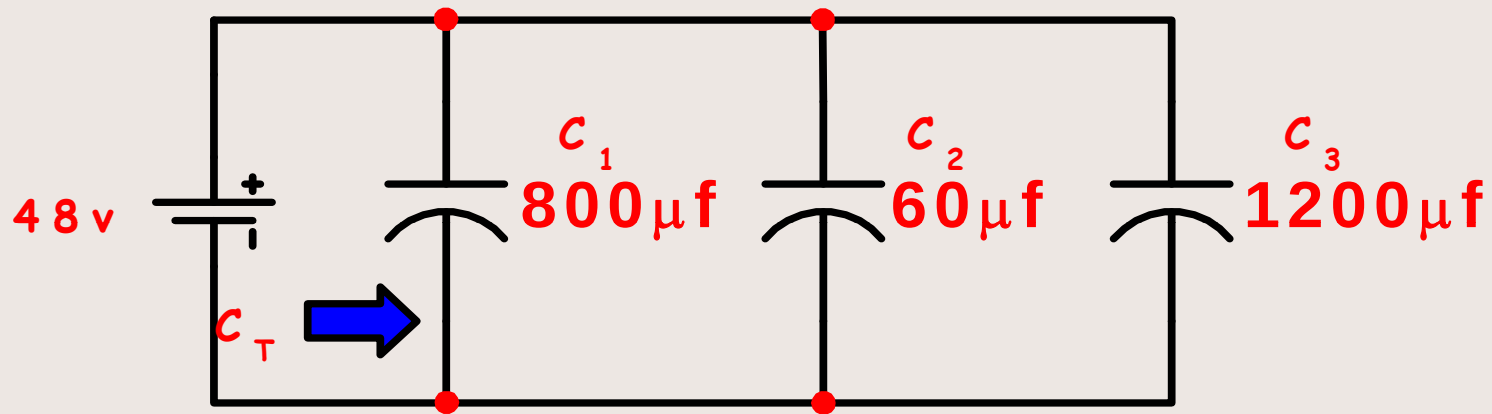

$$C_T = C_1 + C_2 + C_3$$

$$= 800\mu f + 60\mu f + 1200\mu f = \boxed{2.06mf}$$

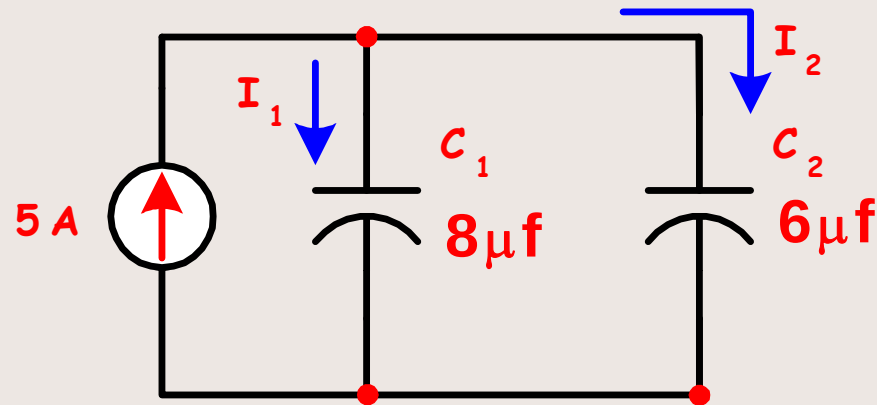Capacitor Current Divider (Like a resistor voltage divider)




$$I_1 = \frac{IC_1}{C_1 + C_2} = \frac{5A(8\mu\text{f})}{8\mu\text{f} + 6\mu\text{f}} = \boxed{2.857A}$$

$$I_2 = \frac{IC_2}{C_1 + C_2} = \frac{5A(6\mu\text{f})}{8\mu\text{f} + 6\mu\text{f}} = \boxed{2.143A}$$

The two currents together **MUST**
add up to 5 amps (Naturally) (taking
roundoff error into account)

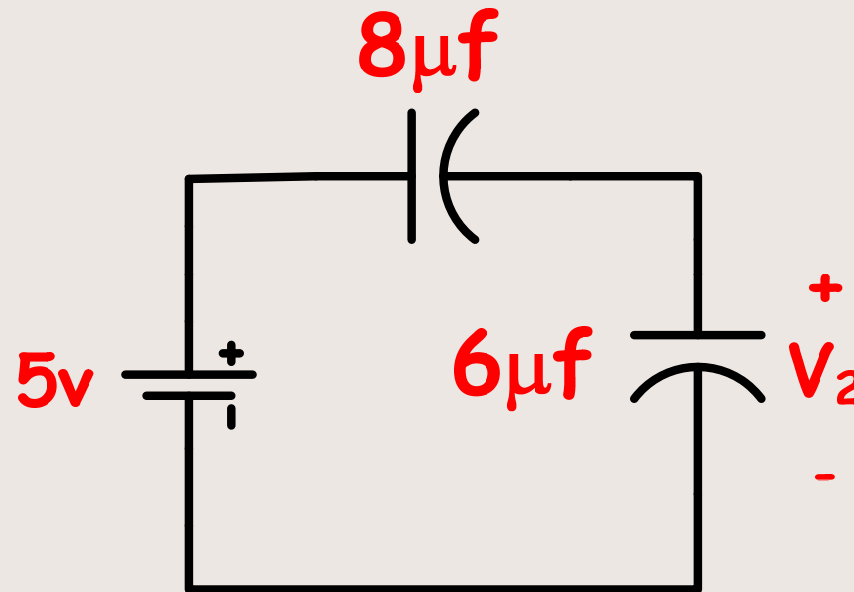Capacitor voltage divider (Like a resistor current divider)



$$V_2 = \frac{5\text{v}C_1}{C_1 + C_2} = \frac{5\text{v}(8\mu\text{f})}{8\mu\text{f} + 6\mu\text{f}} = \frac{40\text{v}}{14} = \boxed{2.857\text{v}}$$

Inductors

Treat inductors just like resistors.
This includes the inductive voltage
and current divider equations.

First Order Fundamentals

Final Value
(steady state value)

$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$$

Initial Value

time constant

The diagram shows the equation $v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$ with several annotations. A bracket above the equation points to $v(\infty)$ and is labeled "Final Value (steady state value)". An arrow points from below to $v(0^+)$ and is labeled "Initial Value". A bracket to the right of the equation points to the exponent $-t/\tau$ and is labeled "time constant". The variable t in the exponent is red, and τ is blue.

Initial and Final Values

To start with, let's consider a switch. In analyzing the switch, we will consider two extremes:

- ◆ The instant a switch is closed (the **Initial Value**), and
- ◆ the **steady state value** (a long time has passed since the switch closed) (The **Final Value**).



When you have a circuit in which you are working out the initial values,

- An **uncharged capacitor** acts as a **short circuit**.
(It opposes a change in voltage)
- A **un-fluxed inductor** acts as an **open circuit**.
(It opposes a change in current).

Extending this idea to the device with an Initial charge, we get:

$$V_C(0+) = V_o \Leftarrow \text{a voltage source!}$$

$$i_L(0+) = I_o \Leftarrow \text{a current source!}$$

Final Conditions


$$i_c(t \Rightarrow \infty) = 0 \quad \text{Capacitor current} \Rightarrow 0 \quad [\text{open}]$$
$$v_L(t \Rightarrow \infty) = 0 \quad \text{Inductor voltage} \Rightarrow 0 \quad [\text{short}]$$

another way to write these values would be:

$$i_c(\infty) = 0 \quad \text{and} \quad v_L(\infty) = 0$$



RC circuit - Charge Phase

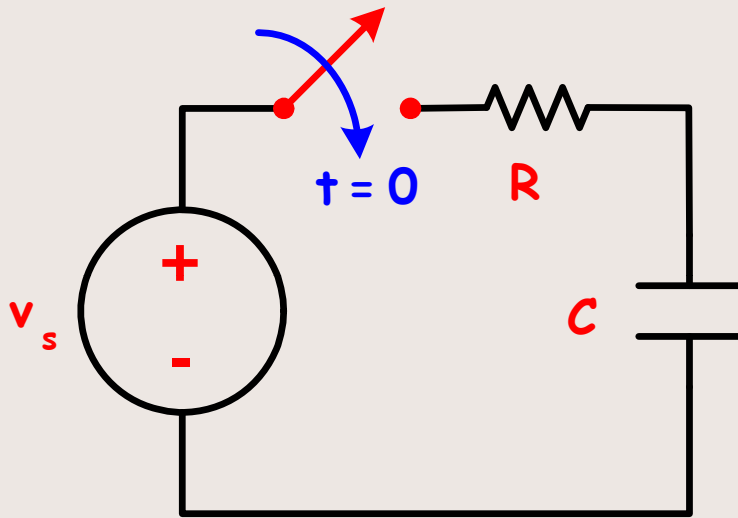

$$\tau = RC$$


$$y = V_c(t)$$

$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-t/\tau}$$

$$\left. \begin{array}{l} y(0^+) = V_c(0^+) = 0v \\ y(\infty) = V_c(\infty) = V_s \end{array} \right\} \begin{array}{l} \text{determined} \\ \text{earlier} \end{array}$$

$$V_c(t) = V_s + [0v - V_s] e^{-t/RC}$$
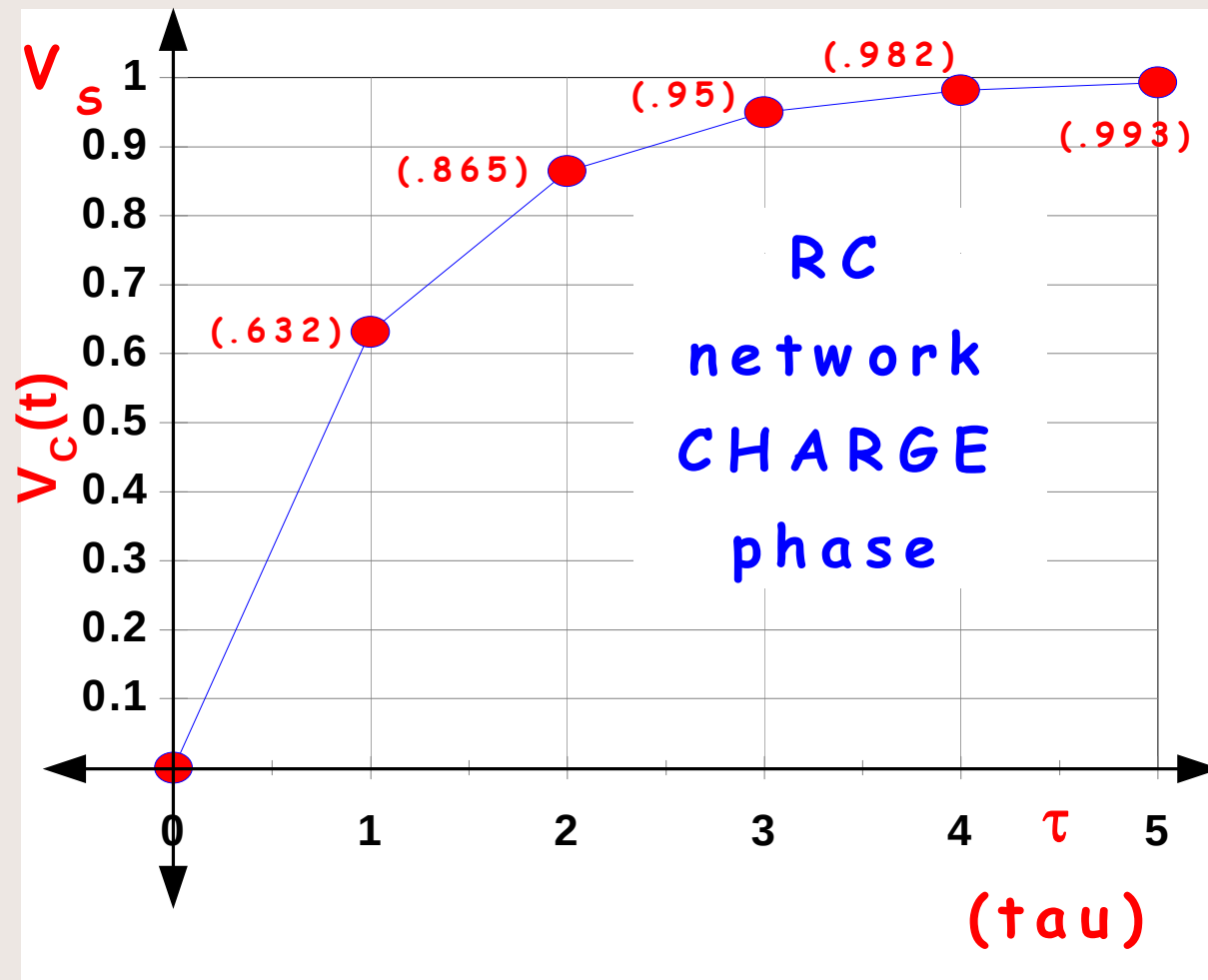
$$V_c(t) = V_s \left(1 - e^{-t/RC} \right)$$



RC Circuit - Discharge Phase


Discharge phase - Voltage

$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-t/\tau}$$


$$V_c(0^+) = V_s \quad V_c(\infty) = 0v$$

Note that it is assumed here that the capacitor had time to completely charge to V_s .
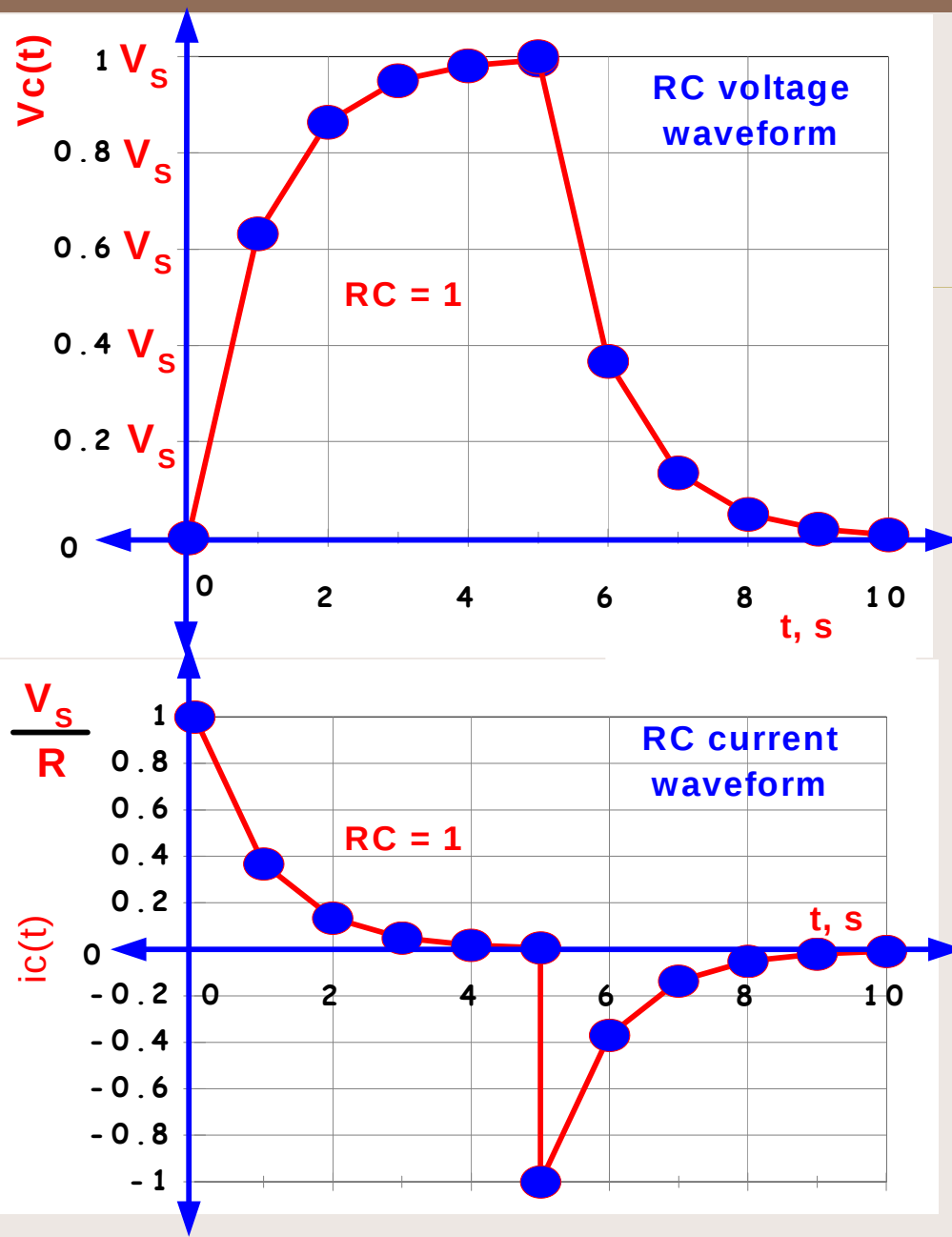
$$V_c(t) = 0v + [V_s - 0v] e^{-t/RC} \Rightarrow V_c(t) = V_s e^{-t/RC}$$





Example

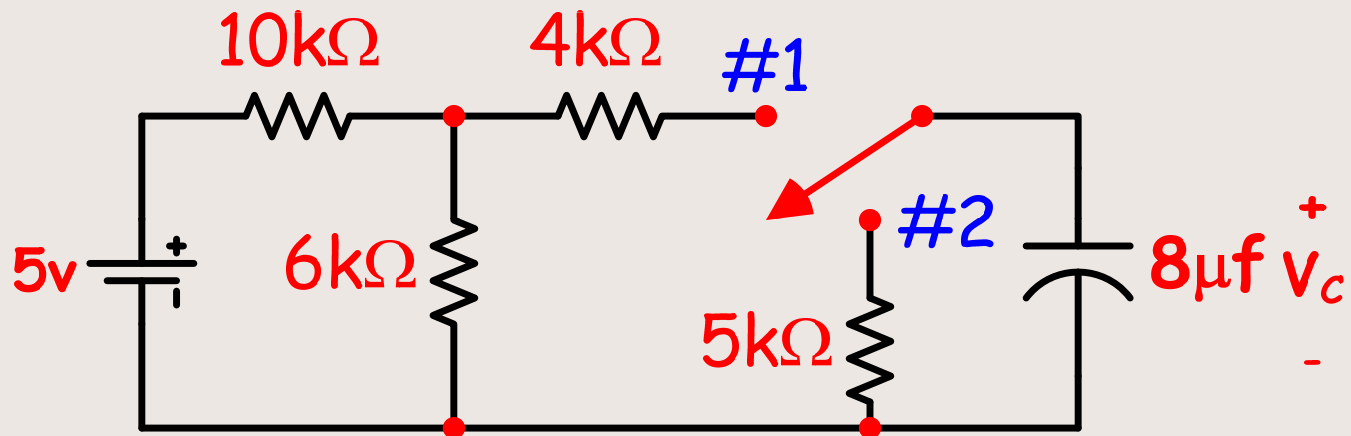


At time $t = 0$ the switch goes to position #1.
The initial charge on the capacitor is 0 volts.
Show the charge graph of the capacitor voltage.

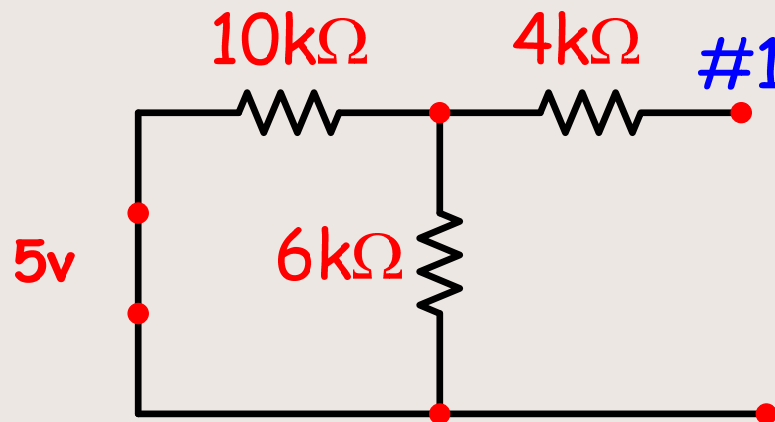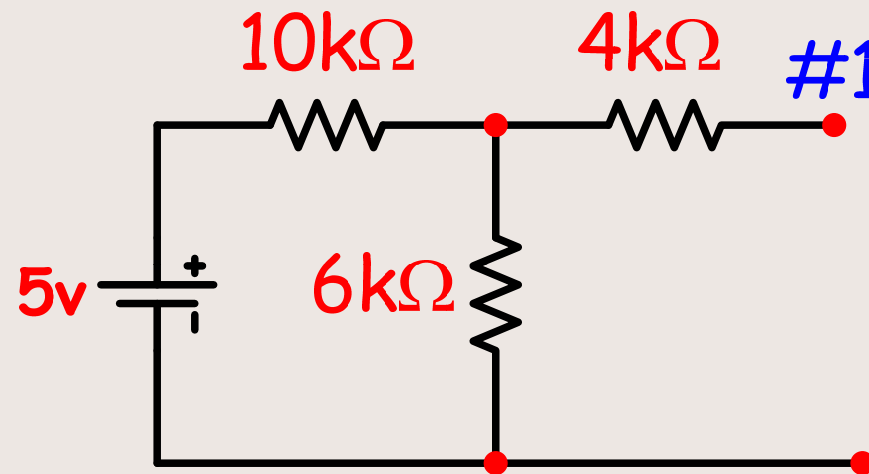Step 1: Remove the load (the capacitor) and the Discharge Resistor and determine the Thevenin Ckt.



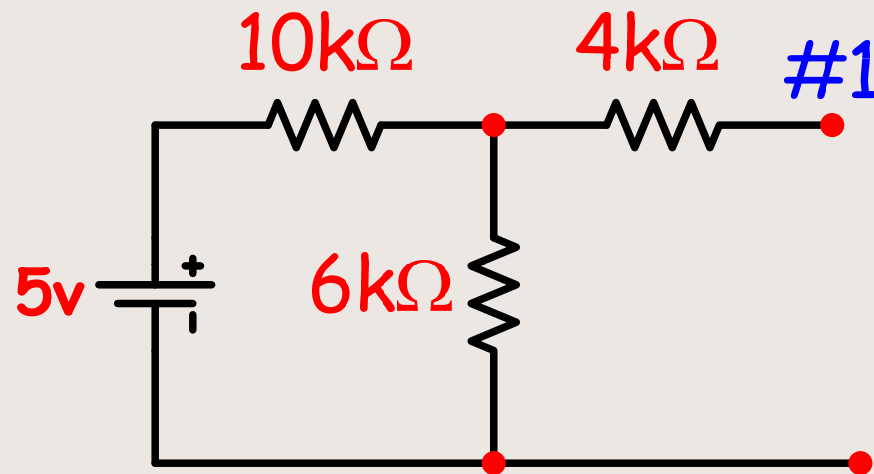
$$\begin{aligned} R_{Th} &= 10k\Omega \parallel 6k\Omega + 4k\Omega \\ &= 3.75k\Omega + 4k\Omega \\ &= \boxed{7.75k\Omega} \end{aligned}$$



$$V_{Th} = \frac{5v (6k\Omega)}{10k\Omega + 6k\Omega} = 1.875v$$

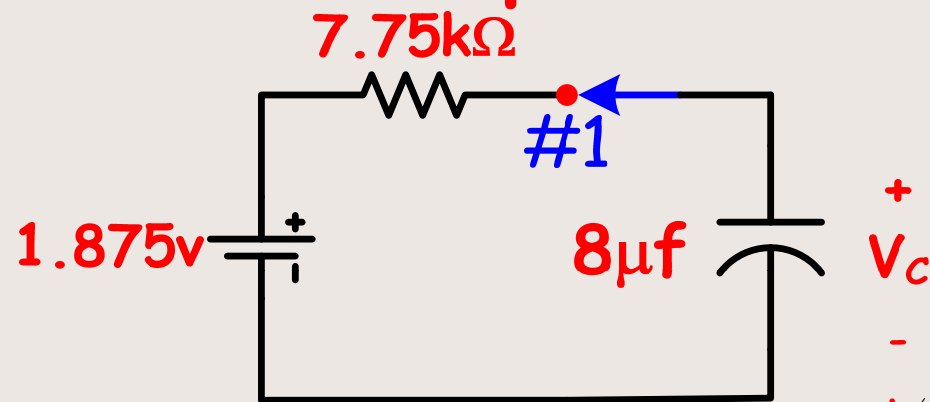Place the Cap onto the Thevenin circuit and then calculate the charge eqn.



$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-t/\tau}$$

$$\tau = RC = 7.75k\Omega (8\mu f) = 62ms$$


$$V_c(0^+) = 0v \quad V_c(\infty) = 1.875v$$

$$V_c(t) = 1.875v + [0v - 1.875v] e^{-t/62ms}$$

$$= 1.875 - 1.875e^{-t/62ms}$$

$$= 1.875 \left(1 - e^{-t/62ms} \right)$$

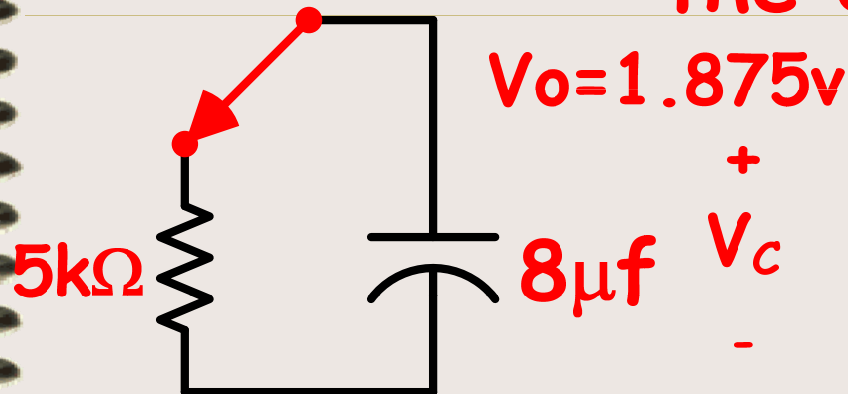Now place the cap with the discharge resistor and recalculate the eqn.



$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-t/\tau}$$

$$\tau = RC = 5k\Omega(8\mu f) = 40ms$$

$$V_c(0^+) = 1.875v \quad V_c(\infty) = 0v$$

$$V_c(t) = 0v + [1.875v - 0v] e^{-t/\tau}$$

$$V_c(t) = 1.875v e^{-t/40ms}$$