

FE Review

AC CIRCUIT ANALYSIS

1

8/25/2010

---

---

---

---

---

---

---

---

AC ANALYSIS

2

Values:

- Peak,
- RMS,
- Effective
- Reactance
- Admittance
- Impedance
- Phasors

- Maximum Power Xfer
- Series
- Parallel
- Series and Parallel Resonance
- Transformers
- Impedance Matching
- Complex Power

8/25/2010

---

---

---

---

---

---

---

---

Peak Values

3

$V(t) = 10 \sin(1kt + 30^\circ)$   
 $V_{\text{peak}} = |V| = 10V$

8/25/2010

---

---

---

---

---

---

---

---

## RMS Values

4

$$i(t) = 5\text{mA} \sin(1kt + 30^\circ)$$

$$I_{\text{peak}} = 5\text{mA}$$

$$I_{\text{rms}} = \frac{5\text{mA} \angle 30^\circ}{\sqrt{2}}$$

$$= 3.536\text{mA} \angle 30^\circ$$

8/25/2010

---

---

---

---

---

---


---

---
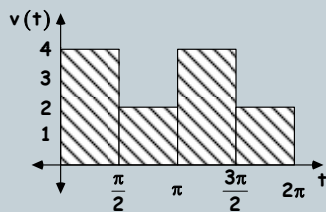
## Example

5

Find the effective value of the voltage for the periodic waveform shown



Example continued on the next slide.

8/25/2010

---

---

---

---

---

---


---

---

## Example (continued)

6

$$\begin{aligned} V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \\ &= \sqrt{\frac{1}{T} \left( \int_0^{T/2} (4)^2 dt + \int_{T/2}^T (2)^2 dt \right)} \\ &= \sqrt{\frac{1}{T} \left( 16t \Big|_0^{T/2} + 4t \Big|_{T/2}^T \right)} \\ &= \sqrt{\frac{1}{T} \left( 16 \left( \frac{T}{2} - 0 \right) + 4 \left( T - \frac{T}{2} \right) \right)} \\ &= \sqrt{\frac{1}{T} (8T + 2T)} = \sqrt{\frac{1}{T} (10T)} = \sqrt{10} = 3.16 \end{aligned}$$

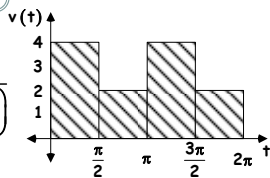

8/25/2010

---

---

---

---

---

---

---

---

## Capacitive and Inductive Reactance

7

$$X_c = \frac{1}{2\pi fC}$$

$$C = 5\mu\text{f} \quad T = 1\text{ms} \therefore f = \frac{1}{T} = \frac{1}{1\text{ms}} = 1\text{kHz}$$

$$X_c = \frac{1}{2\pi(1\text{kHz})(5\mu\text{f})} = 31.83\Omega$$

$$X_L = 2\pi fL$$

$$L = 2\text{mH}$$

$$X_L = 2\pi(1\text{kHz})(2\text{mH}) = 12.57\Omega$$

8/25/2010

---

---

---

---

---

---

---

---

## Conductance and Admittance

8

$$\text{Conductance} = G = \frac{1}{R} = \frac{1}{10\Omega} = 100\text{mS}$$

$$\text{Admittance} = Y = \frac{1}{X}$$

$$Y_L = \frac{1}{X_L} = \frac{1}{j12.57\Omega} = -j79.55\text{mS}$$

$$Y_c = \frac{1}{X_c} = \frac{1}{-j31.83\Omega} = j31.42\text{mS}$$

8/25/2010

---

---

---

---

---


---

---

---

## Impedance (Z)

9

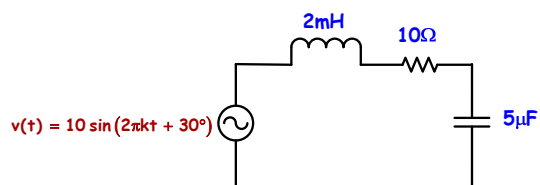

$$Z_T = R + jX_L - jX_c$$

8/25/2010

---

---

---

---

---

---


---

---

## AC Circuit (Phasor Domain) Example

10

Analyze the following series AC circuit

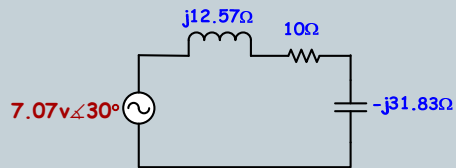

Example continued on the next slide.

8/25/2010

---

---

---

---

---


---

---

---

## Example (continued)

11

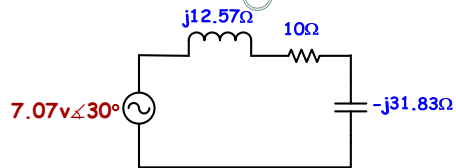

$$\begin{aligned} Z_T &= R + jX_L - jX_C \\ &= 10 + j12.57\Omega - j31.83\Omega \\ &= 10 - j19.26\Omega \\ &= 21.7\angle -62.56^\circ \end{aligned}$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

## Example (continued)

12

$$\begin{aligned} I_T &= \frac{V_T}{Z_T} = \frac{7.07V\angle 30^\circ}{21.7\angle -62.56^\circ} = 325mA\angle 92.56^\circ \\ V_C &= \frac{V_T X_C}{Z_T} = \frac{7.07V\angle 30^\circ (31.83\angle -90^\circ)}{21.7\angle -62.56^\circ} \\ &= \frac{225.0\angle -60^\circ}{21.7\angle -62.56^\circ} = 10.37\angle 2.56^\circ \end{aligned}$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---


---

---
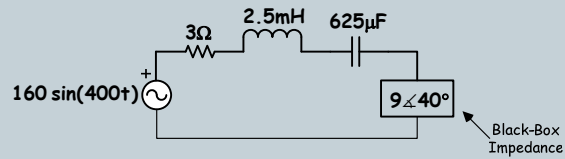
### Example

13

Analyze the following series AC circuit.  
Note the use of a "Black Box".



Example continued  
on the next slide.

8/25/2010

---

---

---

---

---


---

---

---

### Example (continued)

14

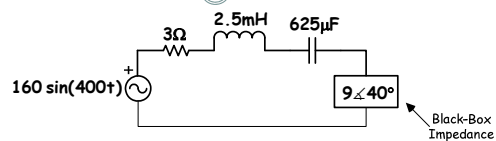

$$X_L = \omega L = 400(2.5\text{mH}) = 1\Omega \quad (Z_L = 1\Omega \angle 90^\circ)$$

$$X_C = \frac{1}{\omega C} = \frac{1}{400(625\mu\text{F})} = 4\Omega \quad (Z_C = 4\Omega \angle -90^\circ)$$

$$Z_T = 3 + j1 - j4 + 9 \angle 40^\circ$$

$$= 3 - j3 + 6.89 + j5.785$$

$$= 9.89 + j2.785 = 10.275\Omega \angle 15.727^\circ$$

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---


---

---

---

### Example (continued)

15

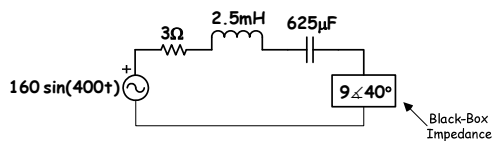

$$\bar{V} = 160 \angle 0^\circ \text{V}$$

$$\bar{I} = \frac{\bar{V}}{Z_T} = \frac{160 \angle 0^\circ \text{V}}{10.275 \angle 15.727^\circ} = 15.725 \text{A} \angle -15.725^\circ$$

$$i(t) = 15.725 \text{A} \sin(400t - 15.725^\circ)$$

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

16

$$\bar{V} = 160V \angle 0^\circ$$

$$\bar{I} = 15.725A \angle -15.725^\circ$$

$$Z_T = 10.275\Omega \angle 15.727^\circ = 9.89\Omega + j2.785\Omega$$

The Circuit is **INDUCTIVE** in Nature

**ELI** the **ICE** person

**ELI** => In an **Inductive** circuit, **E** leads **I**

**ICE** => In a **Capacitive** circuit, **I** leads **E**

The current lags the voltage in this circuit

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

17

The voltage across the inductor is:

$$V_L = IZ_L$$

$$= 15.725A \angle -15.725^\circ (1 \angle 90^\circ)$$

$$= 15.725V \angle 74.275^\circ$$

8/25/2010

---

---

---

---

---

---


---

---

### Parallel Example

18

Find the  $Z_T$  of the circuit shown

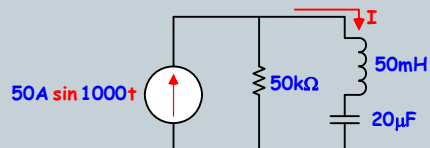

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---


---

---

---

## Parallel Example (continued)

19

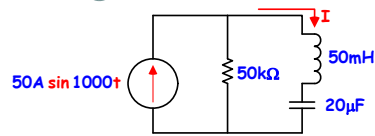

$$X_L = \omega L = 1000(50\text{mH}) = 50\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000(20\mu\text{F})} = 50\Omega$$

$$Z_L + Z_C = j50 + -j50 = \boxed{0\Omega} \leftarrow !!! \text{ Example continued on the next slide.}$$

8/25/2010

---

---

---

---

---


---

---

---

## Parallel Example (continued)

20

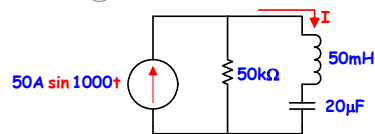

So, that leg is shorting out the other leg so the total impedance of the circuit is equal to 0.

A side note: Since the LC leg is shorting out the other leg then ALL the current is going thru it as well.

8/25/2010

---

---

---

---

---

---


---

---
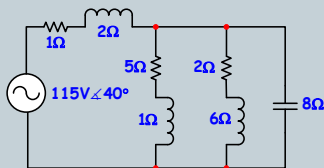
## Example

21

Find the total impedance and average power dissipated in the circuit shown



Example continued on the next slide.

8/25/2010

---

---

---

---

---


---

---

---

## Example (continued)

22

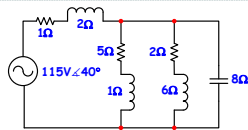

$$\begin{aligned} Z_T &= (1 + j2) + [(5 + j1) \parallel (2 + j6) \parallel (-j8)] \\ &= (1 + j2) + \left[ \frac{1}{\frac{1}{(5 + j1)} + \frac{1}{(2 + j6)} + \frac{1}{-j8}} \right] \\ &= 1 + j2 + 3.8621 + j1.0115 \\ &= 4.862 + j3.012 = \boxed{5.7192 \angle 31.773^\circ} \end{aligned}$$

Example continued on the next slide.

8/25/2010

## Example (continued)

23


$$\begin{aligned} Z_T &= 4.862 + j3.012 = 5.72 \angle 31.77^\circ \\ V &= 115V \angle 40^\circ \text{ assumed to be RMS} \\ I &= \frac{V}{Z_T} = \frac{115V \angle 40^\circ}{5.72 \angle 31.77^\circ} = 20.1 \angle 8.23^\circ \text{ Arms} \\ P_{avg} &= V_{rms} I_{rms} \cos \theta \\ &= (115V)(20.1) \cos 31.77^\circ = \boxed{1.965kW} \end{aligned}$$

8/25/2010
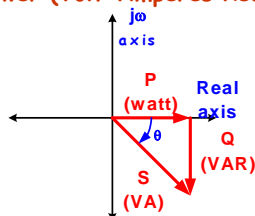
## Power Triangle (Complex Power)

24

- True Power (Watts)
- Apparent Power (Volt-Amperes) or (VA)
- Reactive Power (Volt-Amperes Reactive) or (VARs)




8/25/2010


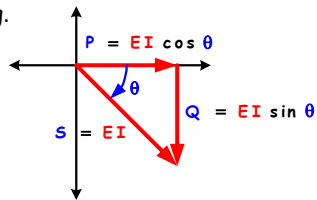
### Power Factor Angle

25

- The power factor angle ( $\theta$ ) goes **FROM** True Power **TO** the Apparent Power
- The magnitudes of the three powers can be found using Trig.



8/25/2010

---

---

---

---

---

---

---

### Effective Values **NOT** Peak Values

26

**The title says it all. Convert from Peak to effective before you do anything!!!!!!**

8/25/2010

---

---

---

---

---

---

---

### Power Factor Calculation

27

$$F_p = \cos(\theta) = \frac{P}{S}$$

8/25/2010

---

---

---

---

---


---

---
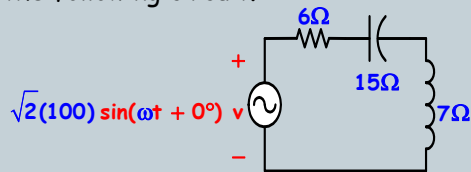
### Example

28

Find the Power Triangle for the following circuit.



Example continued on the next slide.

8/25/2010

---

---

---

---

---

---


---

---
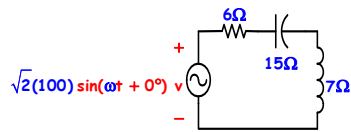
### Example (continued)

29

The example was kind enough to Represent peak voltage with a Square root of 2 showing!



$$E_{rms} = \frac{e(t)}{\sqrt{2}} = \frac{\sqrt{2}(100v)}{\sqrt{2}} = 100v$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---


---

---

---

### Example (continued)

30

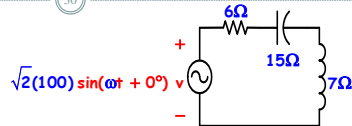

$$E_{rms} = 100v$$

$$Z_T = 6 - j15 + j7 = 6 - j8 = 10\Omega \angle -53.13^\circ$$

$$I = \frac{E}{Z_T} = \frac{100v}{10\Omega \angle -53.13^\circ} = 10A \angle 53.13^\circ$$

Example continued on the next slide.

8/25/2010

---

---

---

---


---

---

---

---

### Example (continued)

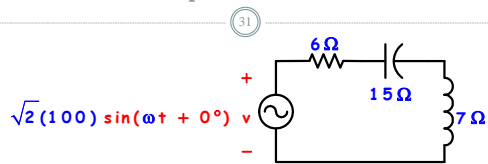

$$V_R = IR = (10A \angle 53.13^\circ) 6\Omega = 60V \angle 53.13^\circ$$


$$V_C = IX_C = (10A \angle 53.13^\circ) (15\Omega \angle -90^\circ) = 150V \angle -36.87^\circ$$

$$V_L = IX_L = (10A \angle 53.13^\circ) (7\Omega \angle 90^\circ) = 70V \angle 143.13^\circ$$

Example continued  
on the next slide.

8/25/2010

### Example (continued)

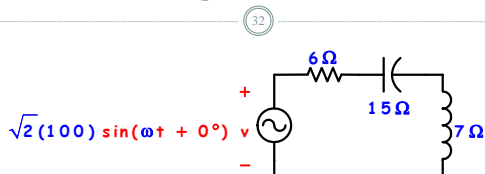

Note that since the capacitive reactance of the circuit is greater than the inductive reactance, the **Power factor** of this circuit will be **LEADING**.

Example continued  
on the next slide.

8/25/2010

### Example (continued)

33

Note that since the capacitive reactance of the circuit is greater than the inductive reactance, the **Power factor** of this circuit will be **LEADING**.

ELI the ICE person:

**Inductive** circuits, **voltage LEADS** current.

**Capacitive** circuits, **current LEADS** voltage.

**POWER FACTOR is a CURRENT relationship!**

Example continued  
on the next slide.

8/25/2010

### Example (continued)

34

$$\begin{aligned}\text{Power Factor} &= F_p = \cos(\theta) \\ &= \cos(53.13^\circ) = \boxed{600\text{m LEADING}} \\ \text{Total Apparent Power} &= S_T = EI \\ &= 100\text{V}(10\text{A}) = \boxed{1000\text{ VA}} \\ \text{Total Reactive Power} &= Q_T = S \sin(53.13^\circ) \\ &= (1000\text{ VA})(800\text{m}) = \boxed{800\text{ VAR}}\end{aligned}$$

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

35

$$\begin{aligned}\text{Power Factor} &= \boxed{600\text{m LEADING}} \\ \text{Total Apparent Power} &= \boxed{1000\text{ VA}} \\ \text{Total Reactive Power} &= \boxed{800\text{ VAR}} \\ \text{Total True Power} &= P_T = S \cos(53.13^\circ) \\ &= (1000\text{ VA})(600\text{m}) = \boxed{600\text{ Watt}} \\ \text{Power Factor} &= F_p = \frac{P}{S} = \frac{600}{1000} = \boxed{600\text{m LEADING}} \\ &\text{(Note that this is the same as earlier found)}\end{aligned}$$

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---


---

---

---

### Example (continued)

36

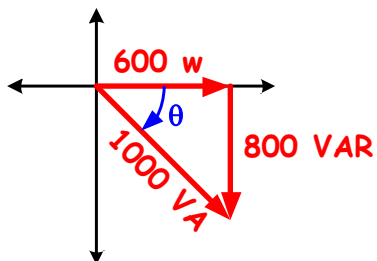

8/25/2010

---

---

---

---

---

---

---

---

## Power Factor Correction

37

The power company has very big interest in insuring that power supplied is available at peak efficiency. This implies that the current must be as low as possible. Thus, **Apparent Power (S)** should be as low as possible since the smaller the reactive power, the closer the apparent power will match true power.

$$S_T = EI_T = \sqrt{P_T^2 + Q_T^2}$$

8/25/2010

---

---

---

---

---

---

---

---

## Example

38

A **5 hp** motor with a **0.6 lagging** power factor with an efficiency of 92% is connected to a **208-V, 60 hz** supply. Find the **Power Triangle**.

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

## Example (continued)

39

- 5 hp motor
- 0.6 **lagging** power factor
- efficiency = 92%
- 208-V, 60 hz supply.

Most MOTORS (but not all) are inductive in nature. Since the **power factor is lagging**, this motor must be **inductive**!

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

40

- 5 hp motor
- 0.6 **lagging** power factor
- efficiency = 92%
- 208-V, 60 hz supply.

$$1\text{hp} = 746\text{W}$$

$$P_o = 5\text{hp} = 5(746\text{W}) = 3730\text{ W}$$

$$P_{in} = \frac{P_o}{\eta} = \frac{3730}{.92} = 4054.348\text{ W}$$

$$F_p = \cos(\theta) = .6 \text{ so } \theta = \cos^{-1}(.6) = 53.13^\circ$$

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)


41

Since it was lagging, it was inductive,

Since  $P = S \cos(\theta)$  then

$$S = \frac{P}{\cos(\theta)} = \frac{4054.348\text{W}}{.6} = 6757.246\text{ VA}$$
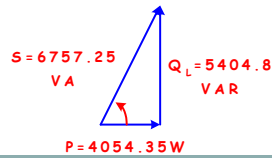
$$Q = S \sin(\theta) = 6757.246\text{VA} \sin(53.13) = 5405.79\text{ VAR}$$



8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

42

Now that a Power Triangle has been found, we need to insert the required component in the circuit which will counteract the amount of reactive power to reduce the difference between the apparent and true power. Since the circuit is inductive in nature we need to add in a capacitance to the problem.

Example continued  
on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

43

A net unity power factor level is needed by introducing a **capacitive reactive power level of 5405.8 VARs** to balance  $Q_L$ . Find the required  $C$ .

$$Q_c = \frac{V^2}{X_c} \text{ so}$$

$$X_c = \frac{V^2}{Q_c} = \frac{(208V)^2}{5405.8\text{VAR}} = 8\Omega$$

$$C = \frac{1}{2\pi f X_c} = \frac{1}{2\pi (60)(8\Omega)} = 331.6\mu\text{F}$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

44

At **0.6F<sub>p</sub>** (before correction)

$$S = VI = 6757.25 \text{ VA}$$

$$\text{and } I = \frac{S}{V} = \frac{6757.25 \text{ VA}}{208V} = 32.49 \text{ A}$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

45

At **Unity F<sub>p</sub>** (after correction)

$$S = VI = 4054.35 \text{ VA}$$

$$\text{and } I = \frac{S}{V} = \frac{4054.35 \text{ VA}}{208V} = 19.49 \text{ A}$$

$$\frac{32.49\text{A} - 19.49 \text{ A}}{32.49\text{A}} * 100\%$$

$$= 40\% \text{ reduction in current}$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

46

In the motor (**before correction**), the current lagged the voltage by 53.13 degrees and the true power was 4054.35W

$$I_m = \frac{P}{E \cos(\theta)} = \frac{4054.35}{(208V)(.6)} = 32.49A$$

which gives us  $I_m = 32.49A \angle -53.13^\circ$

Therefore,

$$Z_m = \frac{E}{I_m} = \frac{208V \angle 0^\circ}{32.49A \angle -53.13^\circ} = 6.4 \angle 53.13^\circ = 3.84\Omega + j5.122\Omega$$

In parallel, it would be

$$Y = \frac{1}{6.4 \angle 53.13^\circ} = .094S - j.125S = \frac{1}{10.64\Omega} + \frac{1}{j8\Omega}$$


Example continued on the next slide.

8/25/2010

### Example (continued)

47

Motor (**before correction**)

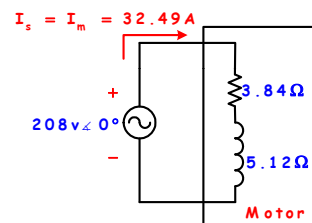


Example continued on the next slide.

8/25/2010
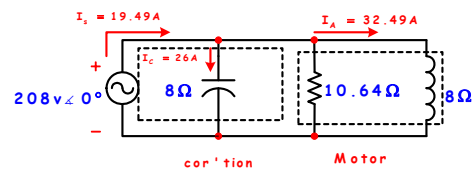
### Example (continued)

48

Earlier we calculated the parallel values of the motor and even earlier we found that the required additional C reactance 8 ohms.




Example continued on the next slide.

8/25/2010



### Example (continued)

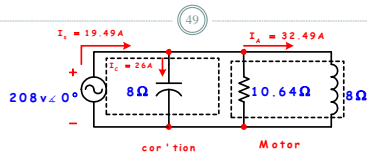

Since

$$Y_T = \frac{1}{-jX_C} + \frac{1}{R} + \frac{1}{+jX_L} = \frac{1}{R}$$

$$|I_s| = EY_T = E\left(\frac{1}{R}\right) = 208V\left(\frac{1}{10.64}\right) = 19.54A$$

$$|I_C| = \frac{E}{X_C} = \frac{208V}{8\Omega} = 26A$$

8/25/2010


### Resonant Circuits

A resonant circuit has a zero degree current phase angle difference. This is the same thing as saying that the circuit is purely resistive (the power factor is equal to '1')

In order for this to occur, the inductive and the Capacitive reactance's must cancel each other out.

8/25/2010

### Resonant Circuits

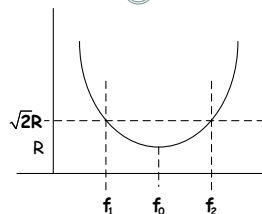


As a circuit approaches resonance, there are two points called the half-power points (where the power is dissipated in the resistor). The frequency difference between the half power points is the BW.

8/25/2010

## Resonant Circuits

52

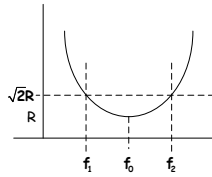

$$BW = f_2 - f_1$$

$$\text{Resonant Freq} = f_0$$

8/25/2010

---

---

---

---

---

---

---

---

## Quality Factor (Q)

53

The quality factor,  $Q$ , for a resonant circuit is a dimensionless value which compares reactive energy stored in the reactive elements to the resistive energy dissipated.

$$Q = \frac{f_0}{BW} = \frac{X_T}{R}$$

8/25/2010

---

---

---

---

---

---

---

---

## Series Resonant Circuits

54

Impedance is at a minimum  
Impedance equals  $R$   
Current and Voltage are in phase  
Current is maximum  
Power dissipation is maximum

8/25/2010

---

---

---

---


---

---

---

---

### Series Resonant Circuit Example

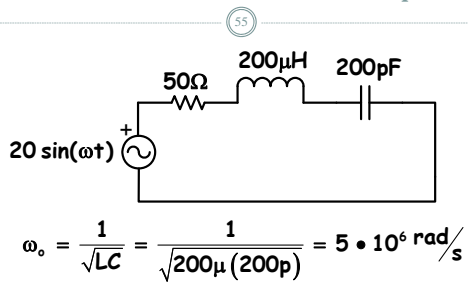

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

56

half - power points are:

$$\omega_0 \pm \frac{R}{2L} = 5M \pm \frac{50\Omega}{2(200\mu H)}$$

$$= 5.125M \text{ rad/s} \text{ and } 4.875M \text{ rad/s}$$

The total circuit Z is just the resistance at resonance.

The resonant current is:

$$I_0 = \frac{V}{Z_0} = \frac{V}{R} = \frac{20\angle 0^\circ}{50\Omega} = 400mA\angle 0^\circ$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---

---

### Example (continued)

57

The voltages across the elements are:

$$V_R = I_0 R = 400mA(50\Omega) = 20V\angle 0^\circ$$

$$V_L = I_0 X_L = 400mA(\omega_0)200\mu H$$

$$= j400mA(5M \text{ rad/s})200\mu H$$

$$= 400\Omega\angle 90^\circ$$

$$V_C = I_0 X_C = 400mA\left(\frac{-j}{400mA(5M \text{ rad/s})200pF}\right)$$

$$= 400\Omega\angle -90^\circ$$

Example continued on the next slide.

8/25/2010

---

---

---

---

---

---

---


---

### Example (continued)

58

What  $C$  value is needed for the circuit to have a Power Factor = 1?

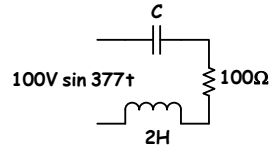Power factor = 1 at  
Circuit resonance so,



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{(\omega_0)^2 L} = \frac{1}{(377)^2 2H} = 3.5\mu F$$

8/25/2010

---

---

---

---

---

---

---

---

### Parallel Resonant Circuits

59

Same as Series Resonant Circuits except that:  
Current is at a minimum and  
Power Dissipated is at a minimum.

At resonance:

$$X_L = X_C$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 RC = \frac{R}{\omega_0 L} = R \sqrt{\frac{C}{L}}$$

8/25/2010

---

---

---

---

---

---


---

---
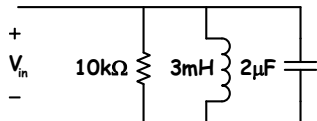
### Parallel Resonance Example

60

Calculate the resonant freq and the  $Q$  for  
the circuit below



Example continued  
on the next slide.

8/25/2010

---

---

---

---

---

---


---

---
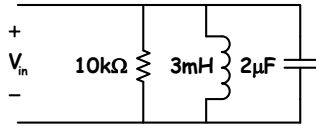
### Example (continued)

61

Calculate the resonant freq and the Q for the circuit below.



$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(3\text{mH})(2\mu\text{F})}} = \frac{1}{\sqrt{6 \cdot 10^{-9}}} = 12.9\text{k rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{10 \cdot 10^3}{12.9 \cdot 10^3 \text{ rad/s} (3 \cdot 10^{-3} \text{H})} = 258.4$$

8/25/2010

---

---

---

---

---

---

---

---

### AC Maximum Power Transfer

62

In DC circuits, in order for the Maximum power to be transferred to the load,  $R_{\text{load}} = R_{\text{Thevenin}}$ .

In AC circuits, the requirement is slightly different.

In order for the maximum power to be transferred to the load:

$$R_{\text{load}} = R_{\text{Thev}}$$

$$X_{\text{load}} = -X_{\text{Thev}}$$

8/25/2010

---

---

---

---

---

---

---

---