AC Circuits

Using Complex Numbers

Algebra of Complex Numbers

Complex numbers may be designated in Rectangular form, Polar form, or exponential form.

- **Rectangular form**, a complex number is written in terms of its <u>real</u> and <u>imaginary</u> components:
 - $Z = R \pm jX, \text{ where}$ R = Real component of the number X = Imaginary component of the number $j = \sqrt{-1} \quad (\text{Engineering form})$ or $i = \sqrt{-1} \quad (\text{Math and Physics form})$
- Polar form, a complex number is written in terms of a phasors <u>magnitude</u> and its <u>phase</u> angle:

 $\overline{Z} = A \measuredangle \theta, \text{ where}$ $A = \sqrt{R^2 + X^2} \quad (\text{also known as modulus of } Z)$ $\theta = \tan^{-1} \left(\frac{\text{Imaginary}}{\text{Real}} \right) = \tan^{-1} \left(\frac{X}{R} \right)$ Real = $A \cos \theta$ Imaginary = $A \sin \theta$

• Exponential form is another way to represent polar form numbers: $A \measuredangle \theta \Rightarrow A e^{j\theta}$

Complex numbers are added and subtracted in rectangular form.

 $\begin{array}{rcl} \text{if} & & & \\ & Z_1 & = & R_1 + jX_1 & = & A_1\left(\cos\theta_1 + j\sin\theta_1\right) = A_1 \measuredangle \theta_1 \\ & Z_2 & = & R_2 + jX_2 & = & A_2\left(\cos\theta_2 + j\sin\theta_2\right) = A_2 \measuredangle \theta_2 \\ \text{then} & & \\ & Z_1 + Z_2 & = & \left(R_1 + R_2\right) + j\left(X_1 + X_2\right) \\ & Z_1 - Z_2 & = & \left(R_1 - R_2\right) + j\left(X_1 - X_2\right) \\ \end{array}$

While complex numbers are multiplied and divided in polar form.

$$Z_{1} \bullet Z_{2} = (A_{1} \bullet A_{2}) \measuredangle (\theta_{1} + \theta_{2})$$
$$\frac{Z_{1}}{Z_{2}} = \left(\frac{A_{1}}{A_{2}}\right) \measuredangle (\theta_{1} - \theta_{2})$$

FE Review Tes	AC Circuits	
9/10/2011		PAGE - 2
	Complex Number Examples	
Problem 1:	Express 18∡33.7° in rectangular form .	
	$= 18 \cos 33.7^{\circ} + j18 \sin 33.7^{\circ} = 14.98 + j9.987$	
Problem 2:	Express 14 + j20 in polar form.	
	$= \sqrt{14^2 + 20^2} \tan^{-1}\left(\frac{20}{14}\right) = \boxed{24.41 \measuredangle 55.01^{\circ}} \left[\text{quadrant 1}\right]$	
Problem 3:	Express 48 X – 45° in rectangular form.	
	= 48 cos 45° + j48 sin 45° = $33.94 - j33.94$ [Quadrant 4]	
Problem 4:	Perform: $(22\measuredangle - 40^\circ) \bullet (11\measuredangle - 60^\circ)$	
	$= (22 \bullet 11) \measuredangle (-40^\circ + -60^\circ) = \boxed{242\measuredangle - 100^\circ}$	
Problem 5:	Perform: (22 + j9) - (-11 + j6)	
	$= \left[22 - \left(-11\right)\right] + j\left[9 - 6\right] = \boxed{33 + j3}$	
	18 + j4	
Problem 6:	Perform: $6 - j8$	
_	$\sqrt{18^2 + 4^2} \measuredangle \tan^{-1}\left(\frac{4}{18}\right) \left[\text{quadrant } 1 \right]$	
_	$\sqrt{6^2 + 8^2} \measuredangle \tan^{-1} \left(\frac{-8}{6} \right) \left[\text{quadrant 4} \right]$	
=	$\frac{18.44 \measuredangle 12.53^{\circ}}{10 \measuredangle -53.13^{\circ}} = \frac{18.44}{10} \measuredangle (12.53^{\circ} - (-53.13^{\circ})) = 1.844 \measuredangle 65.66^{\circ}$	
Problem 7:	Perform the following with the result in polar format : $48 \measuredangle 60^\circ + 80 \measuredangle - 135^\circ$ $48 \measuredangle 60^\circ + 80 \measuredangle - 135^\circ$	
	48 cos 60 + j48 sin 60 + 80 cos (-135) + j80 sin (-135)	
	24 + j41.57 + (-56.57) + j(-56.57)	
	= 24 - 56.57 + j(41.57 - 56.57)	
	= -32.57 - j15 = $\sqrt{32.57^2 + 15^2} \tan^{-1}\left(\frac{-15}{-32.57}\right)$	
	quadrant 3 = 35.86 $(24.73 - 180) = 35.86 (-155.3^{\circ})$	

AC Circuits

PAGE - 3

Phasor Transforms of Sinusoids

$$V_{peak} \cos(\omega t + \theta) = \frac{V_{peak}}{\sqrt{2}} \measuredangle \theta = \overline{V}$$

 $I_{peak} \cos(\omega t + \theta) = \frac{I_{peak}}{\sqrt{2}} \measuredangle \theta = \overline{I}$

Problem 8: Express $v = 212 \sin(\omega t + 45^{\circ}) V$ in phasor notation.

$$v = 212 \sin(\omega t + 45^{\circ}) V = 212 \cos(\omega t + 45^{\circ} - 90^{\circ}) V$$

= 212 cos(\omega t - 45^{\circ}) V
$$\overline{v} = \frac{212}{\sqrt{2}} \measuredangle - 45^{\circ} = \boxed{149.9 \measuredangle - 45^{\circ} V}$$

Problem 9: Express $v = 141.4 \cos(\omega t - 90^{\circ}) V$ in phasor notation.

$$\mathbf{v} = \mathbf{141.4} \cos \left(\mathbf{\omega t} - \mathbf{90^{\circ}} \right) \mathbf{V}$$
$$\frac{1}{\mathbf{v}} = \frac{\mathbf{141.4}}{\sqrt{2}} \measuredangle - \mathbf{90^{\circ}} = \boxed{\mathbf{99.98} \measuredangle - \mathbf{90^{\circ}V}}$$

Problem 10: Express $v = 38 \cos(\omega t + 15^{\circ}) V$ in phasor notation.

$$\mathbf{v} = \mathbf{38} \cos\left(\mathbf{\omega t} + \mathbf{15^{\circ}}\right) \mathbf{V}$$
$$\frac{-}{\mathbf{v}} = \frac{\mathbf{38}}{\sqrt{2}} \measuredangle \mathbf{15^{\circ}} = \mathbf{26.87} \measuredangle \mathbf{15^{\circ}V}$$

Problem 11: Express $v = 24 \measuredangle 60^{\circ}V$ as a sinusoid.

$$\mathbf{v} = \left(\sqrt{2} \cdot 24\right) \cos\left(\omega t + 60^{\circ}\right) \mathbf{V}$$
$$\mathbf{v} = \left[\mathbf{33.94} \cos\left(\omega t + 60^{\circ}\right) \mathbf{V}\right]$$

Problem 12: Express $v = 10 \measuredangle - 45^{\circ}V$ as a sinusoid.

$$\mathbf{v} = \left(\sqrt{2} \cdot 10\right) \cos\left(\omega t - 45^{\circ}\right) \mathbf{V}$$
$$\mathbf{v} = \left[\mathbf{14.144} \cos\left(\omega t - 45^{\circ}\right) \mathbf{V}\right]$$





FE Review Test Masters	AC Circuits		
9/10/2011			PAGE - 5
(2) Even though RESISTANCE and	REACTANCE ar	e both measured in OHA	NS, you can't just
add them together to get impec	dance!		
IMPEDANCE ≠ RESIS	STANCE + REA	ACTANCE	
a. This is because RESIST .	ANCE is a REAL	# and REACTANCE is a	an IMAGINARY # .
Together they make up a	a COMPLEX #.		
Z _{magnitude} = R	+ $j(X_L - X_c) =$	$= \sqrt{\mathbf{R}^2 + \left(\mathbf{X}_{L} - \mathbf{X}_{\mathcal{C}}\right)^2}$	
Z _R = R ///	Z _L = +jX _L	$Z_{c} = -jX_{c}$	
10Ω	10Ω	10Ω	
10Ω	+j10Ω	-j10Ω	
(3) CAPACITORS and INDUCTORS voltage: a. The phase of the impeda b. The phase of the impeda	5 affect the pha ance of a capacit ance of an i nduct	se relationship between or is -90 degrees or is +90 degrees	current and
sine $V(r)$ $I(r)$ $V(r)$ $V(r)$ A B C D	Ţ	$X_{1} = Z$ $R + jX = Z \neq \Theta R - j$	$\frac{1}{2} = \frac{1}{2} - \frac{1}{2}$

FIGURE 1

FIGURE 3

E_A 100 V

995 Hz

R = 30Ω

ر 4µF



PROBLEMS:

1. Given the following **RLC** circuits, express the impedance of the circuit in both **rectangular** and **polar form**.



2. Express the **resistance** or the **reactance** for the following elements in **rectangular and in polar form**:



AC Circuits

PROBLEMS:

Example 1: A series circuit of R = 10 ohms and C = 40μ F has an applied voltage of: $v(t) = 500 \cos(2500t - 20^\circ)$. Find the current i(t).

$$\begin{split} X_{c} &= \frac{1}{\omega C} = \frac{1}{2500 (40 \mu f)} = 10\Omega \\ \overline{Z} &= R - jXc \\ &= 10 - j10 = 14.14\measuredangle - 45^{\circ} \\ \overline{V} &= \frac{V_{p}}{\sqrt{2}} = \frac{500}{\sqrt{2}} = 353.6v\measuredangle - 20^{\circ} \\ \overline{I} &= \frac{\overline{V}}{\overline{Z}} = \frac{353.6v\measuredangle - 20^{\circ}}{14.14\measuredangle - 45^{\circ}} = 25A\measuredangle 25^{\circ} \\ i(t) &= 25A\cos(2500t + 25^{\circ}) \\ &\qquad \left(\begin{array}{c} \text{Current is LEADING Voltage as would be} \\ &= \text{expected in a Capacitive circuit} \end{array} \right) \end{split}$$

Example 2:

(a) For the parallel circuit shown below, find the branch currents and the total current.

(b) Find
$$Z_{eq}$$
 from $\sqrt[V]{I}$ and compare with the result of $\binom{(Z_1Z_2)}{(Z_1 + Z_2)}$

$$\mathbf{I}_{1} \bigvee_{AC} 3\Omega \qquad \qquad \mathbf{I}_{1} = \frac{V}{Z_{1}} = \frac{50 \measuredangle 0^{\circ}}{3 - j4} = \frac{50 \measuredangle 0^{\circ}}{5 \measuredangle - 53.13^{\circ}} = 104 \measuredangle 53.13^{\circ}$$
$$\mathbf{I}_{2} = \frac{V}{Z_{2}} = \frac{50 \measuredangle 0^{\circ}}{10} = 54 \measuredangle 0^{\circ}$$
$$\mathbf{By} \ \mathbf{KCL}$$
$$\mathbf{0} = -\mathbf{I}_{T} + \mathbf{I}_{1} + \mathbf{I}_{2}$$
$$\mathbf{I}_{T} = \mathbf{I}_{1} + \mathbf{I}_{2} = 104 \measuredangle 53.13^{\circ} + 54 \measuredangle 0^{\circ}$$
$$= 6 + j8 + 5 = 11 + j8 = 13.64 \measuredangle 36^{\circ}$$

$$Z_{T} = \frac{V_{T}}{I_{T}} = \frac{50V \measuredangle 0^{\circ}}{13.6A \measuredangle 36^{\circ}} = \boxed{3.676\Omega \measuredangle - 36^{\circ}}$$
$$Z_{T} = Z_{1} \mid \mid Z_{2}$$
$$= \frac{(5\measuredangle - 53.13^{\circ})(10\measuredangle 0^{\circ})}{3 - j4 + 10} = \frac{50\measuredangle - 53.13^{\circ}}{13.6\measuredangle - 17.1^{\circ}} = \boxed{3.676\Omega \measuredangle - 36^{\circ}}$$

FE Review || Test Masters

AC Circuits



9/10/2011

Example 3: For the series-parallel circuit shown below, find the current in each element.



$$\begin{aligned} Z_{T} &= 10\Omega + \frac{5\Omega(j10\Omega)}{5\Omega + j10\Omega} \\ &= 10\Omega + \frac{50\Omega\measuredangle90^{\circ}}{11.18\measuredangle63.43^{\circ}} \\ &= 10\Omega + \left(\frac{50\Omega\measuredangle90^{\circ}}{11.18\measuredangle63.43^{\circ}}\right) \\ &= 10 + \left(4 + j2\right) = 14 + j2 = 14.14\measuredangle8.13^{\circ} \\ I_{T} &= \frac{100\measuredangle0^{\circ}}{14.14\measuredangle8.13^{\circ}} = \boxed{7.07\measuredangle - 8.13^{\circ}} \\ I_{L} &= \frac{I_{T}R_{1}}{R_{1} + Z_{L}} = \frac{7.07\measuredangle - 8.13^{\circ}(5)}{5 + j10} \\ &= \frac{35.36\measuredangle - 8.13^{\circ}(5)}{11.18\measuredangle63.43^{\circ}} = \boxed{3.162\measuredangle - 71.56^{\circ}} \\ IR_{1} &= I_{T} - I_{L} \\ &= 7.07\measuredangle - 8.13^{\circ} - \left(3.162\measuredangle - 71.56^{\circ}\right) \\ &= \left(7 - j1\right) - \left(1 - j3\right) = 6 + j2 = \boxed{6.325\measuredangle18.43^{\circ}} \end{aligned}$$

FE Review Test Masters	AC Circuits				
9/10/2011		PAGE - 9)		
Problem 1 : The series circuit of R = 8 ohms and L = 0.02 Henrys has an applied voltage of:					
$v(t) = 283 \sin(300t + 90^{\circ})$. Find	d the current i(t).				
$v(t) = 283 \sin(300t + 90^\circ)$					
$= 283 \cos(300^{+} + 90^{\circ} + 90^{\circ})$					
$= 283 \cos (300 \dagger + 180^{\circ})$					
$\overline{V} = \frac{283}{\sqrt{2}} \measuredangle 180^\circ = 200.1 \measuredangle 180^\circ$	$\Theta \omega = 300 \text{ rad/s}$				
$X_{L} = \omega L = 300(0.02) = 6\Omega$					
$\overline{I} = \frac{\overline{V}}{Z_{T}} = \frac{200.1V \measuredangle 180^{\circ}}{8\Omega + j6\Omega} = \frac{200}{10}$	$\frac{0.1 \sqrt{180^{\circ}}}{\sqrt{36.87^{\circ}}} = 20.01 \cancel{143.1^{\circ}}$				
$i(t) = 20.01\sqrt{2}\cos(300t + 143.1)$	l°)				
$= 28.3 \sin(300t + 143.1^{\circ} - 9)$	$90^{\circ}) = 28.3 \sin(300 + 53.1^{\circ})$				

Of course, knowing where we were going to end up, you could have left out several steps including the conversion to COS (since we were going to end up back at SIN anyway).

Problem 2: Calculate the impedance, Z_2 , in the series circuit shown below:



AC Circuits

Problem 3: In the series circuit shown below, the **effective** (rms) value of the current is 5 amps. What are the readings on the voltmeter placed 1st across the entire circuit and then across each element?



Remember that voltmeters do not measure phase angle

$$\overline{V}_{T} = I_{T}Z_{T}$$

$$= 5A \measuredangle 0^{\circ} (2\Omega + j4\Omega - j6\Omega)$$

$$= 5A \measuredangle 0^{\circ} (2\Omega - j2\Omega)$$

$$= 10 - j10 = 14.14 \measuredangle 45^{\circ}$$

$$= 14.14V$$

$$V_{R} = I_{T}R$$

$$= 5A \measuredangle 0^{\circ} (2\Omega) = 10V$$

$$\overline{V}_{L} = I_{T}Z_{L}$$

$$= 5A \measuredangle 0^{\circ} (4\Omega \measuredangle 90^{\circ}) = 20V$$

$$\overline{V}_{C} = I_{T}Z_{C}$$

$$= 5A \measuredangle 0^{\circ} (6\Omega \measuredangle - 90^{\circ}) = 30V$$

Problem 4: The two impedances \mathbf{Z}_1 and \mathbf{Z}_2 shown are in series with a voltage of $V = 100 \measuredangle 0^\circ$. Find the voltage across each impedance.



$$\begin{split} \mathbf{I}_{\mathsf{T}} &= \frac{\mathsf{V}}{\mathsf{Z}_{\mathsf{T}}} = \frac{100\mathsf{v}\measuredangle0^{\circ}}{10 + 4.47\measuredangle63.4^{\circ}} \\ &= \frac{100\mathsf{v}\measuredangle0^{\circ}}{10 + (2 + \mathsf{j}4)} = \frac{100\mathsf{v}\measuredangle0^{\circ}}{12 + \mathsf{j}4} \\ &= \frac{100\mathsf{v}\measuredangle0^{\circ}}{12.65\measuredangle18.42^{\circ}} = \boxed{7.9A\measuredangle - 18.42^{\circ}} \\ \mathsf{V}_{\mathsf{R}} &= \mathbf{I}_{\mathsf{T}}\mathsf{R} = (7.9A\measuredangle - 18.42^{\circ})\mathbf{10\Omega} \\ &= \boxed{79V\measuredangle - 18.42^{\circ}} = \boxed{74.9V - \mathsf{j}25V} \\ \mathsf{V}_{\mathsf{Z}} &= \mathbf{I}_{\mathsf{T}}\mathsf{Z}_{\mathsf{Z}} \\ &= (7.9A\measuredangle - 18.42^{\circ})4.47A\measuredangle63.4^{\circ} \\ &= \boxed{35.31V\measuredangle45^{\circ}} = \boxed{25V + \mathsf{j}25V} \\ \end{split}$$

Ch

$$VR + VZ = (74.9V - j25V) + (25V + j25V)$$

= 99.9V ≈ 100V

AC Circuits

The Power Triangle

Real Power is defined as:



Where θ is the Power Factor angle (it also turns out to be the impedance angle). The Power Factor angle is measured <u>from the voltage phasor to the current phasor</u>.

The Power Factor (pf) itself is defined as: $\mathbf{pf} = \mathbf{cos} \theta$ The terms leading and lagging are usually attached to the Power Factor. These terms are <u>defined by the current thru the load</u>.

- If the <u>current waveform thru the load is leading the voltage waveform</u> across the load then the **power factor is a LEADING pf**.
- If the <u>current waveform thru the load is lagging the voltage waveform</u> across the load then the **power factor is a LAGGING pf**.

Reactive power is defined as:

$$Q = \frac{1}{2} E_p I_p \sin \theta \quad \text{Volt-Amperes Reactive (VARS)}$$
$$= E_{rms} I_{rms} \sin \theta$$

Apparent power is defined as:

$$S = \frac{1}{2} E_p I_p \quad \text{Volt-Amperes } (VA)$$
$$= E_{rms} I_{rms}$$
$$= P \pm jQ$$

For <u>totally resistive</u> circuits, $\theta = 0$, so Real power is:

$$P = E_{rms}I_{rms} = \frac{E_{rms}^2}{R_T} = I_{rms}^2R_T$$

ELI the ICE person

ELI \rightarrow Voltage <u>Leads</u> Current in Inductive circuits (or Current <u>Lags</u> Voltage since the current phase angle is negative),



ICE→Current Leads Voltage in Capacitive circuits (since the current phase angle is positive)



Real Power = $P = \frac{R}{R} = \frac{1.44 \text{ kW}}{10\Omega}$ Reactive Power = $Q = E_{\text{rms}}I_{\text{rms}} \sin \theta = 5 \sin 68.2^{\circ} = 3.877 \text{ kVA}(.9285) = 3.6 \text{ kVAR}$ or





AC Circuits

RESONANCE

Up to this point, any sources we had in a circuit were required to have a **CONSTANT FREQUENCY**. In fact, it is a very helpful when solving for voltages and currents to be able to assume that only the phase angle will change. The Frequency has always stayed constant. As a matter of fact, once you converted into the **PHASOR DOMAIN**, all that the frequency was needed for was for calculating inductive and capacitive reactance.

The study of resonance is the study of AC <u>circuit behavior when the frequency of the AC</u> <u>sources is allowed to change</u>.

SERIES RESONACE

The circuit shown here consists of a **source**, an **R**, **L**, and **C**. We assume that the source peak value will remain constant, but the frequency will be allowed to vary. Now we need to develop and understanding of how the voltages, currents, and impedances will vary with the frequency and after being exposed to each other.



The impedance of the circuit (in the time domain) is simply: $\mathbf{Z} = \mathbf{R} + \mathbf{j}\mathbf{X}_{L} - \mathbf{j}\mathbf{X}_{C}$. If we were to backtrack and substitute the frequency equivalents we would get:

$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right), \text{ and the current equation: } I = \frac{V}{R + j \left(\omega L - \frac{1}{\omega C} \right)}$$



There comes a point on the graph where the capacitive and inductive reactance's CANCEL each other out: $\omega L = \frac{1}{\omega C}$.

When this cancellation occurs in a **SERIES RESONANT circuit**, the:

- Impedance goes through a MINIMUM and
- The current goes through a MAXIMUM.

Of course, this only occurs at a specific frequency known as the "SERIES RESONANT FREQUENCY".

$$\omega_r = \frac{1}{\sqrt{LC}}$$
 or $f_r = \frac{1}{2\pi\sqrt{LC}}$

EXAMPLE PROBLEM:

Determine the SERIES RESONANT FREQUENCY (in hertz) if $C = 0.02\mu$ F, L = 0.1H, R = 100 ohms and the source voltage is $60\nu \measuredangle 0^{\circ}$. Also determine the maximum current at resonance.

$$f_{r} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{\left(0.1H\right)\left(0.02\mu f\right)}} = 3.559 \text{khz} \simeq \boxed{3.56 \text{khz}}$$
$$I_{r}(\text{max}) = \frac{V}{R} = \frac{60v}{100\Omega} = 600 \text{mA} [\text{since the reactances cancelled}]$$

AC Circuits

Quality Factor (Q)

A very important characteristic of resonance is the width of the curve around the resonance frequency. This width is called the Quality Factor, or more commonly referred to as Q.

> The greater the Q, the sharper and narrower the resonant curve (the more selective it becomes)

The Q of a Series Resonant Circuit is given by: $Q_s = \frac{\omega_r L}{D}$.

BANDWIDTH (BW)

Another important measure of the resonant curve is **BANDWIDTH (BW)**. This bandwidth is measured in hertz and is the difference in frequencies between the half-power points on the



For this graph, the actual BW: 250 Hz - 180 Hz = 70 Hz.

AC Circuits

PAGE - 17

SERIES RESONANCE EXAMPLE PROBLEM:

Consider a series circuit with the following values: L = 54mH and C = 470pF.

A) What is the resonant frequency?

$$f_{r} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(54 \cdot 10^{-3} \text{H})(4700 \cdot 10^{-12} \text{F})}} = 9.99 \text{kHz} \approx \boxed{10 \text{kHz}}$$

B) What value of R is required to provide a BW of 100 Hz?

$$Q_{s} = \frac{\omega_{r}L}{R}$$

and $f_{r} = 10$ khz
$$BW = \frac{f_{r}}{Q}$$

$$R = \frac{\omega_{r}L}{Q} = \frac{2\pi f_{r}L}{Q}$$
$$Q = \frac{f_{r}}{BW}$$
so,
$$R = \frac{2\pi f_{r}L}{\frac{f_{r}}{BW}} = \frac{2\pi f_{r}L(BW)}{f_{r}}$$
$$R = 2\pi L(BW) = 2\pi (54mH)(100Hz) = 33.93\Omega$$

PARALLEL RESONACE

A second type of **RESONACE** is **PARALLEL RESONANCE**. Rather than go thru the math with this type we will just focus on the equations and <u>the effect on the circuit</u> at **RESONANCE**. Some of the equations are the same as for the SERIES RESONANCE circuits.



Note the difference in this equation for Q_p from the equation for Q_s in SERIES RESONANCE.

$$\mathsf{BW} = \frac{\mathsf{f}_{\mathsf{r}}}{\mathsf{Q}}$$

 Q_p

AC Circuits

PAGE - 18

PARALELL RESONANCE EXAMPLE:

For a parallel circuit with R = $100k\Omega$, C = $.001\mu$ F, L = 15mH, V = $20 \measuredangle 0^{\circ}$:

a) What is the resonant frequency, f_r ?

$$f_{r} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(15\text{mH})(.001\mu\text{F})}} = \boxed{41.09\text{kHz}}$$

b) What if the Q and the BW?

$$Q = \frac{R}{\omega_{r}L} = \frac{R}{2\pi f_{r}L} = \frac{100k\Omega}{2\pi (41.09kHz)(15mH)} = \boxed{25.82}$$
$$BW = \frac{f_{r}}{Q} = \frac{41.09kHz}{25.82} = \boxed{1.59kHz}$$

c) What is the current of from the source at resonance? $I = \frac{V}{R} = \frac{20v}{100k\Omega} = 200\mu A$

RESONANCE REVIEW

- Capacitive reactance decreases as the applied frequency increases
- Inductive reactance increases as the applied frequency increases
- At some specific frequency $X_c = X_L$ and they will cancel out.



