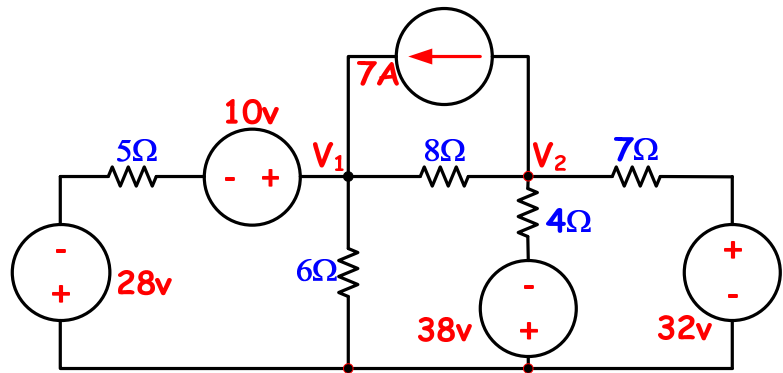


For the circuit shown,

- Write the **node voltage equations**,
- Arrange the results of (a) in a mathematical standard form and **solve for the node voltages**, and
- Determine the voltage across the 5 ohm resistor.**

Solution:



Node V_1

$$0 = \frac{V_1 - (-18\text{V})}{5\Omega} - 7\text{A} + \frac{V_1 - V_2}{8\Omega} + \frac{V_1}{6\Omega}$$

$$\left[7\text{A} = \frac{V_1 + 18\text{V}}{5\Omega} + \frac{V_1 - V_2}{8\Omega} + \frac{V_1}{6\Omega} \right] \cdot 120\Omega$$

$$840 = 24[V_1 + 18\text{V}] + 15[V_1 - V_2] + 20V_1$$

$$840 = 24V_1 + 432 + 15V_1 - 15V_2 + 20V_1$$

$$408 = 59V_1 - 15V_2$$

Node V_2

$$0 = \frac{V_2 - (32\text{V})}{7\Omega} + 7\text{A} + \frac{V_2 - (-38\text{V})}{4\Omega} + \frac{V_2 - V_1}{8\Omega}$$

$$\left[-7\text{A} = \frac{V_2 - 32\text{V}}{7\Omega} + \frac{V_2 + 38\text{V}}{4\Omega} + \frac{V_2 - V_1}{8\Omega} \right] \cdot 56\Omega$$

$$-392 = 8[V_2 - 32\text{V}] + 14[V_2 + 38\text{V}] + 7[V_2 - V_1]$$

$$-392 = 8V_2 - 256 + 14V_2 + 532 + 7V_2 - 7V_1$$

$$-392 + 256 - 532 = -7V_1 + (8 + 14 + 7)V_2$$

$$-668 = -7V_1 + 29V_2$$

$$\begin{bmatrix} 408 \\ -668 \end{bmatrix} = \begin{bmatrix} 59 & -15 \\ -7 & 29 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1.128\text{V} \\ -22.762\text{V} \end{bmatrix}$$

$$V_{5\Omega} = V_1 - (-18\text{V}) = -1.128\text{V} - 18\text{V} = -19.128\text{V}$$

