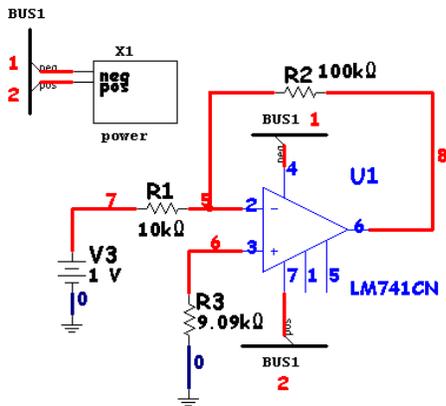



Transfer Function Analysis in Multisim




Note the circuit to the left. (R3 is not calculated correctly on purpose). Note that the power supply sub-circuit has been connected in via the bus method as discussed in a separate tutorial.

If a Transfer Function Analysis is desired, choose **Simulate/Analysis/Transfer Function** from the pull-down menu.

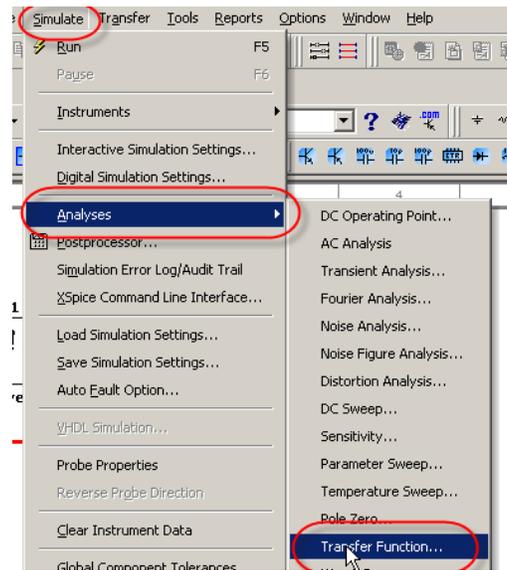
Once there, it will need to know the name of the **input source** first. Be careful to use the correct one since the sub-circuit has two voltage sources in it as well. For this example I have entered **vv3** (for V3). Then for the **output node** I have entered **node number 8**. If the node names are not present, go to **Options/Sheet Properties/Circuit** and choose **Show All**.



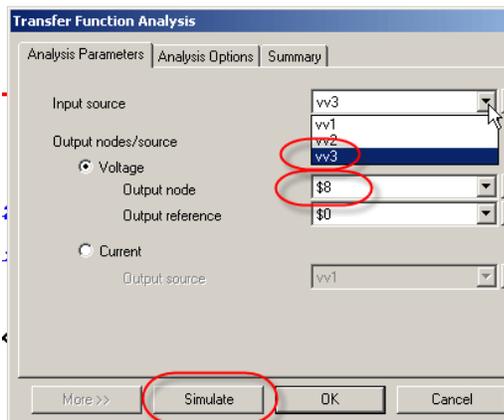Directly below the Output node is **"Output Reference"**. You need to make sure the **circuit's ground node** (should be 0 if connected correctly) here. If this is not done the answers will be incorrect.



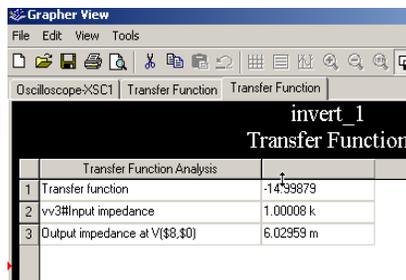Once this has been accomplished, select **Simulate** and the window shown below should open and provide the needed answers.



Note that this result will also be in the Grapher.